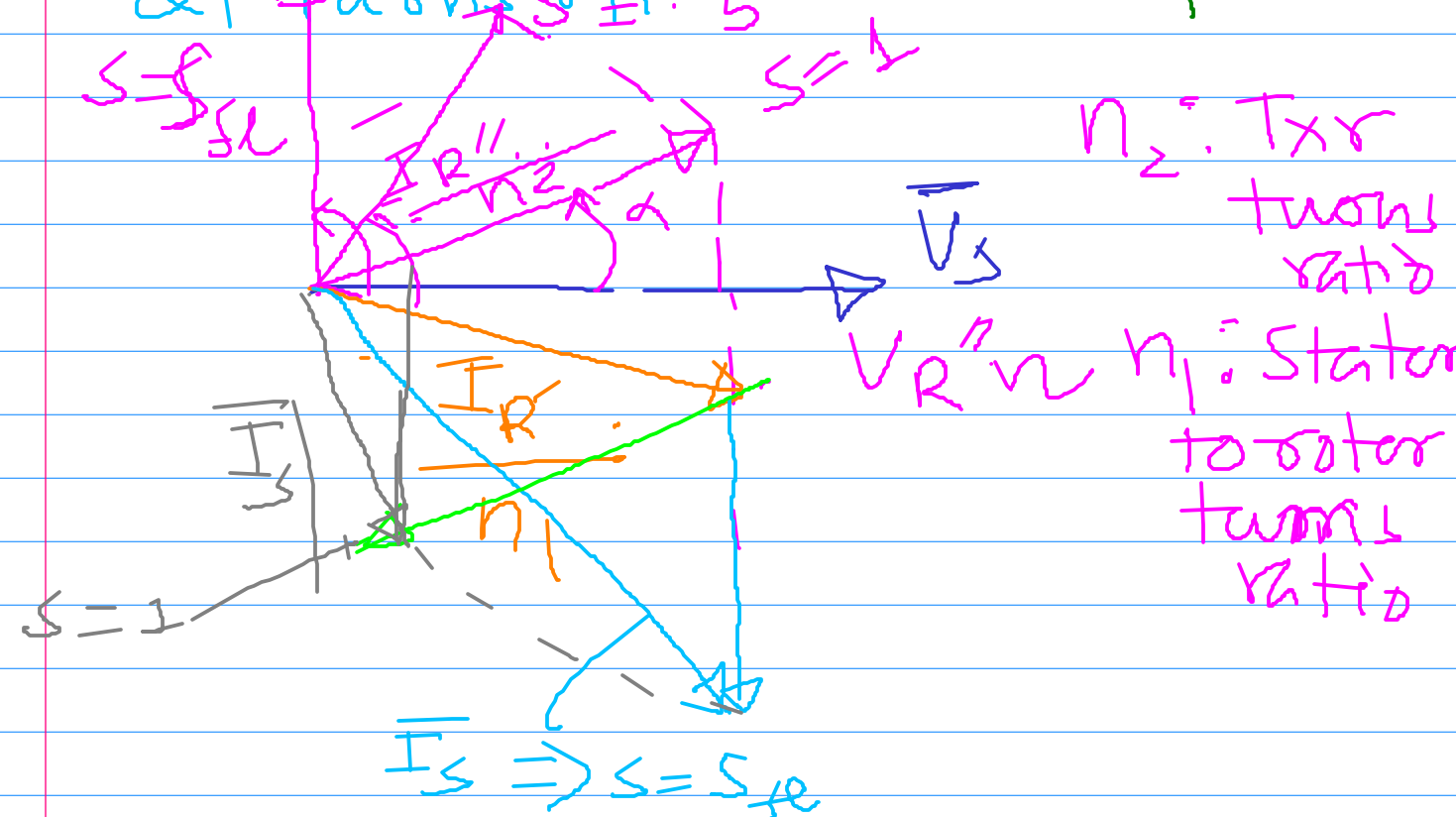
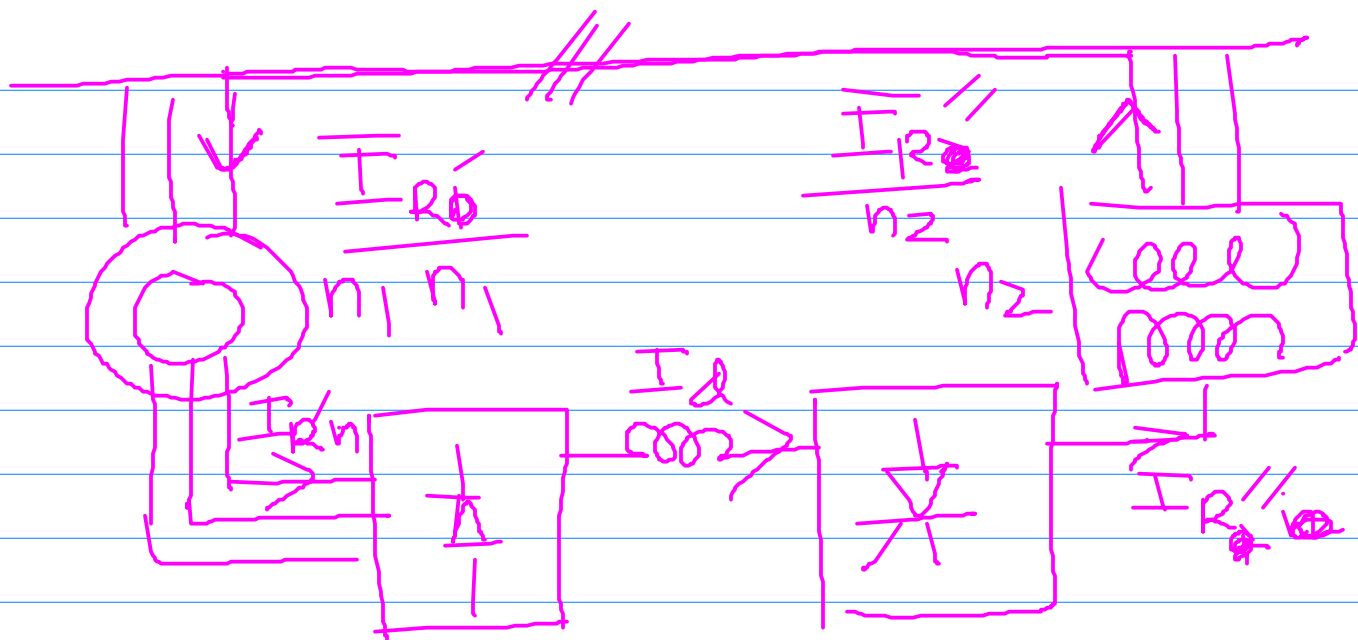


$V_{R''} < 0$  at the instant  $Q_1$  turns off.





$$I_s = \frac{I_R}{n_1} - \frac{I_R'}{n_2}$$

415V (L-L)

For a 500 Hp, Wound Rotor Machine the rated slip is 3% and the slip at maximum torque is 12%. Ignore all other resistances and reactances except the rotor resistance ( $R_2$ ) and ( $X_2$ ). This is a 4 pole, 50 Hz machine and it is used in the slip power recovery drive. Find the firing angle  $\alpha$  for running the rotor at 500 rpm, 1000 rpm and 1200 rpm. Assume,  $n_1 = n_2 = 1$ .