
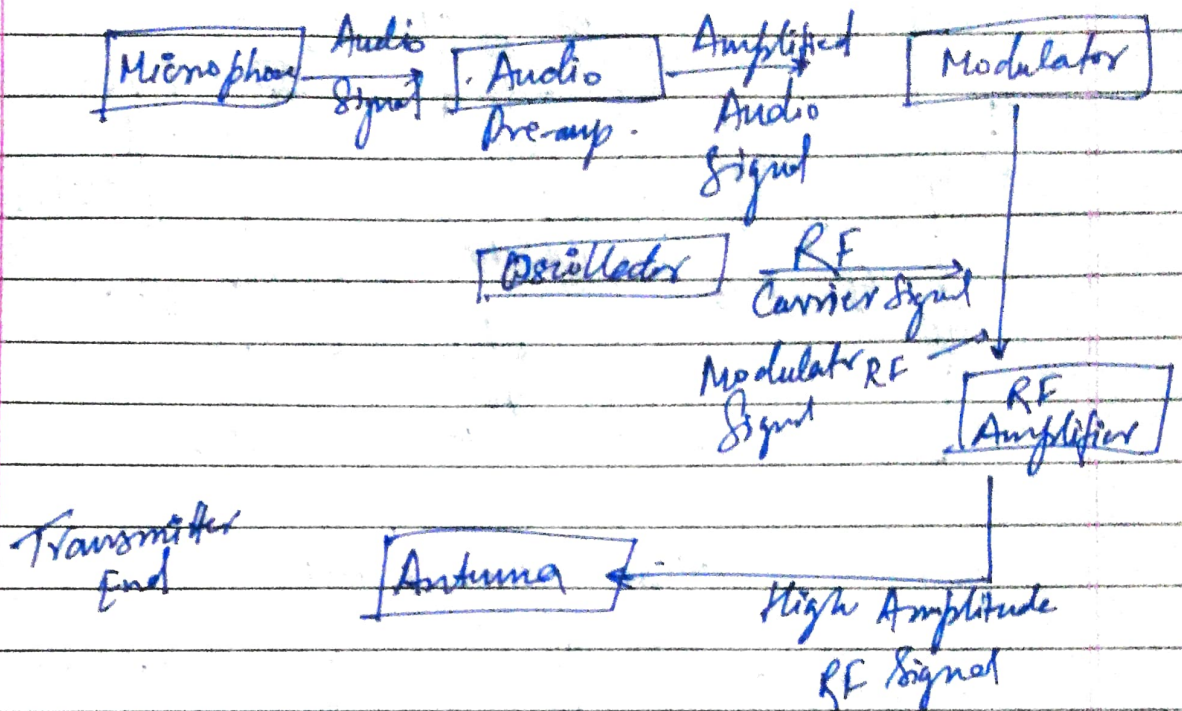


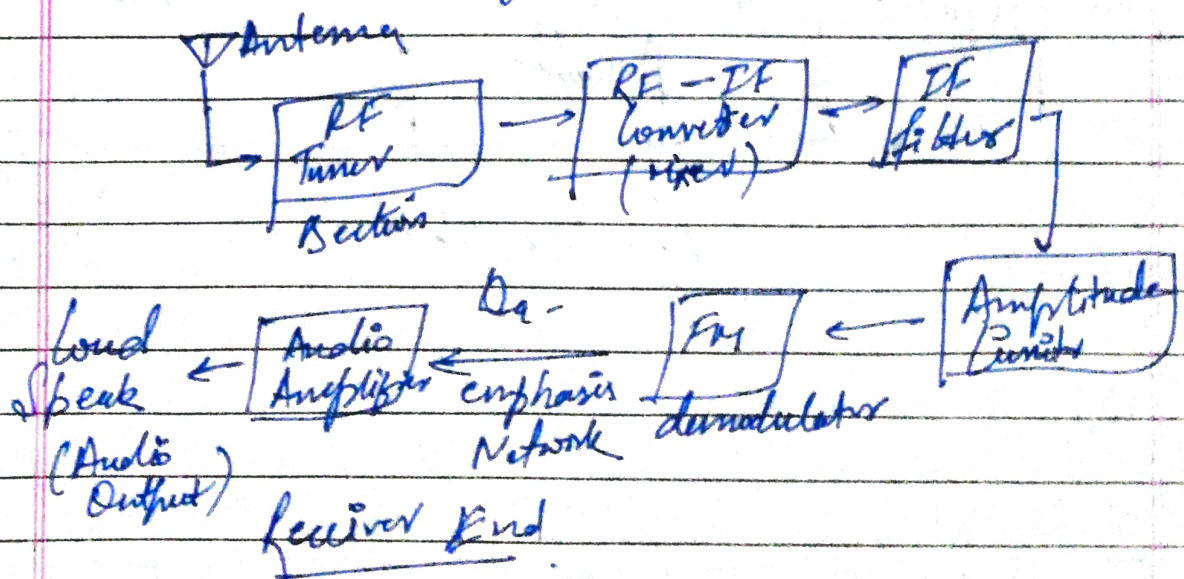
We represent the circuit transmitter diagram concept in block diagram.




On the receiver end,
the block diagram can be represent as:-



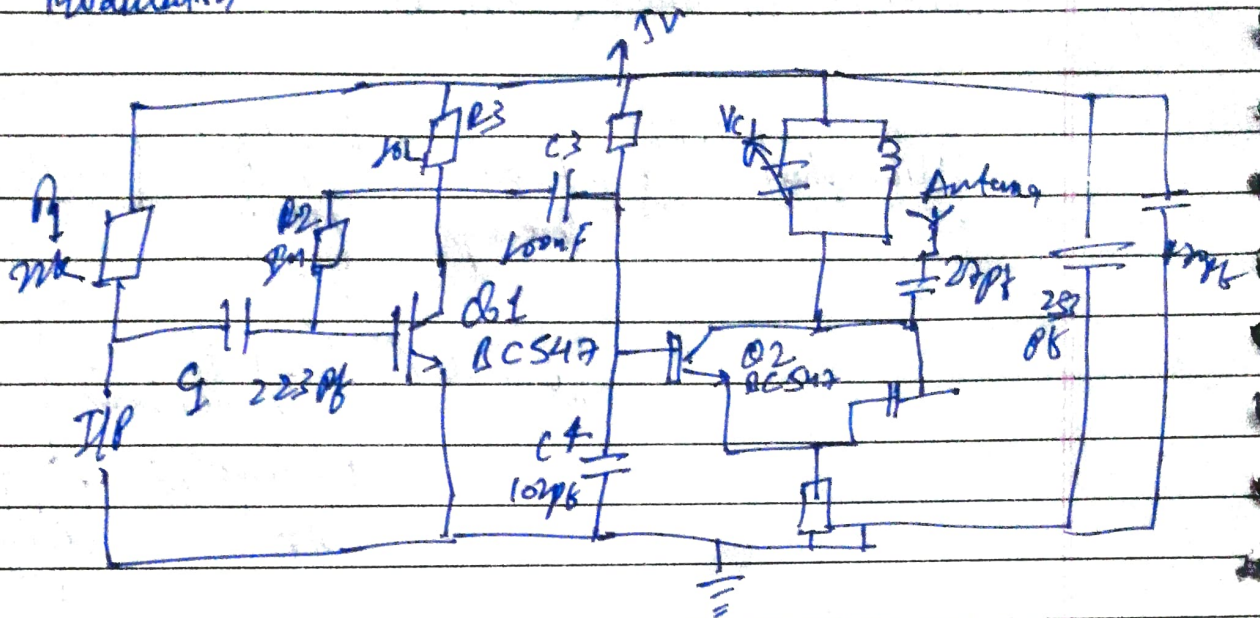A circuit diagram is presented on the next page that transmits audio signal with freq. Modulation.



Transmitter Circuit

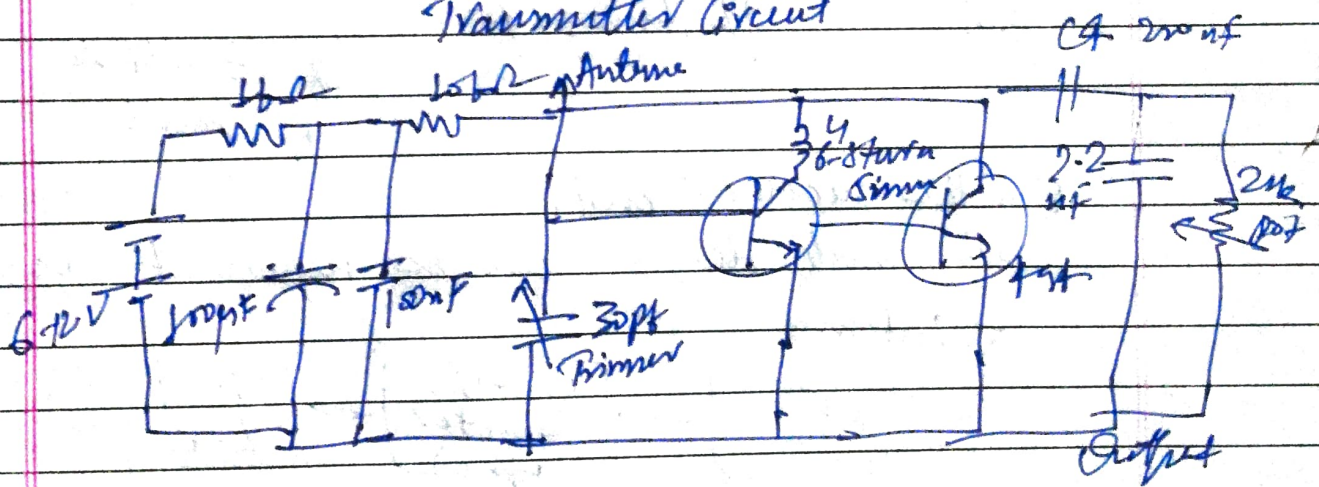

Receiver Ckt