

# Analog Signal Processing


Date:	/	/
Page:		

Pratyush Jaimal  
18GE35064

## Lecture-11

Q.S.

In S-domain

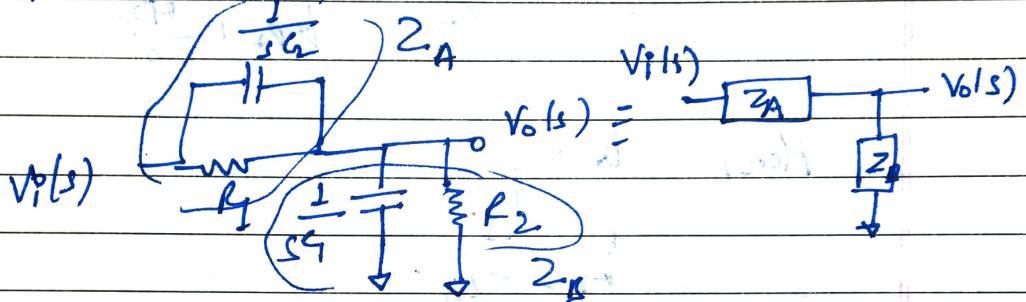

$$\text{Here, } Z_A = \frac{1}{sC_1} \parallel R_1$$

$$= \frac{R_1}{sC_1 R_1 + 1}$$

$$Z_B = \frac{1}{sC_2} \parallel R_2 = \frac{R_2}{sC_2 R_2 + 1}$$

$$V_o(s) = \frac{Z_B}{Z_A + Z_B} \cdot V_i(s)$$

$$= \frac{\frac{R_2}{sC_2 R_2 + 1}}{\frac{R_1}{sC_1 R_1 + 1} + \frac{R_2}{sC_2 R_2 + 1}} V_i(s)$$

$$= \frac{R_2 (1 + sR_1 C_1)}{R_1 + sR_1 R_2 C_1 + R_2 + sR_2 C_2} V_i(s)$$

$$V_o(s) = \frac{R_2 + s R_2 L C_2}{(G + R_2) + s(G + G_2)(R_1 R_2)} V_i(s)$$

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{R_2 (s + s R_2 C_2)}{(G + R_2) + s G R_2 (G + G_2)}$$

$$\text{DC gain} = \left| \lim_{s \rightarrow 0} H(s) \right|$$

$$= \frac{R_2}{G + R_2}$$

$$\text{High frequency gain} = \left| \lim_{s \rightarrow \infty} H(s) \right|$$

$$= \frac{R_2 R_2 L C_2}{R_1 R_2 (G + G_2)} = \frac{L C_2}{R_1 (G + G_2)}$$


$$= \frac{G_2}{G + G_2} \cdot \frac{C_2}{G + G_2}$$

$$\text{Pole } \omega_p = -\frac{L}{(G + G_2)} \left( \frac{R_1 + R_2}{R_1 R_2} \right) = -\frac{L}{G + G_2} \cdot \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$


$$\text{zero } \omega_z = -\frac{1}{R_1 C_2}$$

To attain low pass filter,


pole  $\omega_0 < \text{zero } \omega_2$

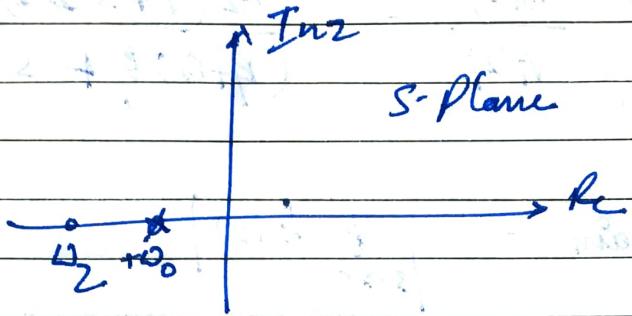


main Characteristics of low pass filter

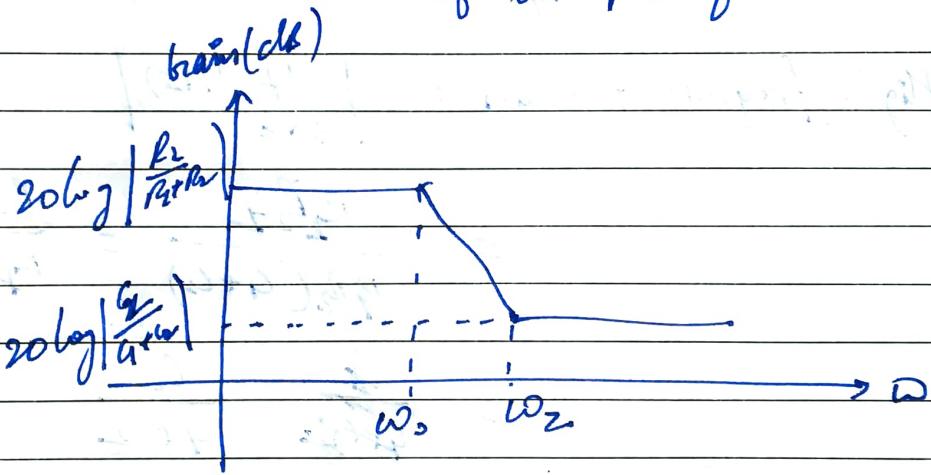

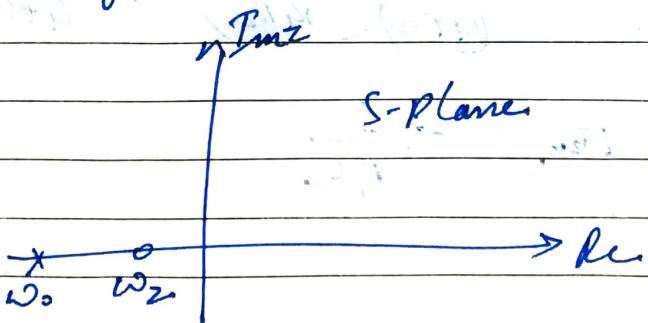
To attain High Pass filter, zero  $\omega_2 < \text{pole } \omega_0$


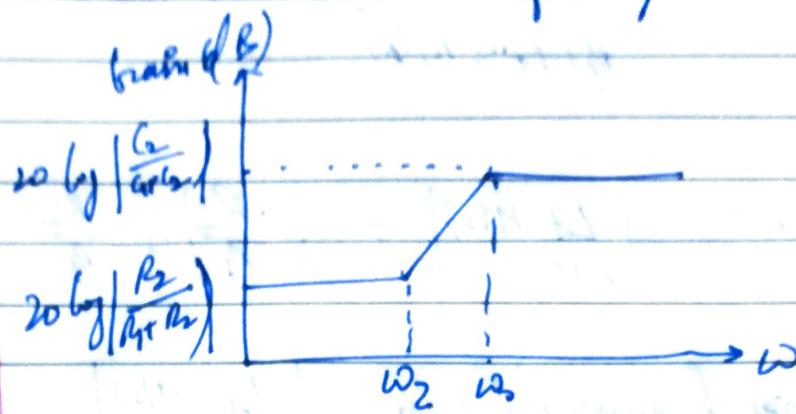
## Gain Characteristics of High Pass Filter



$\Omega_2 =$  In s-domain

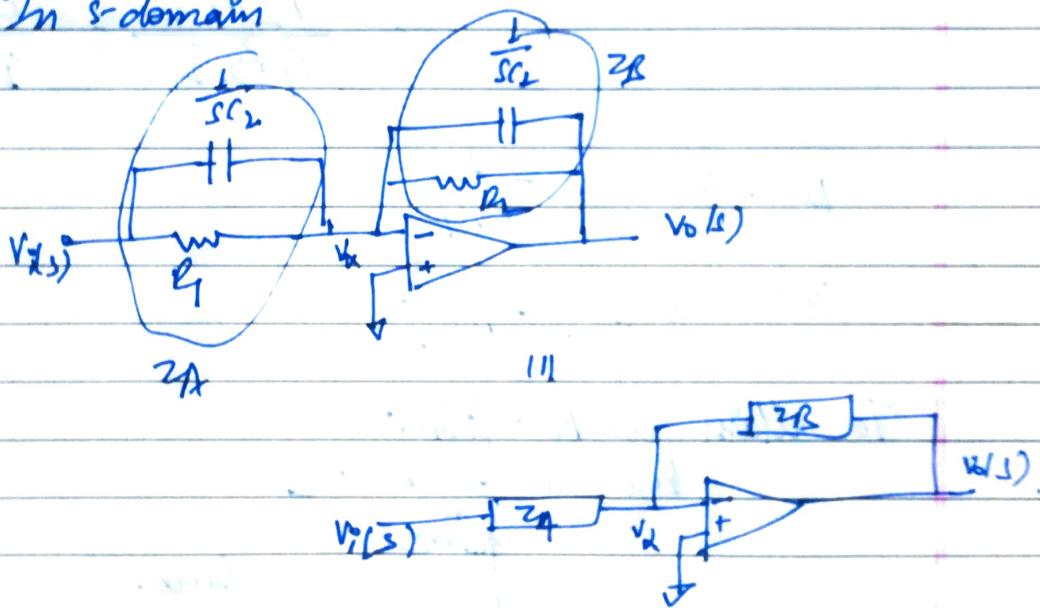

Here  $V_x = 0$  (using virtual grounding concept)  
 $V_t = V^+$

$$Z_A = \frac{R_1}{1 + sR_1C_2}, \quad Z_R = \frac{R_2}{1 + sR_2L_2}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{-Z_R}{Z_A} = \frac{-R_2(1 + sR_1C_2)}{R_1(1 + sR_2L_2)}$$

$$H(s) = \frac{-R_2(1 + sR_1C_2)}{R_1(1 + sR_2C_1)}$$

$$\text{DC Gain} = \left| \lim_{s \rightarrow 0} H(s) \right| = \left| \frac{-R_2}{R_1} \right| = \frac{R_2}{R_1}$$

$$\text{High voltage frequency Gain} = \left| \lim_{s \rightarrow \infty} H(s) \right|$$

$$= \frac{R_2 R_1 C_1}{R_1 R_2 C_2} = \frac{C_1}{C_2}$$

$$\text{Pole } \omega_0 = -\frac{1}{R_2 C_1}$$


$$\text{Zero } \omega_z = -\frac{1}{R_1 C_2}$$

To attain low Pass filter

$$\text{Pole } \omega_0 < \text{zero } \omega_z$$

$j\omega$

s-Plane

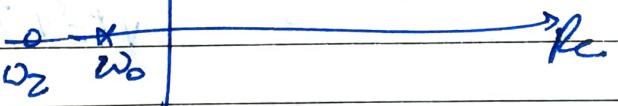


Gain Characteristics for LPF

Gain (dB)


$$20 \log \left( \frac{R_2}{R_1} \right)$$
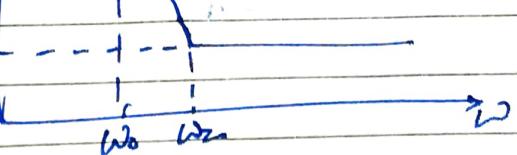
$$20 \log \left( \frac{C_1}{C_2} \right)$$




To attain High Pass Filter,

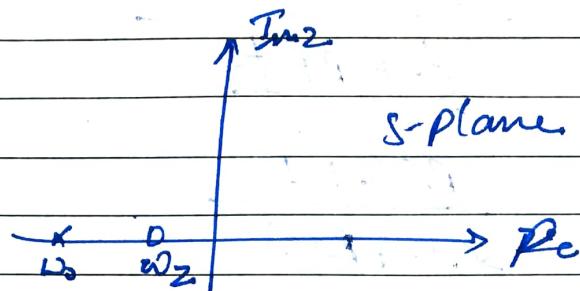pole  $\omega_0 > \text{zero } \omega_2$ .




Grain Characteristics for HPF

Grain (dB)

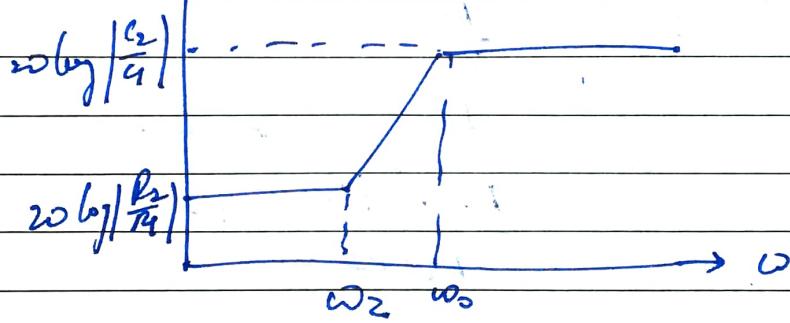

## # Lecture 15

$\frac{d}{dt}$  In s-domain

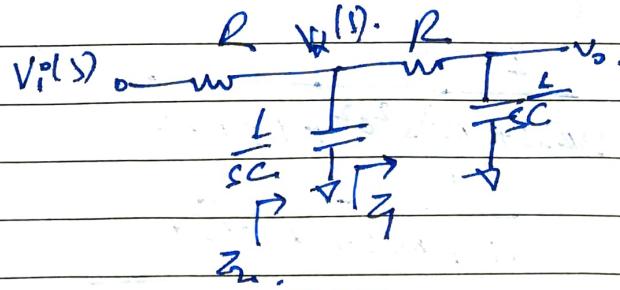

$$\boxed{q = R + \frac{L}{sc}} ; z_2 = \frac{L}{sc} || z$$

$$\begin{aligned}
 Z_2 &= \frac{\frac{1}{sc}}{1 + \frac{1}{sc}} \\
 &= \frac{\left(\frac{1}{sc}\right) \times \left(1 + \frac{1}{sc}\right)}{\frac{1}{sc} + 1 + \frac{1}{sc}} \\
 &= \frac{RSC + 1}{sc(2 + RSC)}
 \end{aligned}$$

$$\begin{aligned}
 \frac{V_o(s)}{V_i(s)} &\stackrel{V_o(s)}{=} \frac{Z_2}{R + Z_2} \\
 &= \frac{\frac{1}{sc}}{\frac{R}{sc} + 1} \\
 &= \frac{1}{RSC(2 + RSC) + sc} \quad -(i)
 \end{aligned}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{\frac{1}{sc}}{R + \frac{1}{sc}} = \frac{1}{(1 + RSC)} \quad -(ii)$$

Multiplying eq (i) & (ii).


$$\begin{aligned}
 \frac{V_o(s)}{V_i(s)} &= \frac{1}{2RSC + R^2s^2c^2 + 1 + RSC} \\
 \frac{V_o(s)}{V_i(s)} &= \frac{1}{1 + 2RSC + R^2s^2c^2}
 \end{aligned}$$

$$\boxed{\frac{V_o(s)}{V_i(s)} = \frac{1}{C^2R^2 \left( s^2 + \frac{2s}{RC} + \frac{1}{R^2C^2} \right)}}$$

$\alpha_2 =$ 

In s-domain

from virtual ground concept.

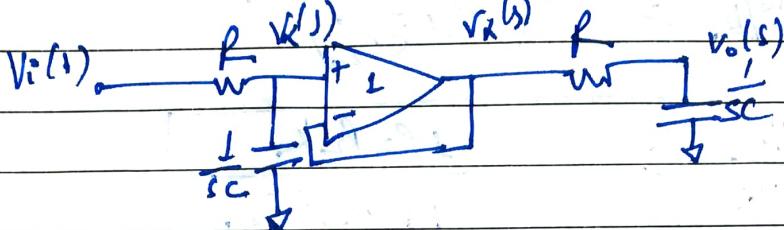

$$\frac{V_o(s)}{V_i(s)} = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} = \frac{1}{1 + RSC} \quad \text{--- (i)}$$

$$\frac{V_o(s)}{V_R(s)} = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} = \frac{1}{1 + RSC} \quad \text{--- (ii)}$$


Multiplying Eqs (i) &amp; (ii)

$$\frac{V_o(s)}{V_i(s)} = \frac{1}{(1 + RSC)^2} = \frac{1}{R^2 C^2 \left( \delta^2 + \frac{2\delta}{R} + \frac{1}{R^2 C^2} \right)}$$

#

Lecture - 16 $\alpha_2 =$ 

In s-domain

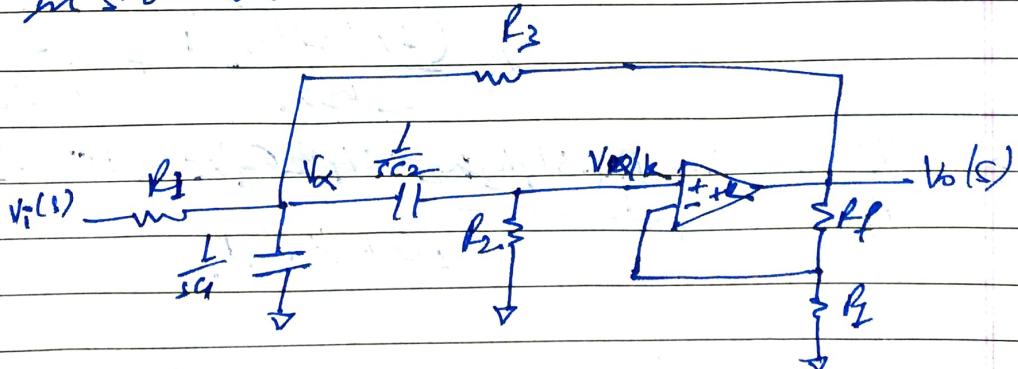

Here,

$$\frac{V_o}{k} = \left( \frac{R_2}{R_2 + \frac{1}{SC_2 k}} \right) V_x$$

$$\boxed{\frac{V_o}{V_x} = \frac{SC_2 R_2 k}{1 + R_2 S C_2}}$$

Here,

$$\frac{V_o - V_x}{R_L} = \frac{V_x - V_o}{R_3} + \frac{V_x}{\frac{1}{SC_2 k}} + \frac{V_x}{\frac{1}{SC_2 k} + R_2}$$

$$\Rightarrow \frac{V_o}{R_L} = V_x \left( \frac{1}{R_1} + \frac{1}{R_3} + \frac{k}{SC_2 k} SG + \frac{SC_2}{1 + R_2 S C_2} \right) - \frac{V_o}{R_3}$$

$$\Rightarrow \frac{V_o}{R_L} = \frac{V_o (1 + R_2 S C_2)}{SC_2 R_2 k} \left( \frac{1}{R_1} + \frac{1}{R_3} + SG + \frac{SC_2}{1 + R_2 S C_2} \right) - \frac{V_o}{R_3}$$

$$\Rightarrow \frac{V_o}{R_L} = V_o \left( \left( \frac{(1 + R_2 S C_2)}{SC_2 R_2 k} - 1 \right) \frac{1}{R_3} + \frac{1 + R_2 S C_2}{(B_C R_2 k) R_1} \right. \\ \left. + \frac{(1 + R_2 S C_2) G}{C_2 R_2 k} + \frac{1}{R_2 k} \right)$$

$$\Rightarrow \frac{V_o}{R_L} = \frac{V_o (R_1 + S R_1 R_2 S C_2 - S R_1 R_2 E_2 k + R_2 + S C_2 R_2 R_2)}{8 C_2 R_2 k R_3 R_1} \\ + \frac{8 R_3 R_1 (1 + R_2 S C_2) G}{8 C_2 R_3 R_1} \\ + \frac{S C_2 R_3 R_1}{8 C_2 R_3 R_1}$$

$$\Rightarrow \frac{V_o}{R} = v_0 \left( s^2 R_2 R_3 C_2 G + \frac{s(R_1 C_2 - R_1 R_2 G_k + R_2 C_2 + R_1 R_3 G + R_1 R_3 C_2) + R_1 + R_3}{s C_2 R_2 k R_1 R_3} \right)$$

$$\Rightarrow \frac{V_o(s)}{V_i} = \frac{s C_2 R_2 L R_3}{s^2 R_1 R_2 R_3 G C_2 + s(R_1 R_2 C_2 - R_1 R_2 G_k + R_2 C_2 + R_1 R_3 G + R_1 R_3 C_2) + (R_1 + R_3)}$$

$$\Rightarrow \frac{V_o(s)}{V_i(1)} = \frac{\frac{sL}{R_1 G}}{\underbrace{s^2 + \frac{1}{(1-k)} R_1 R_2 C_2 + (R_1 + R_3) R_2 C_2 + R_1 R_3 G}_{R_1 R_2 R_3 G C_2} + \frac{(R_1 + R_3)}{R_1 R_2 R_3 G C_2}}$$

Comparing denominator with the standard form,

$$s^2 + \frac{R_1 R_2}{k} + \omega_0^2 \approx 0;$$

We got

$$\omega_0 = \sqrt{\frac{R_1 + R_3}{R_1 R_2 R_3 G C_2}} = \sqrt{\frac{1 + \frac{R_1}{R_3}}{R_1 R_2 G C_2}}$$

$$\alpha =$$

$$\frac{\omega_0}{Q} = \frac{(1+k)}{R_3 G} + \frac{L}{R_2 G} + \frac{L}{G G} + \frac{L}{R_2 C_2}$$


$$\frac{\omega_0}{Q} = \left( \frac{L}{\sqrt{R_1 R_2 G C_2}} \right)^{-1} \left( \frac{1+k}{R_3 G} + \frac{L}{R_2 G} + \frac{L}{G G} + \frac{L}{R_2 C_2} \right)$$

$$\Rightarrow Q = \frac{\sqrt{R_1 R_2 G C_2} \left( \frac{1+k}{R_3 G} + \frac{L}{R_2 G} + \frac{L}{G G} + \frac{L}{R_2 C_2} \right)}{\sqrt{1 + \frac{R_1}{R_2}}} = \frac{(1+k) \sqrt{R_1 R_2 G}}{R_3 G} + \sqrt{\frac{R_1 C_2}{R_2 G}} + \sqrt{\frac{R_2 G}{G G}} + \sqrt{\frac{R_1 G}{R_2 C_2}}$$

$$Q = \frac{\sqrt{1 + \frac{R_1}{R_2}}}{\left( 1 + \frac{(1+k) R_1}{R_2} \right) \sqrt{\frac{R_2 C_2}{R_1 G}} + \sqrt{\frac{R_1 G}{R_2 G}} + \sqrt{\frac{R_1 G}{R_2 C_2}}}$$

#

## Lecture-20

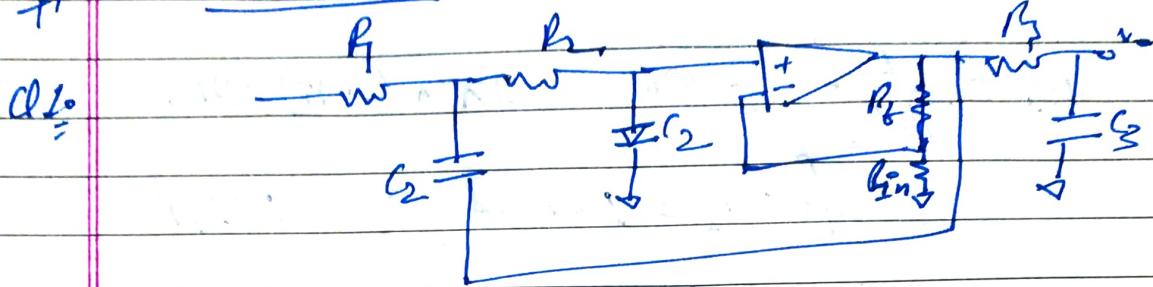

The equal component design,

$$R_1 = R_2 = R, \quad C_1 = C_2 = C$$

from generalized expression of Q,

$$\frac{(1-k)\sqrt{C_1 R_1}}{CR_2} + \sqrt{\frac{R_2 C_2}{R_1 C_1}} + \sqrt{\frac{C_2 R_3}{C_1 R_2}} = \frac{L}{L+1+(L-k)} = \frac{L}{2-k}$$

If  $\alpha = 1$ ,  
 $\Rightarrow k = 2 \Rightarrow L + \frac{R_F}{R_{IN}} = 2$

$$\boxed{R_F = R_{IN}} = 1 \text{ k}\Omega$$

Here,  $\omega_0 = \frac{1}{\sqrt{R_1 C_1 R_2 C_2}} = \frac{1}{RC} = 2\pi \times 1.45 \text{ MHz}$

let us assume  $L = 1 \text{ k}\Omega$

$$C = \frac{e \cdot L}{2\pi \times 1.45} \text{ NF} \approx 109 \text{ pF}$$

$$R_1 = R_2 = 1k\Omega, C_1 = C_2 = 109 \text{ pF}$$

$$\omega_3 = \frac{1}{R_3 C_3} = \omega_0 = 2\pi \times (1045) \text{ rad/s}$$


for  $R_3 = 1k\Omega$  &  $C_3 = 109 \text{ pF}$

$$\omega_0, R_3 = 1k\Omega$$

$$\text{&} C_3 = 109 \text{ pF}$$

Try Yourself:

Q2 In s-domain,

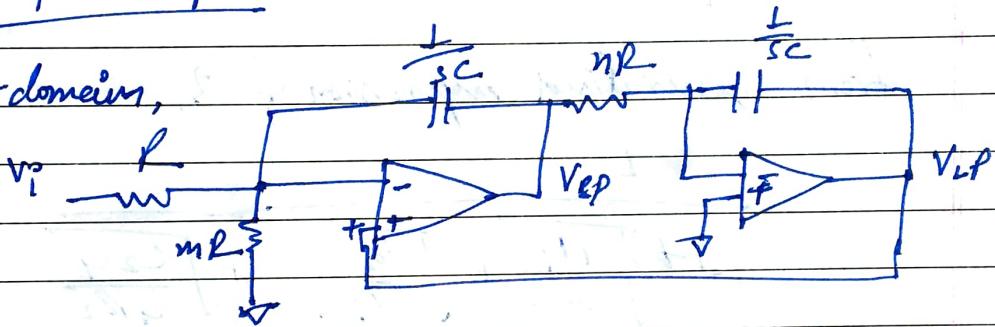

$$\frac{V_{op}}{nR} = -\frac{V_{LP}}{\frac{L}{SC}}$$

$$\Rightarrow \boxed{\frac{V_{op}}{V_{LP}} = -SCnR}$$

$$\frac{V_p - V_{LP}}{R} = \frac{V_{LP}}{mR} + \frac{V_{LP} - V_{op}}{\frac{L}{SC}}$$

70

$$\Rightarrow \frac{V_o}{R} = V_{LP} \left( \frac{L}{R} + \frac{L}{mR} + sC + s^2 nR \right)$$

$$\Rightarrow \frac{V_o}{R} = C^2 n R V_{LP} \left( \frac{(L+m)}{C^2 R^2 n m} + \frac{L}{n R C} s + s^2 \right)$$

$$\boxed{\frac{V_{LP}}{V_o} = \left( \frac{L}{C^2 n C^2} \right) \cdot \frac{L}{\left( s^2 + \frac{s}{n R C} + \frac{L+m}{C^2 R^2 n m} \right)}}$$

$$V_{LP} = -sCnR V_{LP}$$

$$\boxed{\frac{V_{LP}}{V_o} = \frac{-s}{R C \left( s^2 + \frac{s}{n R C} + \frac{L+m}{C^2 R^2 n m} \right)}}$$

Comparing denominator with

$$s^2 + \frac{\omega_0^2}{Q} s + \omega_0^2$$

$$\omega_0^2 = \frac{1+m}{n R C^2} \Rightarrow \omega_0 = \sqrt{\frac{1+m}{n R C^2}}$$

$$= \frac{L}{R C} \sqrt{\frac{L}{n} + \frac{L}{m n}}$$


$$\frac{\omega_0}{Q} = \frac{L}{n R C} \Rightarrow \boxed{\omega_0 = \frac{Q}{n R C}}$$

$$Q = \omega_0 n R C$$

$$= \frac{n R C}{R C} \sqrt{\frac{1}{n} + \frac{L}{m n}} = \sqrt{n \left( 1 + \frac{L}{m} \right)}$$

$$\boxed{Q = \sqrt{n \left( 1 + \frac{L}{m} \right)}} \quad \boxed{\omega_0 = \frac{L}{R C} \sqrt{\frac{L}{n} \left( 1 + \frac{L}{m} \right)}}$$

$\text{Q}_2 = ?$

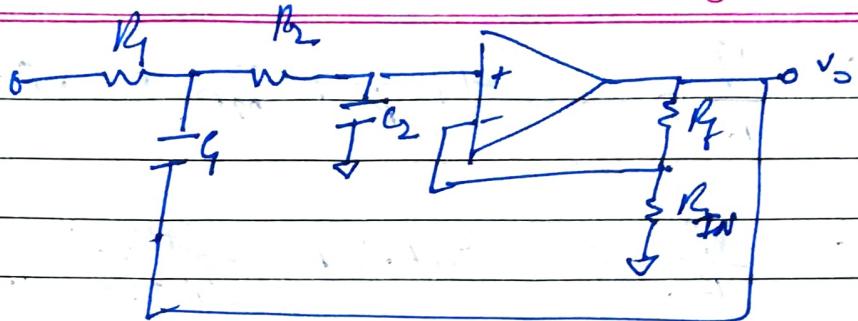

In equal component design,

$$R_1 = R_2, C_1 = C_2, Q = \frac{L}{2\pi k}, \text{ and } \omega_0 = \frac{1}{\sqrt{LC}}$$

known,

$$Q = 5, f_0 = 10 \text{ kHz}$$

$$\omega_0 = 2\pi f_0 = 2\pi \times 10 \times 10^3 \text{ rad/s}$$

$$\frac{L}{4\pi} = 2\pi \times 10 \times 10^3 \text{ rad/s.}$$

let us assume,  $R_1 = 1k\Omega$

$$Q = \frac{L}{2\pi \times 10 \times 10^3} F \approx 15 \text{ or } 15 \text{ nF}$$

$$[R_1 = R_2 = 1k\Omega], [Q = C_2 = 15 \text{ nF}]$$

$$Q = 5$$

$$\frac{L}{8\pi} \therefore 5 \Rightarrow 1 + \frac{R_F}{R_{IN}} = 2.8$$

$$\therefore [k = 2.8]$$

$$\therefore \frac{R_F}{R_{IN}} = 1.8$$

Taking  $R_{IN} = 1k\Omega$

$$R_F = 108 k\Omega$$

Gain in RRC low pass filter,

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{k}{s^2(4C_2R_1R_2) + 8(C_2R_1 + C_2R_2 + R_1R_2 - kC_1R_1) + 1}$$

$$DC \text{ gain} = \left| H(s) \right|_{s=0}$$

$$= |k| = 208$$

## # Lecture-24


Q1 Given,

$$\Delta_{max} = 0.5 \text{ dB}$$

$$f_p = 1 \text{ MHz}$$

$$f_s = 2 \text{ MHz}$$

Order of filter  $N \leq 5$

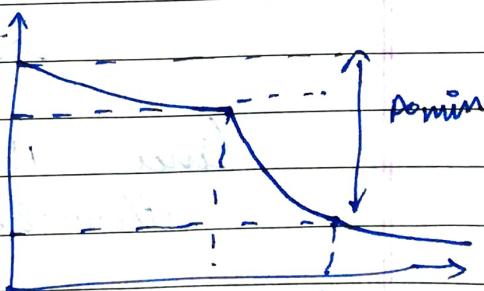

$$f_p = 1 \text{ MHz} = \frac{f_s}{2} \text{ MHz}$$

$N^{\text{th}}$ -Order Butterworth approximation function,

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \epsilon^2 \left(\frac{\omega}{\omega_p}\right)^{2N}}}$$

Pasband Attenuation  $A_{\max} = 10 \log(1 + \epsilon^2)^{\frac{1}{2}}$  dB

$$10 \log(1 + \epsilon^2)^{\frac{1}{2}} = 0.5$$

$$\Rightarrow \epsilon^2 = \sqrt{10^{0.05} - 1}$$

$$\Rightarrow \epsilon = \sqrt{10^{0.05} - 1} \approx 0.349$$

Stopband attenuation  $A_{\min} =$

$$10 \log \left[ 1 + \epsilon^2 \left( \frac{\omega_s}{\omega_p} \right)^{2N} \right] \text{dB} =$$

$$= 10 \log \left[ 1 + 0.349^2 \left( \frac{\omega_s}{\omega_p} \right)^{2N} \right] \text{dB}$$

Since  $N \leq 5$ , the greatest stopband attenuation will occur for  $N=5$ ,

Greatest Stopband Attenuation =

$$10 \log \left[ 1 + 0.349^2 \times 2^{10} \right] \text{dB} = \cancel{20.99 \text{ dB}}$$

$$= 20.99 \text{ dB}$$

$$\Omega_{20} = A_{max} = 25 \text{ dB.}$$

$$B = 5 \text{ MHz}$$

$$f_p = 2 \text{ MHz}$$

Order of filter  $N \leq 5$ .

At stop-band,  $\omega = \omega_s$ .

$$10 \log \left[ 1 + \xi^2 \cosh^2 \left[ N \cosh^{-1} \left( \frac{\omega_s}{\omega_p} \right) \right] \right] = 25 \text{ dB.}$$

As  $N$  increases, the value of  $\xi$  decreases.  
We also know

$$A_{max} = 10 \log (1 + \xi^2)$$

To achieve maximum ripple,  $\xi$  must be minimum & that occurs when  $N=5$ .

So, order of filter = 5


$$10 \log \left[ 1 + \xi^2 \cosh^2 \left[ 5 \cosh^{-1} (2.5) \right] \right] = 2.5$$

$$\Rightarrow \xi^2 \cosh^2 (7.8239) = 10^{2.5} - 1$$

$$\Rightarrow \boxed{\xi = 0.014}$$

$$\begin{aligned} \text{Maximum ripple} &= 10 \log (1 + \xi^2) \\ &= 8.5113 \times 10^{-4} \text{ dB.} \end{aligned}$$

$\omega_3 =$

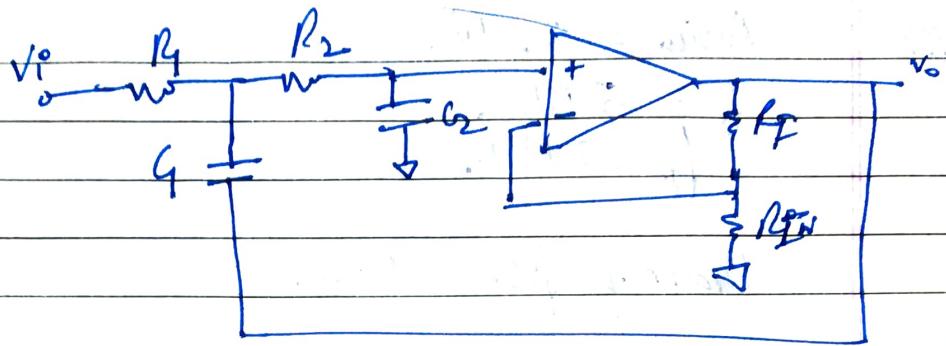

$$\frac{V_o(s)}{V_i(s)} = \frac{k}{s^2 R_2 C_2 C_1 + s [C_2 R_1 + C_2 R_2 + C_1 R_2 - k C_1 R_1] + 1}$$

low frequency gain = 2

$$\lim_{s \rightarrow 0} \frac{V_o(s)}{V_i(s)} = [k = 2] \quad (i)$$

$$\Rightarrow 1 + \frac{R_F}{R_{IN}} = 2$$

$$\Rightarrow R_F = R_{IN}$$

$$\text{Taking } R_{IN} = 1k\Omega$$

$$R_F = 1k\Omega$$

a) In equal component choices.

$$\alpha = \frac{1}{3-k} = 1.5$$

$$\Rightarrow k = 7/3$$

But from the relation (i),  $k=2$ ,

So, we cannot consider this design.

b) Taking equal resistance design,  
 $R_1 = R_2, G_1 \neq G_2$ .

$$\alpha = \frac{L}{\sqrt{\frac{G_2 R_1}{G_1 R_2}} + \sqrt{\frac{G_2 R_2}{G_1 R_1}} + \sqrt{\frac{G_1 R_1}{R_2 G_2}}} (L-k)$$

Given,

$$\alpha = \frac{3}{2}, k = 2, G_1 = R_2, G_2 \neq R_1$$

$$\frac{3}{2} = \frac{L}{2\sqrt{\frac{G_2}{G_1}} - \sqrt{\frac{G_1}{G_2}}}$$

$$2\sqrt{\frac{C_2}{4}} - \sqrt{\frac{9}{C_2}} = \frac{2}{3}$$

$$\Rightarrow \text{Taking } \frac{C_2}{C_1} = n$$

$$\Rightarrow 2\sqrt{n} - \frac{1}{\sqrt{n}} = \frac{2}{3}$$

Squaring both sides,

$$4n + \frac{1}{n} - 4 = \frac{4}{9}$$

$$\Rightarrow 4n^2 + 1 - 4n = \frac{4n}{9}$$

$$\Rightarrow 4n^2 - \frac{40n}{9} + 1 = 0.$$

$$n = 0.7977, 0.3134$$

When  $\lambda = 0.7977$

$$\frac{L_2}{G} = 0.7977$$

Taking  $[G = 50 \mu\text{F}]$ ,  $L_2 =$

$$L_2 = 39.885 \mu\text{H}$$

$$[L_2 = 39.885 \mu\text{H}]$$

$$\omega_0 = \frac{1}{\sqrt{R_2 G L_2}} = 2\pi \times 50 \text{ MHz.}$$

$$\frac{L}{\sqrt{R_2 G^2 \times 0.7977}} = 2\pi \times 50 \times 10^6$$

$$\Rightarrow \frac{L}{R_2 G \sqrt{0.7977}} = 2\pi \times 50 \times 10^6.$$

$$\Rightarrow R_2 = \frac{L}{50 \times 10^6 \times \sqrt{0.7977} \times 100\pi \times 10^6}$$

$$= 71.2787 \Omega$$

$$[R_1 = R_2 = 71.2787 \Omega]$$

When  $n = 0.2134$

$$\frac{C_2}{4} = 0.2134$$

Taking  $\boxed{G = 50 \mu F}$

$$\boxed{C_2 = 15.67 \mu F}$$

$$\frac{L}{R G \cdot 0.2134} = 2\pi \times 50 \text{ MHz}$$

$$21 \quad R_f = \frac{1}{50 \times 10^{-12} \times \sqrt{0.2134} \times 2\pi \times 10^6} = 113.71837 \Omega$$

$$\therefore \boxed{R_f = R_2 = 113.7184 \Omega}$$