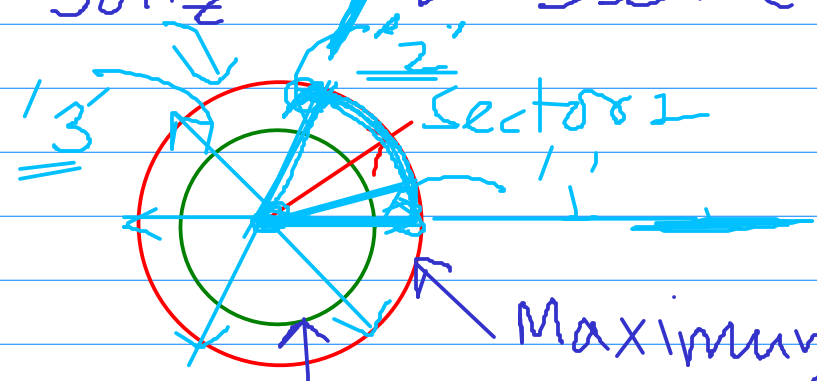


415V (AC)  
↓

560V → 50Hz → 395V (RMS) Line to Line



Maximum possible value of output voltage at 50Hz

Space vector for 20Hz

$$\Rightarrow \frac{560 \times \sqrt{3}}{2} = 485V / 50Hz$$


$$= \frac{2}{5} \times 485V$$

$$= 194V, 20Hz$$

100ms → 50ms →  $\Delta\theta|_{50Hz} = 1.8^\circ$

100ms → 500 steps →  $360^\circ$  1 cycle

$$\Delta\theta|_{20Hz} = \frac{360}{500} = 0.72^\circ$$

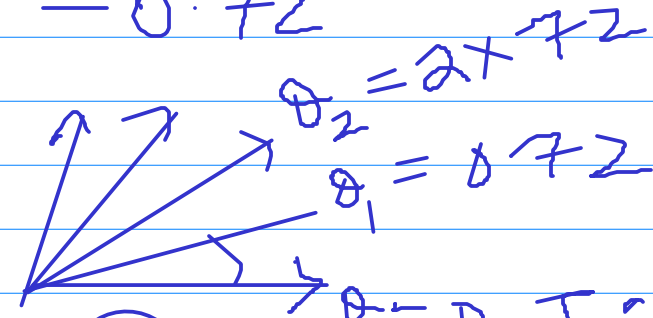

$\frac{194V}{\sqrt{3}} \angle 0^\circ \rightarrow T_1, T_2, T_0$   $T_1$ : Active vector 1

$\frac{194V}{\sqrt{3}} \angle -72^\circ \rightarrow T_1, T_2, T_0$   $T_2$ : Active vector 2  
 $T_0$ : Null vector


Velocity triangle diagram showing the relationship between velocities  $T_1$ ,  $T_2$ , and  $V_2$ . The angle between  $T_1$  and  $T_2$  is  $30^\circ$ . The horizontal vector  $T_1$  is labeled  $(T_1 - T_2) V_1$ .


$$\underline{\underline{T_L = 100 \text{ hSec}}}$$

$$V_0 \rightarrow (T_1 - T_2) \rightarrow T_1$$

$$= 19.88 \text{ h Lek}$$
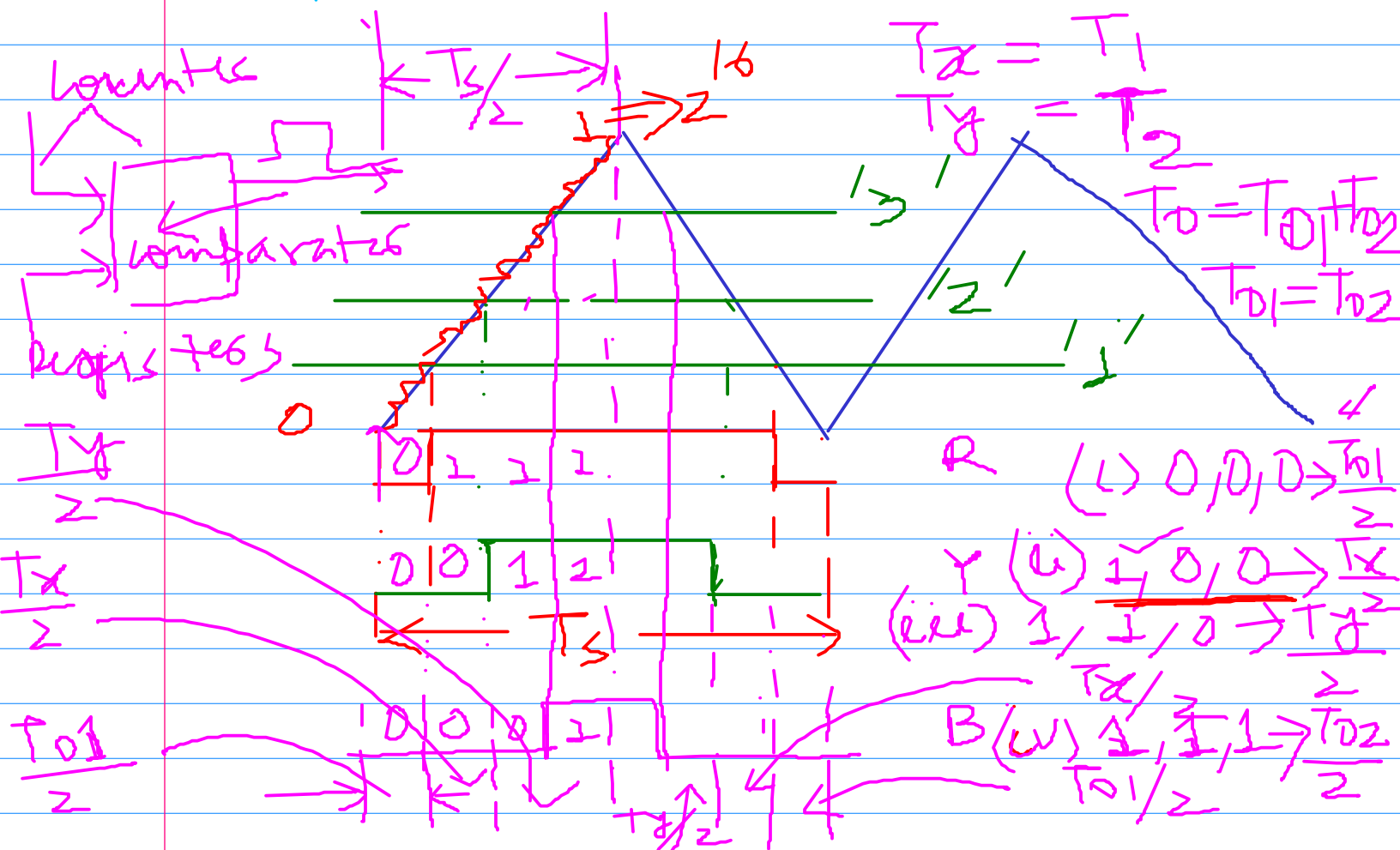
$$T_s - T_1 - T_2 = 100 - 40.12 = \underline{\underline{59.87 \text{ K}}}$$



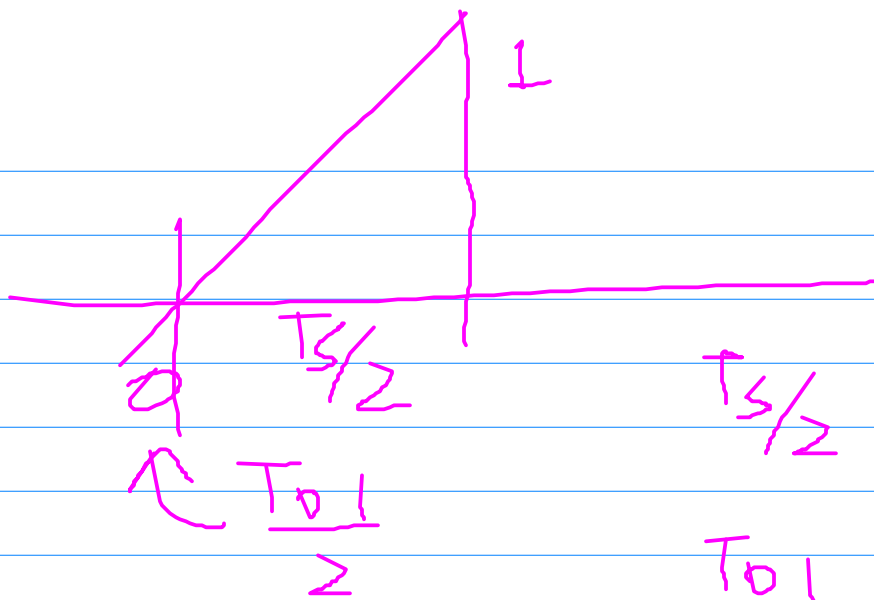

$$T_s/2 \rightarrow 1$$

$$\frac{T_{01}}{2} \rightarrow \frac{2}{T_s} \times \frac{T_{01}}{2}$$

'1'  $\rightarrow$  First comparison value  $\Rightarrow \frac{T_{01}}{T_s}$

$$T_{01} = \frac{T_0}{2}$$

$$T_s \Rightarrow 2^{16}$$

'2'  $\rightarrow \frac{T_{01}}{2} + \frac{T_1}{2} \rightarrow$

$$\frac{T_{01} + T_1}{T_s}$$

'3'  $\rightarrow \frac{T_{01}}{2} + \frac{T_1}{2} + \frac{T_2}{2} \rightarrow$

$$\frac{T_{01} + T_1 + T_2}{T_s}$$

Comparator - Counter Unit  
(DSP)

Load comparator registers with  
'1', '2', '3' values  $\rightarrow$  Switching  
pulses of the three phase  
Inverters