

EE60032: Analog Signal Processing



Dr. Ashis Maity

Assistant Professor

Email: ashis@ee.iitkgp.ac.in

Department of Electrical Engineering

Indian Institute of Technology, Kharagpur


West Bengal, India

Module-4: Phase Locked Loop and Oscillators

Phase locked Loop (PLL)

What is PLL?

 PLL is a negative feedback system that compares the output phase with input reference phase. i.e., $\Phi_{out} = \Phi_{in}$.



What is the purpose?

If phases are same, frequencies are same.

$$f = \frac{d\Phi}{dt} ; \quad \frac{d\Phi_{out}}{dt} = \frac{d\Phi_{in}}{dt} \Rightarrow f_{out} = f_{in}.$$


Why do we need PLL?

- An oscillator with a stable frequency is difficult to get.
- Crystal oscillators are costly, but offers a stable frequency. at low range.
- If $f_{out} \neq f_{in}$ and/or $f_{out1}, f_{out2}, f_{out3} \dots \neq f_{in}$, then you need a PLL.


Applications:-

- Frequency synthesis
- clock recovery


Block Diagram:-

 

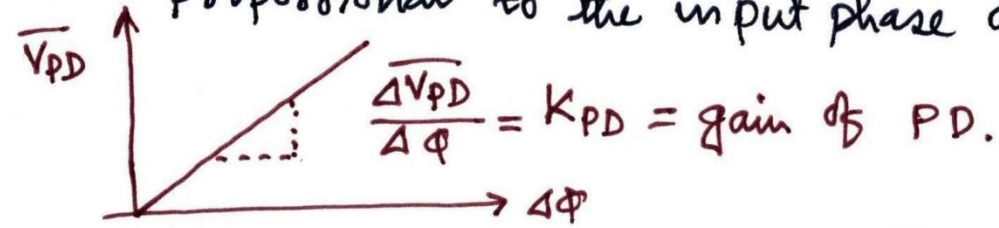● Phase detector :- A phase detector is a ckt whose average output voltage $\overline{V_{PD}}$ is linearly proportional to the input phase difference ($\Delta\phi$).





Implementation :-

 

$$V_{PD} = v_1 \oplus v_2$$

$$= v_1 \overline{v_2} + v_2 \overline{v_1}$$

v_1	v_2	v_{PD}
0	0	0
0	1	1
1	0	1
1	1	0

  

Static characteristic of PD.

Generalised expression:-

1) VCO:-

$$\omega_{out} = \omega_0 + K_{vco} V_{cont}$$

ω_0 = free running freq.
when $V_{cont} = 0$.

K_{vco} = Gain of the VCO.

2) PD:-

$$\overline{V_{PD}} = V_{cont} = K_{PD} \Delta \phi_0$$

K_{PD} = Gain of the PD.

• If $\omega_{in} = \omega_1$, then $\omega_{out} = \omega_1$
under locked condition.


$$\omega_1 = \omega_0 + K_{vco} \cdot V_1$$

$$\text{or, } V_1 = \frac{\omega_1 - \omega_0}{K_{vco}}$$


$$\text{and } V_1 = K_{PD} \Delta \phi_0$$

$$\text{So, } \boxed{\Delta \phi_0 = \frac{\omega_1 - \omega_0}{K_{vco} K_{PD}}}$$

PLL waveforms under Locked Condition

 

(a)

 

(b)

(a) Waveforms in a PLL in locked condition; (b) calculation of phase error.

Observations:-

- 1) To minimise phase error, K_{vco} , K_{PD} must be high.
- 2) Phase error can't be zero, for $\omega_1 \neq \omega_0$.
- 3) Phase error varies with input frequency.

EE60032: Analog Signal Processing



Dr. Ashis Maity

Assistant Professor

Email: ashis@ee.iitkgp.ac.in


Department of Electrical Engineering

Indian Institute of Technology, Kharagpur

West Bengal, India

Process of Locking/Capturing

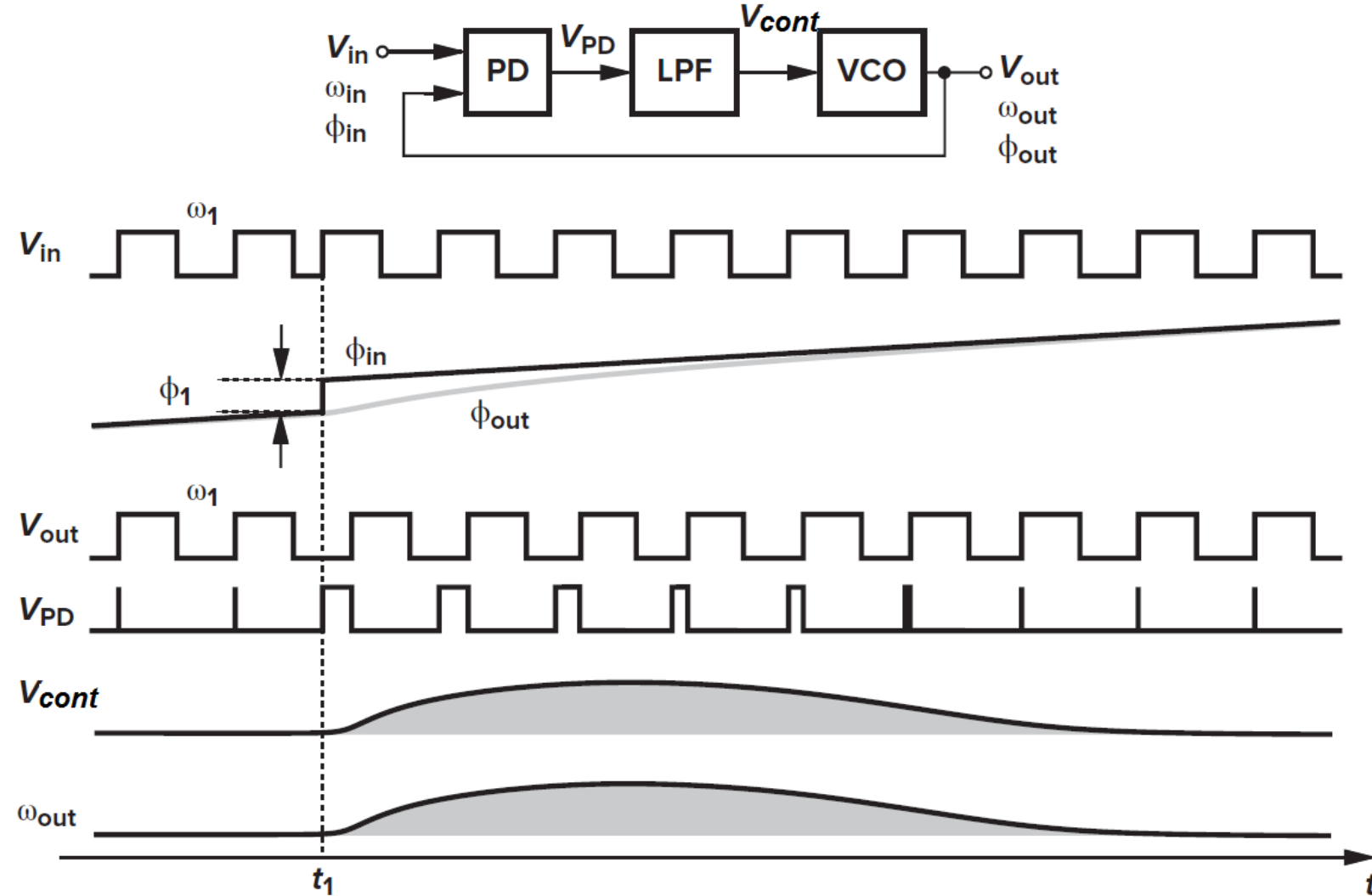
1. When a phase step is given, the phase detector accumulates the phase difference and changes V_{control}
2. VCO changes the frequency to vary phase. $\varphi = \int \omega_{\text{out}} dt$
3. Once phase error reduces, the input frequency gets equal with output frequency and the loop becomes locked again.



Response of a PLL to a phase step.

Process of Locking/capturing

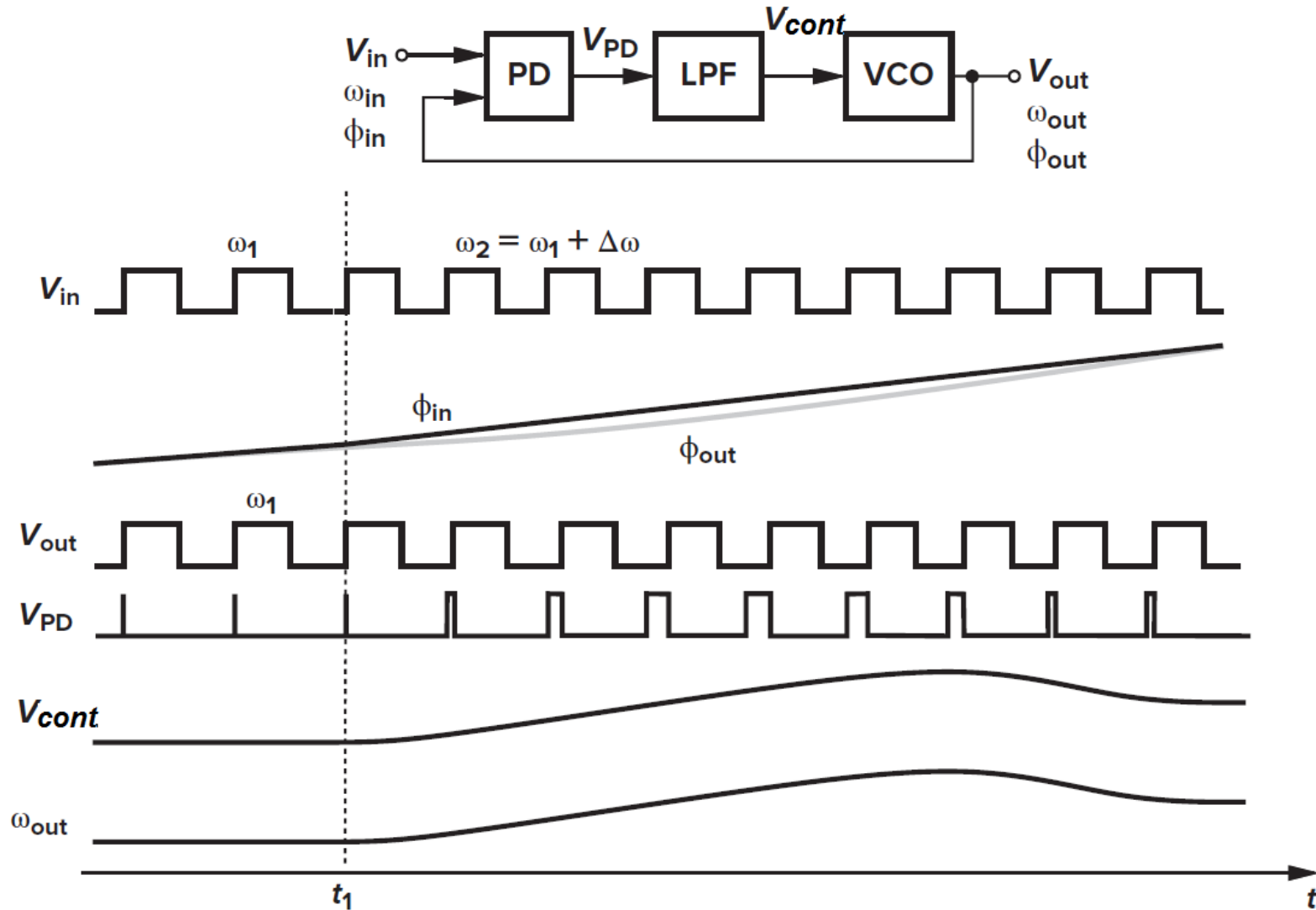1. When a small frequency step is given, the phase detector accumulates the phase difference and changes V_{control}
2. VCO changes the frequency to vary phase. $\varphi = \int \omega_{\text{out}} dt$
3. Once frequency error reduces, the PD produces narrower pulse and V_{cont} settles to a new value to track the new input frequency gets equal with output frequency and the loop becomes locked again.




Response of a PLL to a small frequency step.

Dynamics of PLL


Negative feedback system compares ϕ_{out} with ϕ_{in} .

$$H(s)|_{open} = \frac{\Phi_{out}}{\Phi_{in}}(s)|_{open}$$
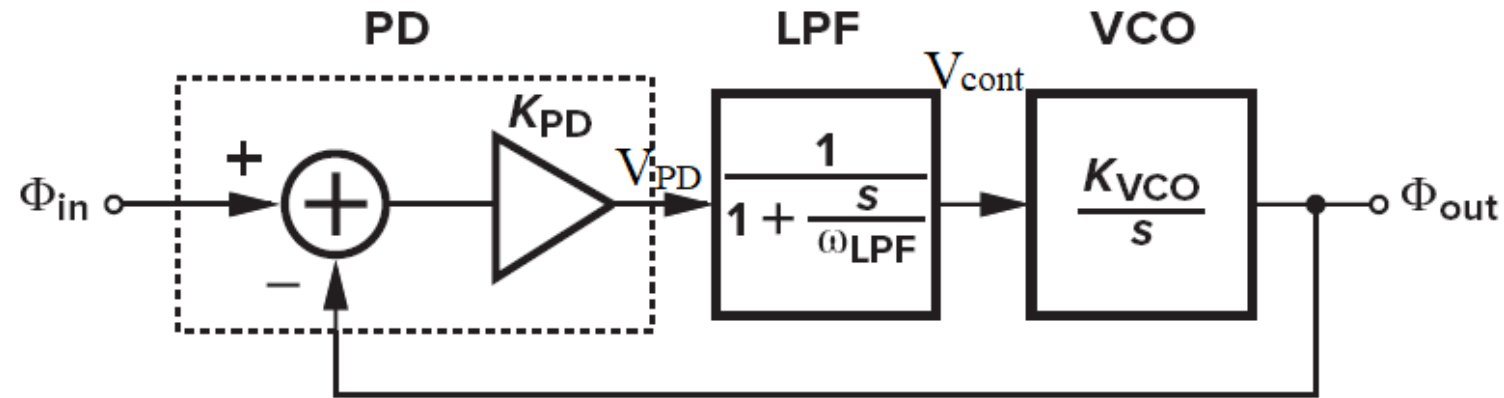
$$= K_{PD} \cdot \frac{1}{1 + \frac{s}{\omega_{LPF}}} \cdot \frac{K_{VCO}}{s}$$



Linear model of type I PLL.

 

Bode plots of type I PLL.

- To minimise the phase error, K_{PD} and K_{VCO} should be high, but stability degrades.
- Pushing ω_{LPF} to high frequency may improve stability; however, it introduces more ripple in V_{cont} and introduces jitter in ω_{OUT} .
- Since the loop gain contains one pole at origin, it is called Type-1 PLL.

$$\omega = \frac{d\phi}{dt} \text{ and } \phi = \int \omega dt$$

$$\Delta\phi = \frac{\Delta\omega}{s}$$

$$K_{VCO} = \frac{\Delta\omega_{out}}{\Delta V_{cont}} = \frac{\Delta\phi_{out} \cdot s}{\Delta V_{cont}}$$

$$\frac{\Delta\phi_{out}}{\Delta V_{cont}} = \frac{K_{VCO}}{s}$$

Dynamics of PLL

$$H(s)|_{\text{closed}} = \frac{K_{PD}K_{VCO}}{\frac{s^2}{\omega_{LPF}} + s + K_{PD}K_{VCO}}$$

$$= \frac{K_{PD}K_{VCO}\omega_{LPF}}{s^2 + s\omega_{LPF} + K_{PD}K_{VCO}\omega_{LPF}}$$


$$H(s) = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

$$\omega_n = \sqrt{\omega_{LPF}K_{PD}K_{VCO}}$$

$$\zeta = \frac{1}{2}\sqrt{\frac{\omega_{LPF}}{K_{PD}K_{VCO}}}$$

$$s_{1,2} = -\zeta\omega_n \pm \sqrt{(\zeta^2 - 1)\omega_n^2}$$
 
$$= (-\zeta \pm \sqrt{\zeta^2 - 1})\omega_n$$



Linear model of type I PLL.

1. If ω_{in} changes very slowly, $s \rightarrow 0$, then ω_{out} tracks ω_{in} .
2. If $\zeta > 1$. poles are real and overdamped response
3. If $\zeta < 1$. poles are complex and underdamped response
4. If $\zeta = 1$. critically damped response

Dynamics of PLL


$$H(s) = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

$$\omega_n = \sqrt{\omega_{LPF} K_{PD} K_{VCO}}$$

$$\zeta = \frac{1}{2} \sqrt{\frac{\omega_{LPF}}{K_{PD} K_{VCO}}}$$

$$\zeta \omega_n = \frac{1}{2} \omega_{LPF}$$
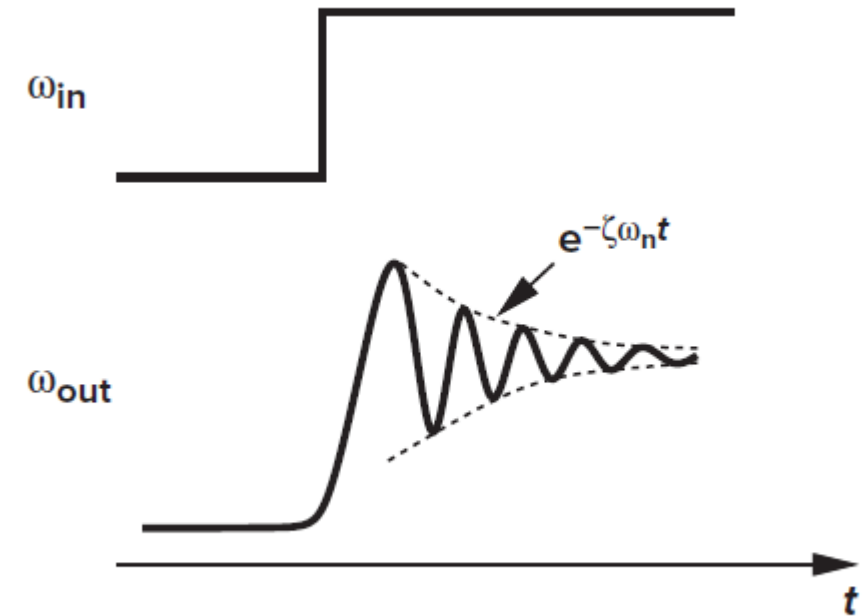
$$s_{1,2} = -\zeta\omega_n \pm \sqrt{(\zeta^2 - 1)\omega_n^2}$$
$$= (-\zeta \pm \sqrt{\zeta^2 - 1})\omega_n$$




Underdamped response of PLL to a frequency step.

1. Settling speed of PLL is an important parameter. Maximizing $\zeta\omega_n$ decreases settling time.
2. To maximize $\zeta\omega_n$, ω_{LPF} has to be increased and it increases ripple of V_{cont} , ω_{OUT} drifts.
3. If $\zeta\omega_n$ is decreased, PLL takes longer time to settle, a lower value of ω_{LPF} reduces ripple in V_{cont} , but stability decreases.
4. Trade-offs exist between settling time, ripple in V_{cont} and stability.

Lock-range and capture-range of PLL

 1. **Lock range:** When PLL is in locked condition, the lock-range represents the range of frequencies for which the PLL maintains the locked condition.
2. **Capture range:** When PLL is unlocked condition, the capture-range is the range of input frequencies within which an initially unlocked loop will get locked with an input frequency.
3. **Capture range is smaller than lock-range.**



Lock and capture processes of PLL

EE60032: Analog Signal Processing



Dr. Ashis Maity

Assistant Professor

Email: ashis@ee.iitkgp.ac.in


Department of Electrical Engineering

Indian Institute of Technology, Kharagpur

West Bengal, India

Oscillator

 An oscillator is a BADLY designed negative feedback amplifier.




$$\left. \frac{V_{out}(s)}{V_{in}(s)} \right|_{\text{Closed}} = \frac{H(s)}{1 + \beta(s)H(s)}$$

If for $s = j\omega_{osc}$,

$$\beta(j\omega_{osc})H(j\omega_{osc}) = -1,$$

 Then $\frac{V_{out}(s)}{V_{in}(s)} = \infty.$






To get a sustained oscillation, the loop gain should be slightly greater than unity

A negative feedback system will oscillate, if $|H(j\omega_{osc})\beta(j\omega_{osc})| \geq 1$.
 $\angle H(j\omega_{osc})\beta(j\omega_{osc}) = 180^\circ$


This is called as "Barkhausen Criteria".

   - These conditions are necessary but not sufficient.
- To get a sustained oscillation across PVT variation, the loop gain should be at least twice or thrice.
- Different views of oscillatory feedback system:-



● Wein Bridge Oscillator:- produce a sinusoidal waveform.

feedback network: non-inverting amp.

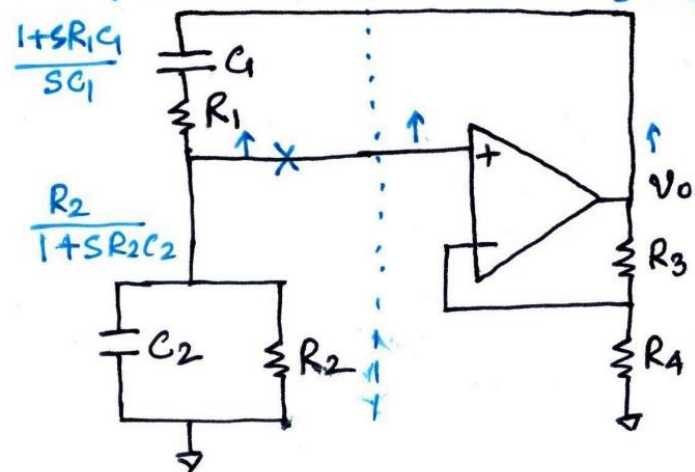

$$\text{Loop gain} = \left(1 + \frac{R_3}{R_4}\right) \frac{R_2 / (1 + sC_2 R_2)}{\frac{R_2}{1 + sC_2 R_2} + \frac{1 + sR_1 C_1}{sC_1}}$$

Assuming $R_1 = R_2 = R$, $C_1 = C_2 = C$.

$$= \left(1 + \frac{R_3}{R_4}\right) \frac{R / (1 + sRC)}{\frac{R}{1 + sRC} + \frac{1 + sRC}{sC}}$$

$$= \left(1 + \frac{R_3}{R_4}\right) \frac{1}{3 + sRC + \frac{1}{sRC}}$$

To get a sustained oscillation, the phase-shift across the loop should be 0° , or 360° .

$$sRC = -\frac{1}{sRC} \Rightarrow s^2 = -\frac{1}{RC} \Rightarrow \omega_{osc} = \frac{1}{RC} \Rightarrow \boxed{f_{osc} = \frac{1}{2\pi RC}}$$


To meet the gain criteria, $\left(1 + \frac{R_3}{R_4}\right) \frac{1}{3} = 1 \Rightarrow \boxed{R_3 = 2R_4}$

Note :- At very low frequency, the feedback loop is broken, not a positive feedback system.


- At ω_{osc} , it only becomes a positive feedback system.
- There is no input to the ckt. How do we get off?

Ring Oscillator :-

 Connect odd number of inverters in the ring.



Steady state response.

 

t_d is the delay of inverter.


Frequency of oscillation $f_{osc} = \frac{1}{6 t_d}$.

For N no. of inverters, $f_{osc} = \frac{1}{2N t_d}$ where $N = \text{odd no.}$


How we can develop VCO from this?

* If there is no noise, then
 $V_x = V_y = V_z = V_{trip}$.
no oscillation.

 * With noise, this state will be disturbed and oscillation will be growing.



Voltage Controlled Oscillator (VCO) :-

 


$$\omega_{out} = \omega_0 + K_{VCO} \cdot V_{cont}.$$

$$K_{VCO} = \frac{\omega_{out} - \omega_0}{V_{cont}}.$$

$(\omega_2 - \omega_0) \rightarrow$ linear tuning range.

Implementation of VCO :-

 A current-starved inverter delay is controlled by the bias current.



Inverter trip voltage = V_{trip} .

- 1) when V_o is charging from low-to-high, the next stage will trip from high-to-low, once the V_o reaches V_{trip} .


$$t_{PLH} = \frac{C_p \times V_{trip}}{I_{source}}$$

- 2) Similarly, when V_o is discharging from high-to-low, the next stage will trip from low-to-high, once V_o reaches to $(V_{DD} - V_{trip})$ from V_{DD} .

$$t_{PHL} = \frac{C_p \times (V_{DD} - V_{trip})}{I_{sink}}$$

If $I_{source} = I_{sink} = I_{bias}$, then $t_p = \frac{t_{PHL} + t_{PLH}}{2} = \frac{C_p V_{DD}}{2 I_{bias}}$

 If $I_{bias} = f(V_{control})$, then $t_p = f(V_{control})$



Frequency of oscillation
$$f_{osc} = \frac{1}{2N \cdot t_p} = \frac{I_{bias}}{N C_p V_{DD}}$$

I_{bias} can be generated from a voltage-to-current converter.

