

Pratyush Jainwal  
18EE35014

Q3:

The input current to the motor at rated conditions

$$= \frac{10 \times 10^3}{0.87} = 11.494 \times 10^3 \text{ W}$$

The supply current to the motor is

$$= \frac{11.494 \times 10^3}{240} \text{ A} = 47.89 \text{ A}$$

Neglecting the field copper loss the armature current

$$= 47.89 \text{ A}$$

The back EMF at the rated conditions is

$$= 240 - 47.89 \times 0.4 = 220.843 \text{ V}$$

(a) At  $\alpha = 0$ , the converter voltage is

$$V_a = \frac{2V_m}{\pi} \cos \alpha = \frac{2 \times \sqrt{2} \times 250}{\pi} \times \cos 0^\circ$$

$$= 225 \text{ V}$$

As the load torque is constant the armature current is same. Therefore the back EMF is

$$= 225 - 47.89 \times 0.4 = 205.844 \text{ V}$$

We know that

$$E_b = k \omega$$

$$\omega = \frac{400 \times 2\pi}{60} = 104.719 \text{ rad/s}$$

$$\therefore k = \frac{E_b}{\omega} = \frac{220.844}{104.719} = 2.11 \text{ V.s/rad.}$$

At  $\alpha = 0^\circ$

$$\text{Speed} = \frac{E_b}{k} = \frac{205.844}{2.11} = 97.649 \text{ rad/sec}$$

$$N = \frac{97.649}{2\pi} \times 60 = 932.479 \text{ RPM}$$

$$\text{Displacement Factor} = DF = \cos \phi = \cos 0^\circ = 1$$

$$\text{Power factor} = PF = \frac{2\sqrt{2}}{\pi} \cos \alpha = \frac{2\sqrt{2}}{\pi} \cos 0^\circ = 0.9$$

$$\text{Input} = 225 \times 47.89 = 10775.25 \text{ W}$$

Output varies linearly with speed

$$\therefore \text{output at } 932.479 \text{ RPM} = 10 \text{ kW (rated)} \times \frac{932.479}{1000} = 9.32479 \text{ kW}$$

$$\therefore \eta = \frac{O/P}{I/P} = \frac{9.32479}{10.77525} = 86.538\%$$

(b) At  $\alpha = 60^\circ$ , the converter voltage is.

$$V_a = \frac{2V_m}{\pi} \cos \alpha = \frac{252 \times 250}{\pi} \times \cos 60^\circ = 112.5 \text{ V}$$

As the load torque is constant, the armature current is same. Therefore the back EMF is.

$$= 112.5 - 47.89 \times 0.4 = 93.344 \text{ V}$$

We know that

$$E_b = k\omega$$

$$\omega = \frac{1000 \times 2\pi}{60} = 104.719 \text{ rad/s.}$$

$$\therefore k = \frac{E_b}{\omega} = \frac{220 \cdot 104 \cdot 93.344}{104.719} = 0.851 \text{ rad/s.}$$

At  $\alpha = 60^\circ$ .

$$\text{Speed} = \frac{E_b}{k} = \frac{93.344}{0.851} = 44.28 \text{ rad/s.}$$

$$N = \frac{44.28 \times 60}{2\pi} = 422.8 \text{ RPM}$$



$$\text{Displacement Factor} = \text{DF} = \cos\phi = \cos 60^\circ = 0.5.$$

$$\text{Power factor} = \frac{2\sqrt{2}}{\pi} \cos\alpha = \frac{2\sqrt{2}}{\pi} \times \frac{1}{2} = 0.45$$

$$\text{Input} = 1120.5 \times 47.89 = 5.387 \text{ kW}$$

$$\text{Output at } 422.8 \text{ rpm} = 1000 \text{ rpm} \times \frac{422.8}{1000} = 4.2227 \text{ kW}$$
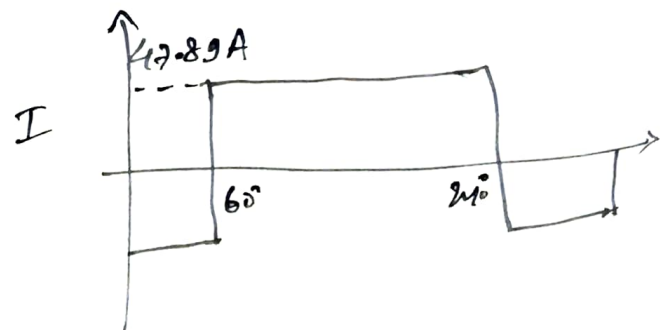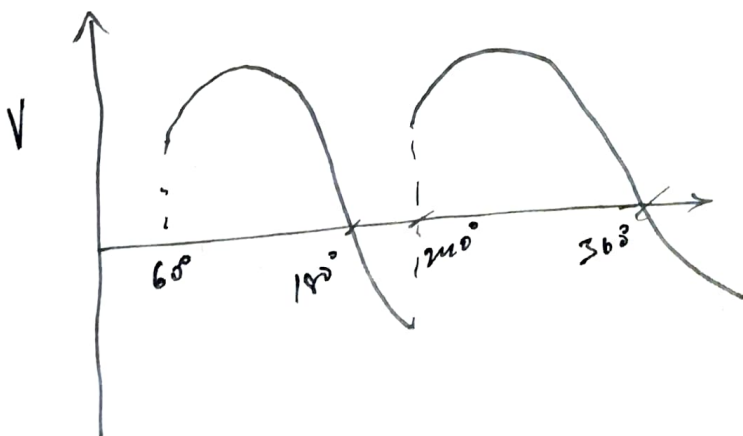
$$\therefore \eta = \frac{\text{O/P}}{\text{i/p}} = \frac{4.2227}{5.387} = 78.338\%$$



Q6:

At rated operation, (980 RPM),

$$E_1 = 210 - 0.04 \times 100 \text{ V} = 206 \text{ V}$$

At 1000 rpm,

$$E_2 = \frac{1000}{980} \times 206 \text{ V} = 210.204 \text{ V}$$

(a) For plugging operation,

$$R_B + R_A = \frac{E + V}{I_a} = \frac{210.204 + 210}{2 \times 100} = 2.10102 \Omega$$

$$\Rightarrow R_B = (2.10102 - 0.04) \Omega = 2.06 \Omega$$

(b) ~~when~~ the braking torque ~~is~~ <sup>at</sup> ~~factor~~ <sup>1000 RPM,</sup>  
In steady state,  $P_m = P_e$

$$T = \frac{E_2 \times I_a}{\omega_m} = \frac{210.204 \times 200}{1000 \times \frac{2\pi}{60}} = 401.46 \text{ N-m}$$

At zero speed,  $E = 0$

$$\frac{V}{I_a} = \frac{V}{R_B + R_A} = \frac{210}{2.10102} \text{ A} = 99.95 \text{ A}$$

As  $T \propto I_a$

$$T = 401.46 \times \frac{99.95}{200} = 200.629 \text{ N-m.}$$

Q2.

We know,  $T = \frac{J \frac{d\omega}{dt}}$

$$T \frac{d\omega}{dt} = 7 - 4 = (T_m - T_c)$$

$$T \frac{d\omega}{dt} = 3 \text{ Nm}$$

$$T d\omega = 3 dt$$

$$T \int_0^{\frac{2\pi \times 1570}{60}} d\omega = \int_0^{150} 3 dt$$

$$\Rightarrow T \times \frac{2\pi \times 1570}{60} = 2 \times 150$$

$$\therefore T = \frac{2 \times 150}{1570 \times \frac{2\pi}{60}} = 1.8247$$

In second case,

$$T = \frac{J \frac{d\omega}{dt}}{T_m - T_c} = \frac{3}{(0.6 \omega + 15) - (5 + 0.2 \omega)}$$

$$= 10 - 0.1 \omega$$

At stand still,

$$T = 0 \Rightarrow \omega = 100 \text{ rad/s}$$

$$T = \frac{J \frac{d\omega}{dt}}{10 - 0.1 \omega}$$

$$10 - 0.1 \omega = T \cdot \frac{d\omega}{dt}$$

95% of  $\omega = 95 \text{ rad/s}$ .

Pratyush Tamsol  
JEE 2014,

Page 6

$$\frac{1}{J} \int_0^t dt = \int_0^{95} \frac{d\omega}{10 - 0.1\omega}$$

$$\Rightarrow t = \frac{J}{-0.1} \log(10 - 0.1\omega) \Big|_0^{95}$$

$$\Rightarrow t = -10 \times 1.8247 \times \log \frac{0.5}{10} \text{ s}$$

$$= 23.739 \text{ s} \approx 23.74 \text{ s}.$$

Q10

$$\omega = \omega_{no} - \frac{R_a}{k_b^2} T_m$$

$$\frac{3}{100} = \frac{\frac{R_a}{k_b^2} \times T_m \times \frac{1}{2}}{\omega_{no}}$$

$$\omega_m = \frac{V_a}{R_a}$$

$$0.03 = \frac{k_a \times I_a \times 0.5}{V_a}$$

$$0.03 = \frac{I_a R_a}{240} \propto 0.5$$

$$I_a R_a = 12.6 \text{ V}$$

$$I_a (\text{starting}) = \frac{V_a (\text{starting})}{R_a}$$

$$42 \times R_a = 12.6$$

$$R_a = \frac{12.6}{42} \Omega = 0.3 \Omega$$




(a)  $I_a(\text{starting}) = \frac{210}{0.3} \text{ A} = 700 \text{ A}$

(b)  $T \propto I^2$   
 $I' = 2 \times \frac{42}{700} \text{ A} = 84 \text{ A}$

$V_a(\text{starting}) = I_a R_a = 84 \times 0.3 \text{ V}$   
 $= \boxed{25.2 \text{ V}}$

(c)  $V_a = 0$

$\omega = \frac{-T_m \times R_a}{k_b^2}$

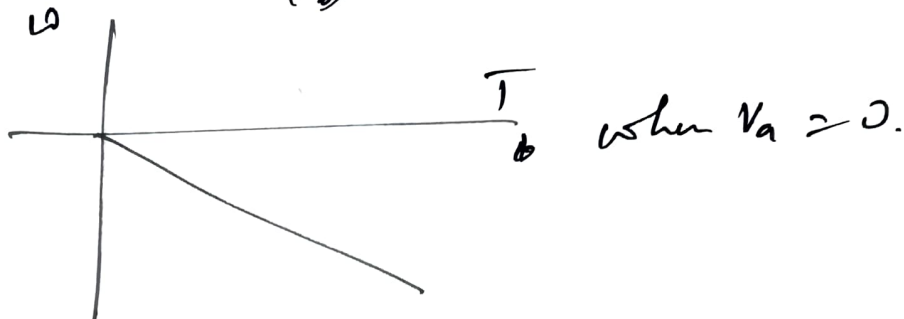

(d)  $\omega = \frac{90 \times 2\pi}{60} = 3 \text{ rad/s}$



$3 T = \frac{-T_m \times R_a}{k_b^2}$

$T_m = \frac{-3 \pi \times (k_b)^2}{R_a}$

$T_m(\text{rated}) = k_b \alpha I_a$

$\omega = \frac{210}{k_b} - \frac{T_a R_a}{k_b} \Rightarrow \omega = \frac{1500 \times 2\pi}{60}$   
 $= 50\pi$

$\omega \times k_b = (210 - 1206) \text{ V}$

$$b_b = 1.2566$$

$$\frac{T_m}{T_{\text{rated}}} = \frac{3\pi \alpha b_b}{I_a R_a}$$

$$= \frac{3\pi \times 1.2566}{12.6}$$

$$= 0.9299 \approx \text{93.99\%}$$