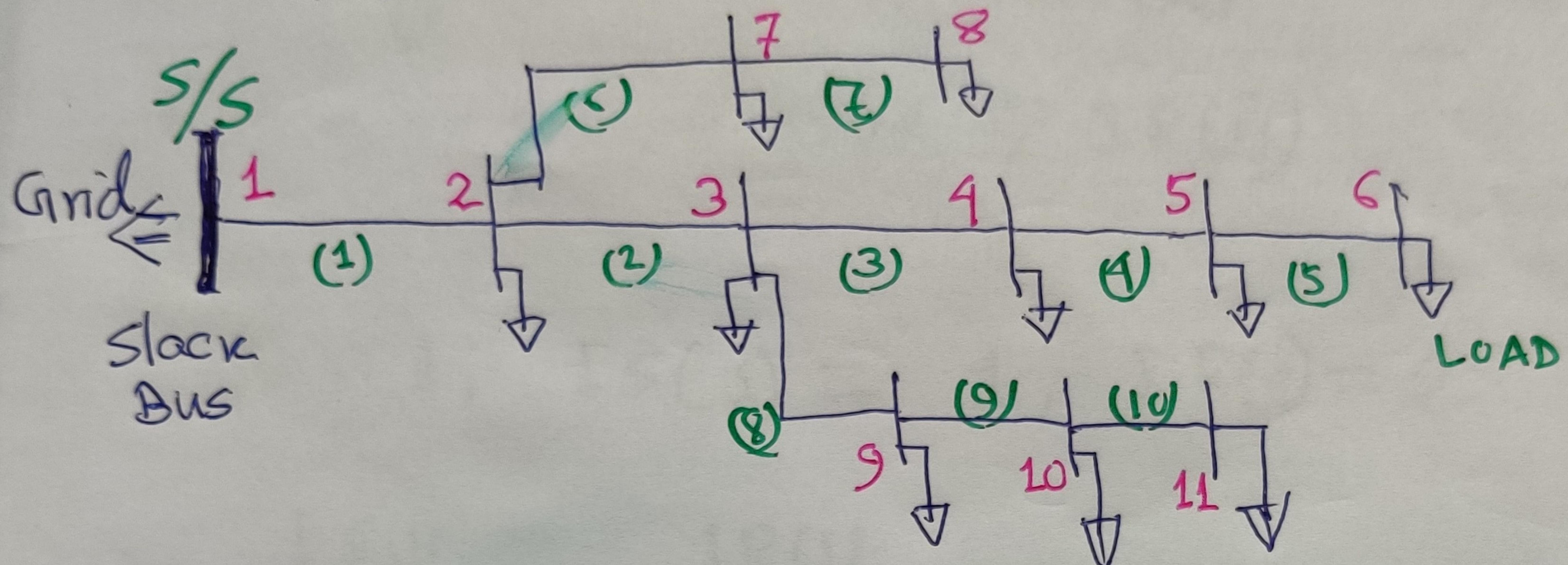


Radial Distribution Power Flow

A)

Identification of Nodes Beyond Each Branch



<u>Branch No:</u> (i,j)	<u>Sending end node</u> , $IS(i,j)$	<u>Receiving end node</u> , $IR(i,j)$
1	1	2
2	2	3
3	3	4
4	4	5
5	5	6
6	2	7
7	7	8
8	3	9
9	9	10
10	10	11

Consider Branch-1

Page-2

Branch Number $\Rightarrow jj$

Sending end node $\Rightarrow IS(jj)$

Receiving end node $\Rightarrow IR(jj)$

When

$$jj = 1, IS(1) = 1, IR(1) = 2$$

<u>IS(U)</u>	<u>IR(U)</u>
1	2 ✓
2	3 ✓
2	7 ✓
3	4 ✓
3	9 ✓
7	8 ✓
4	5 ✓
9	10 ✓
5	6 ✓
10	11 ✓

Beyond Branch 1, Total number of nodes = 10

2, 3, 7, 4, 9, 8, 5, 10, 6, 11

Page-2

Consider Branch - 2

$$jj = 2$$

$$IS(2) = 2, \quad IR(2) = 3$$

IS(2)

2

3

3

4

9

5

10

IR(2)

3 ✓

4 ✓

9 ✓

5 ✓

10 ✓

6 ✓

11

Beyond Branch 2, Total number of nodes = 6

3, 4, 9, 5, 10, 6, 11

Consider Branch -3

$$j_j = 3, \text{IS}(3) = 3, \text{IR}(3) = 4$$

IS(3)

3

4

5

IR(3)

4 ✓

5 ✓

6 ✓

Beyond Branch 3, Total number of nodes = 3

4, 5, 6

Consider Branch -4

$$\textcircled{4} \quad j_j = 4, \text{IS}(4) = 4, \text{IR}(4) = 5$$

IS(4)

4

5

IR(4)

5 ✓

6 ✓

Beyond Branch 4 , Total number of ~~nodes~~ nodes = 2

5, 6

Consider Branch - 5

$$j_j \geq 5, IS(5) = 5, IR(5) = 6$$

IS(5)

5

IR(5)

6 ✓

~~Total number of nodes~~

Beyond Branch 5, Total number of
nodes = 1

6

Consider Branch - 6

$$j_j \geq 6, IS(6) = 2, IR(6) = 7$$

IS(6)

2

IR(6)

7 ✓

7

8 ✓

Beyond Branch 6, Total number of
nodes = 2

7, 8

Consider Branch - F

$$jj = 7, \quad IS(F) = 7, \quad IR(F) = 8$$

Beyond Branch F, Total number of
node = 1

8,

Consider Branch - G

$$jj = 8, \quad IS(G) = 3, \quad IR(G) = 9$$

IS(G)
3
9
10

IR(G)
9
10 ✓
11 ✓

Beyond Branch G, Total number of
nodes = 3

9, 10, 11

Consider Branch 9

$$jj = 9, \quad IS(9) = 9, \quad IR(9) = 10$$

IS(9)
9
10

IR(9)
10 ✓
11 ✓

Beyond Branch 9, Total number of nodes = 2

10, 11

Consider Branch 10

$$jj = 10, \quad IS(10) = 10, \quad IR(10) = 11$$

IS(10)
10


IR(10)
11 ✓

~~Total~~ Beyond Branch 10, Total number of node = 1

11.

<u>Branch</u>	<u>Other option</u>
1	2, 3, 4, 5, 6, 7, 8, 9, 10, 11
2	3, 4, 5, 6, 9, 10, 11
3	4, 5, 6
4	5, 6
5	6
6	7, 8
7	8
8	9, 10, 11
9	10, 11
10	11

[Page-8]

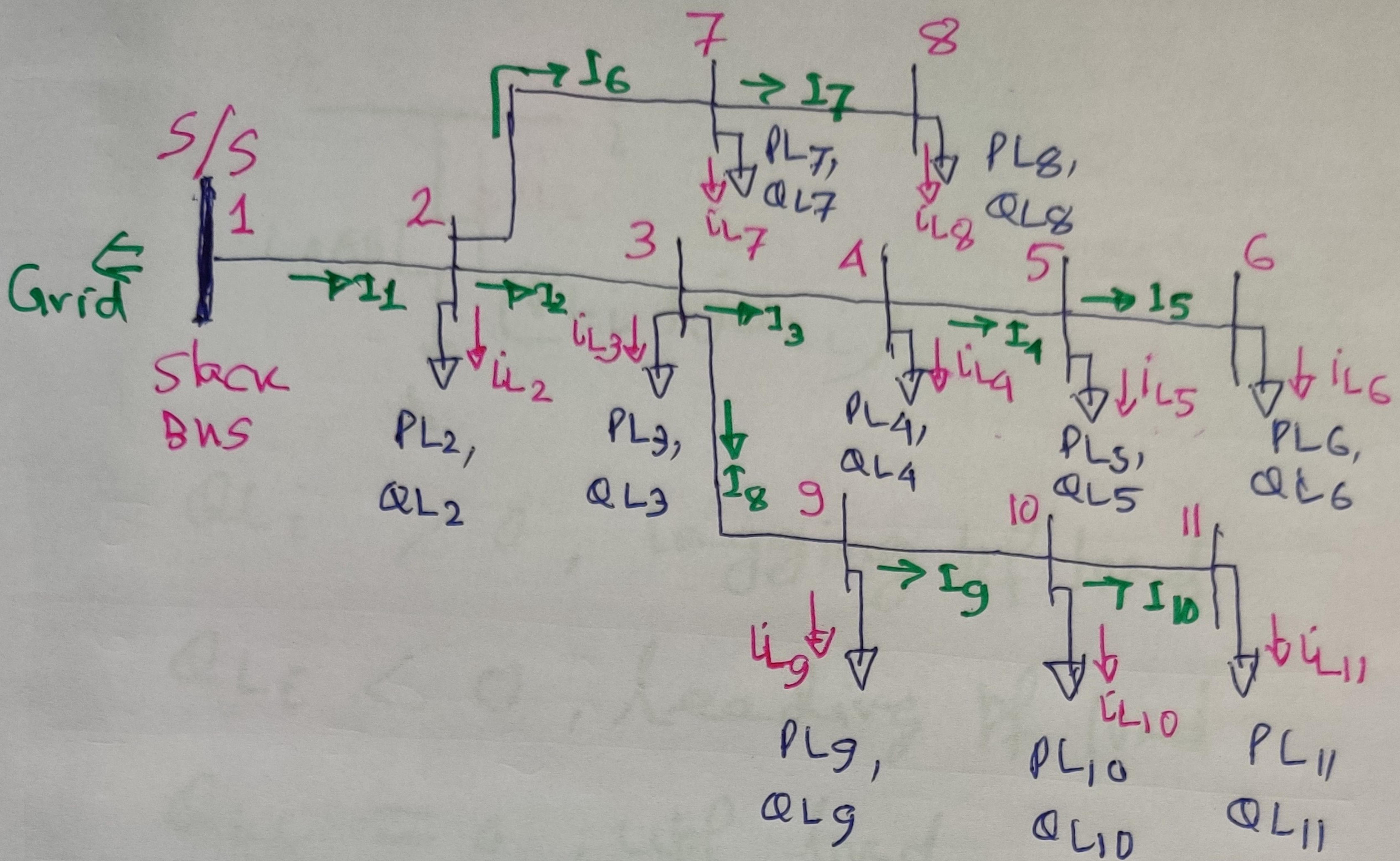

$PL \Rightarrow$ real power load

$QL \Rightarrow$ reactive power load


(PL_i, QL_i) real and reactive power load of node i respectively,

for $i = 2, 3, \dots, 11$

i_{L_i} = load current of node i

for $i = 2, 3, \dots, 11$

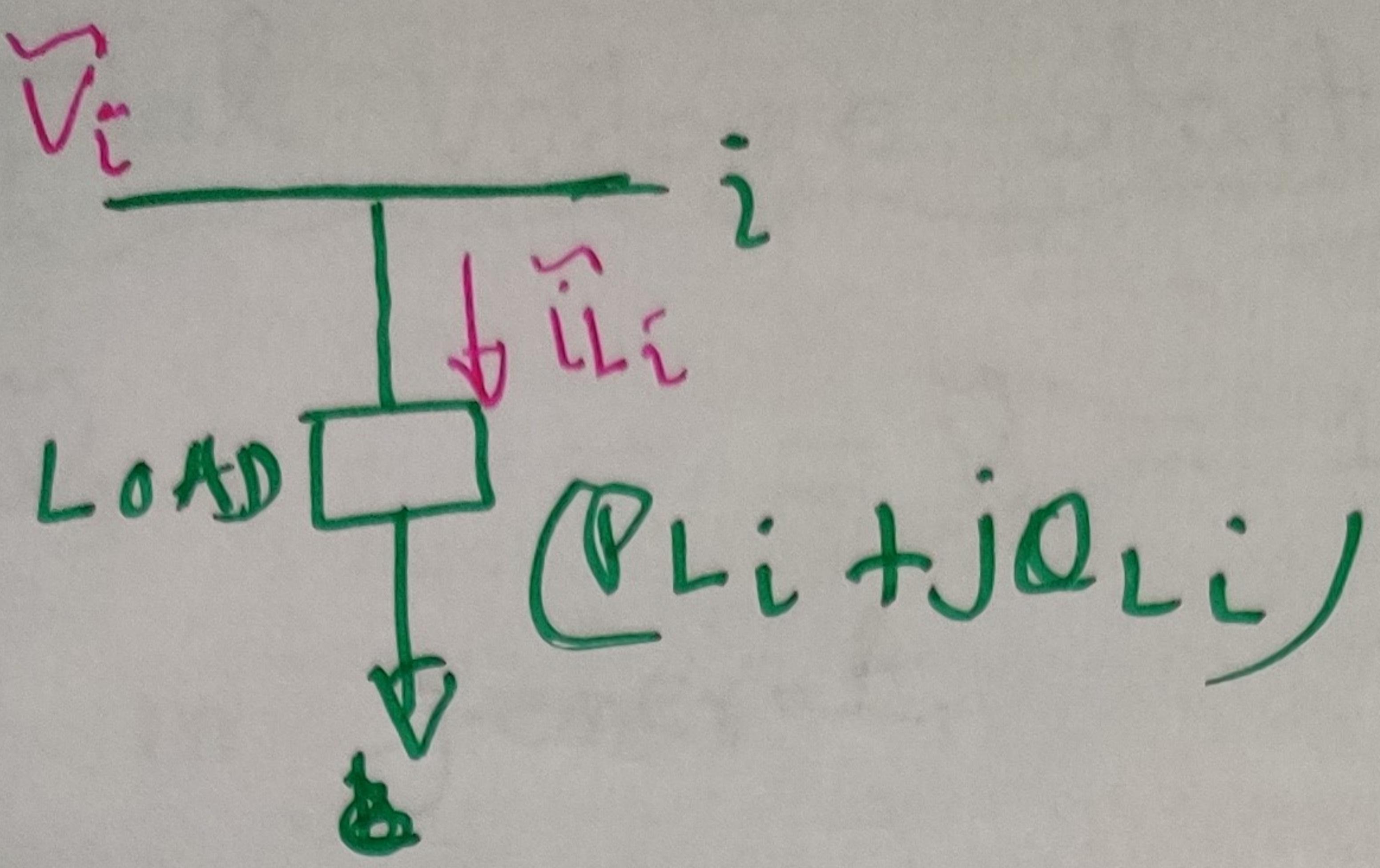$I_1, I_2, \dots, I_{10}, I_{11} \Rightarrow$ Branch currents



$Q_{L_i} > 0$, lagging pf load

$Q_{L_i} < 0$, leading pf load

$Q_{L_i} = 0$, upf load.

$$P_{L_i} - jQ_{L_i} = \tilde{V}_i^* \tilde{I}_{L_i}$$

$$\therefore \tilde{I}_{L_i} = \frac{(P_{L_i} - jQ_{L_i})}{\tilde{V}_i^*} \quad \dots \textcircled{1}$$

~~Node 1~~ Node 1 is slack bus

$$\therefore \tilde{V}_1 = V_1 \underline{\delta_1},$$

Assume $V_1 = 1.0 \text{ pu}$, $\delta_1 = 0.0^\circ$

Flat Voltage Start

$$\tilde{V}_2 = \tilde{V}_3 = \dots = \tilde{V}_{11} = 1[0^\circ] = V_1[\delta_1]$$

or in general,

$$\tilde{V}_i = V_1[\delta_1] = 1[0^\circ] \text{ pu}$$

for $i = 2, 3, \dots, 11$ (NB = 11)

Real and Reactive power loads at each node is known.

Therefore, initial load current at each node can easily be computed using Eq.(1).

After computing load currents initial branch currents can easily be computed, i.e.,

$$\begin{aligned}\tilde{I}_1 &= \tilde{i}_{L_2} + \tilde{i}_{L_3} + \tilde{i}_{L_4} + \tilde{i}_{L_5} + \tilde{i}_{L_6} + \tilde{i}_{L_7} \\ &\quad + \tilde{i}_{L_8} + \tilde{i}_{L_9} + \tilde{i}_{L_{10}} + \tilde{i}_{L_{11}}\end{aligned}$$

$$\begin{aligned}\tilde{I}_2 &= \tilde{i}_{L_3} + \tilde{i}_{L_4} + \tilde{i}_{L_5} + \tilde{i}_{L_6} + \tilde{i}_{L_9} \\ &\quad + \tilde{i}_{L_{10}} + \tilde{i}_{L_{11}}\end{aligned}$$

$$\tilde{I}_3 = \tilde{i}_{L_4} + \tilde{i}_{L_5} + \tilde{i}_{L_6}$$

$$\tilde{I}_4 = \tilde{i}_{L_5} + \tilde{i}_{L_6}$$

$$\tilde{I}_5 = \tilde{i}_{L_6}$$

$$\tilde{I}_6 = \tilde{i}_{L_7} + \tilde{i}_{L_8}$$


$$\tilde{I}_7 = \tilde{i}_{L_8}$$

$$\tilde{I}_8 = \tilde{i}_{L_9} + \tilde{i}_{L_{10}} + \tilde{i}_{L_{11}}$$

$$\tilde{I}_9 = \tilde{i}_{L_{10}} + \tilde{i}_{L_{11}}$$

$$\tilde{I}_{10} = \tilde{i}_{L_{11}}$$

..... (2)

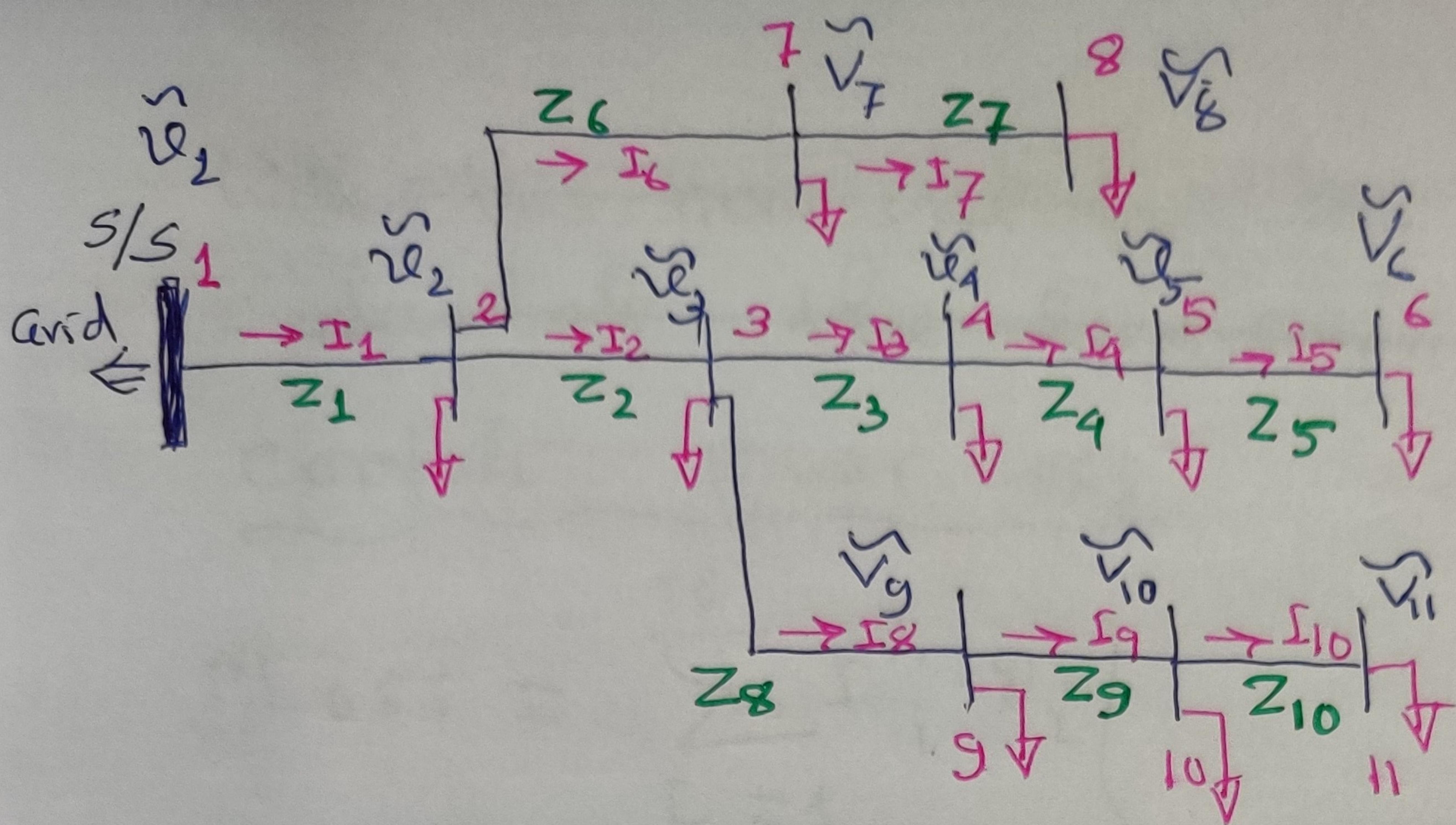

$$\begin{aligned}
 \tilde{v}_2 &= \tilde{v}_1 - I_1 z_1 \\
 \tilde{v}_3 &= \tilde{v}_2 - I_2 z_2 \\
 \tilde{v}_4 &= \tilde{v}_3 - I_3 z_3 \\
 \tilde{v}_5 &= \tilde{v}_4 - I_4 z_4 \\
 \tilde{v}_6 &= \tilde{v}_5 - I_5 z_5 \\
 \tilde{v}_7 &= \tilde{v}_6 - I_6 z_6 \\
 \tilde{v}_8 &= \tilde{v}_7 - I_7 z_7 \\
 \tilde{v}_9 &= \tilde{v}_8 - I_8 z_8 \\
 \tilde{v}_{10} &= \tilde{v}_9 - I_9 z_9 \\
 \tilde{v}_{11} &= \tilde{v}_{10} - I_{10} z_{10}
 \end{aligned}$$

-(3)

~~for m1 = fs~~

for jj = 1, 10

m1 = IS(jj)

m2 = IR(jj)

$\tilde{V}(m_2) = \tilde{V}(m_1) - I(jj) Z(jj)$

end -

~~With this new set of voltages,
calculate the load currents
compute power loss~~

$$P_{Loss} = \sum_{i=1}^{10} I_i^2 R_i \quad (1)$$

$$Q_{Loss} = \sum_{i=1}^{10} I_i^2 X_i \quad (2)$$

$I_i \Rightarrow$ magnitude of current in branch -i

With this new set of voltages,
calculate the load currents
 I_L_i using Eqn.(1) for $i = 2, 3, \dots, 11$.

Then compute branch currents using
Eqn.(2). Then compute voltages using
Eqn.(3).

Then compute Loss using Eqn (4).

Convergence Criteria

$$\Delta P = |PL_{loss}^{(k+1)} - PL_{loss}^{(k)}|$$

$$\Delta \phi = |Q_{loss}^{(k+1)} - Q_{loss}^{(k)}|$$

If $\{(\Delta P \& \Delta \phi) < \epsilon\}$ solution has
converged.