

# EE60032: Analog Signal Processing




**Dr. Ashis Maity**  
**Assistant Professor**

Email: [ashis@ee.iitkgp.ac.in](mailto:ashis@ee.iitkgp.ac.in)  
Department of Electrical Engineering  
Indian Institute of Technology, Kharagpur  
West Bengal, India

## **Module-2: Filters**
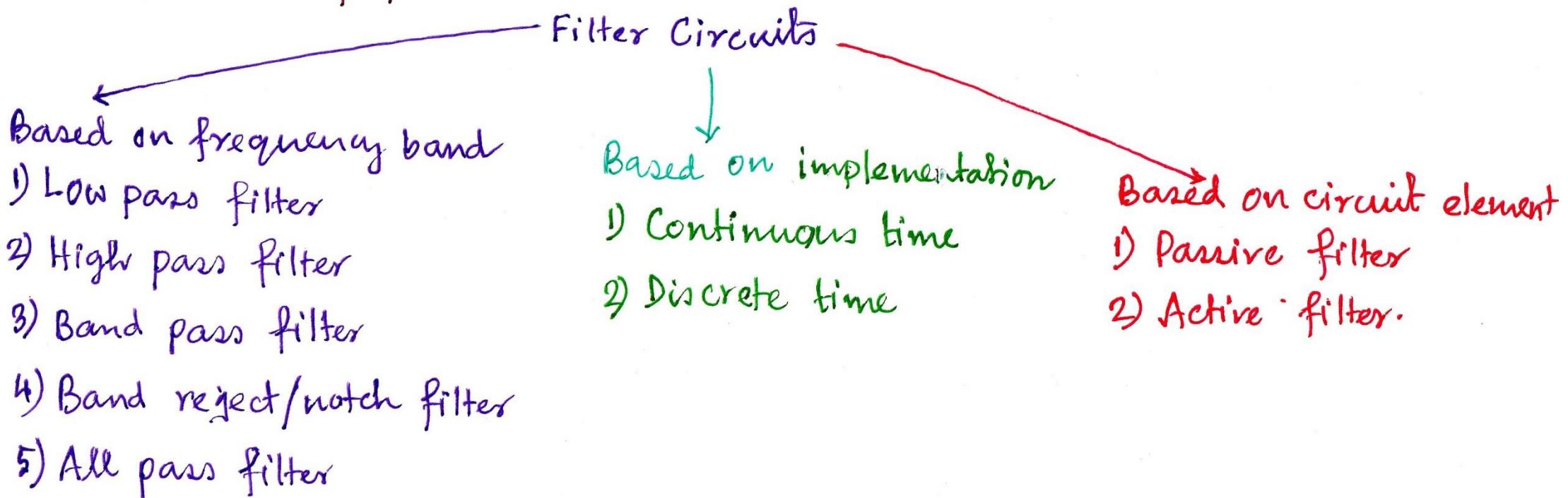
## Introduction to filters


- \* Process signals in frequency domain.
- \* Old technology : using L and C. Works well for high frequency.  
For low frequency, L and C will be bulky, introduce parasitics.
- \* Inductor less filter technology :- Passive RC filter, Active RC filter, switched capacitor filter.
- \* Classifications of filters :-



## Filter classifications
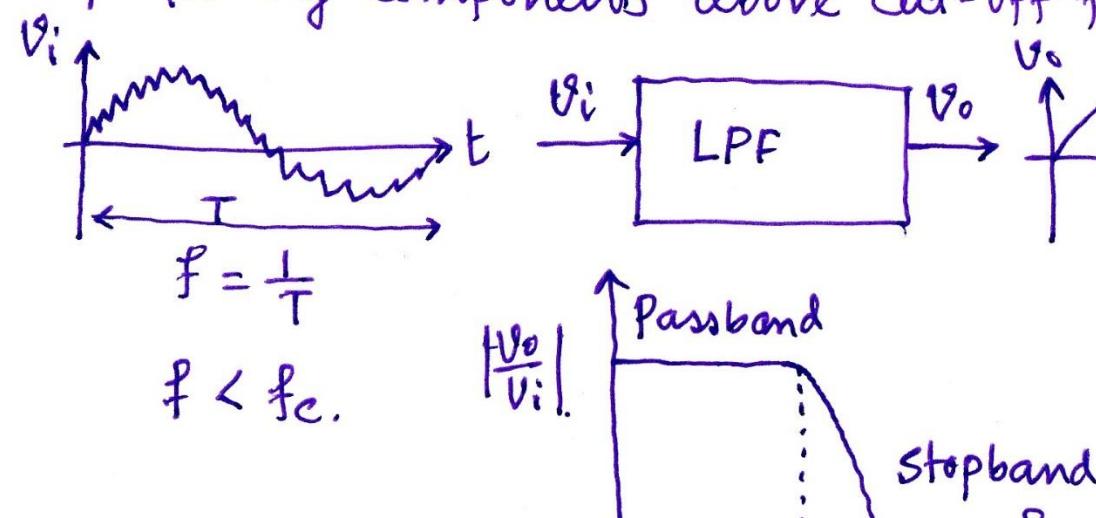
### 1) Low pass filter :- (LPF)


Passes low frequency components of a signal below cut-off frequency. Blocks the high frequency components above cut-off freq.



High frequency noise can be filtered out by using LPF.
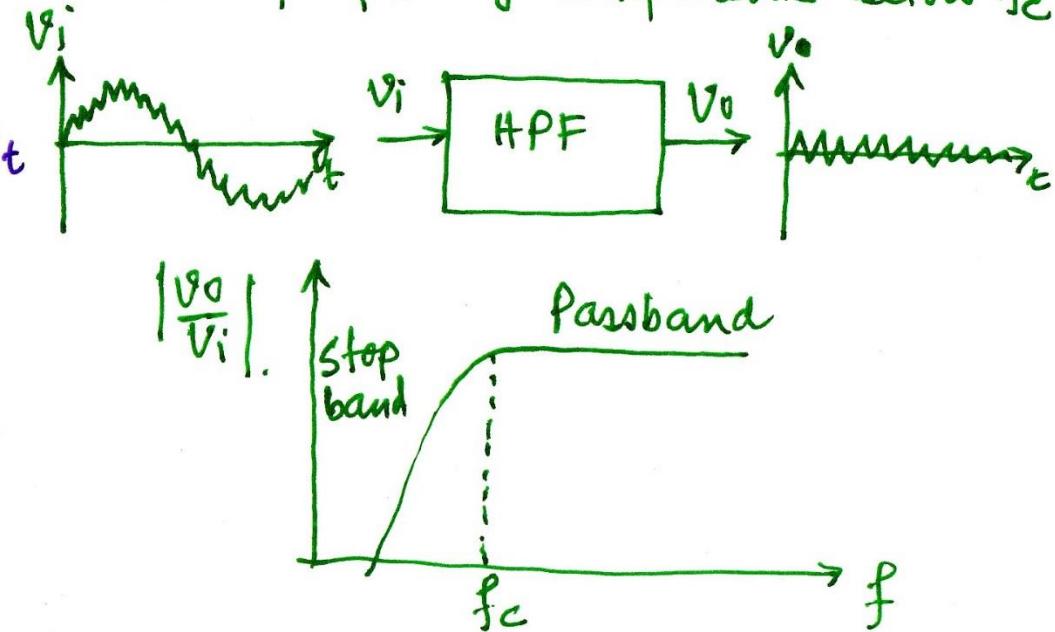
### 2) High pass filter : (HPF)

Passes the frequency components above the cut-off frequency. Attenuates the lower frequency components below  $f_c$ .





Any rectified voltage has power supply noise of 50/60 Hz. That noise can be filtered out by HPF.
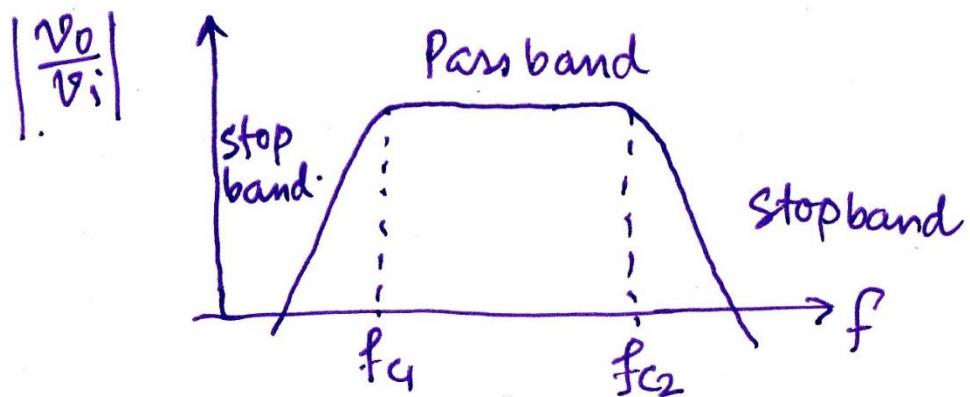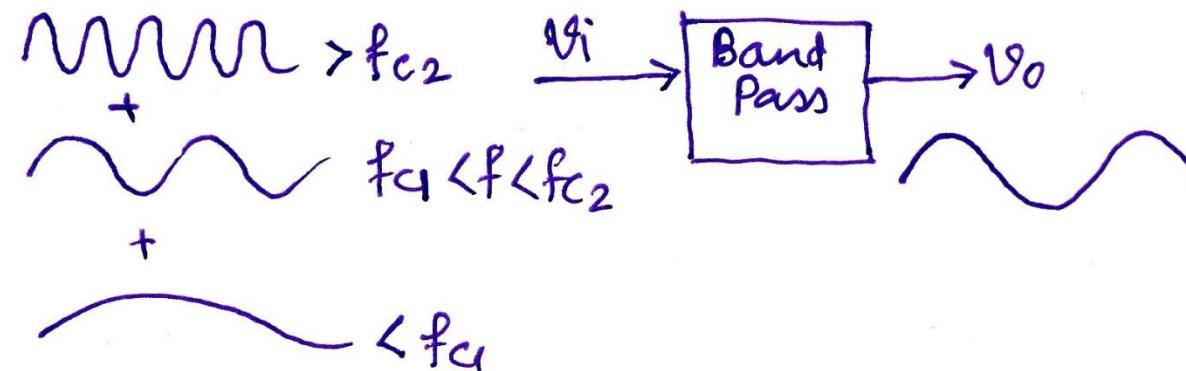
### 3) Band pass filter :-

It has two cutoff frequencies.  $f_{c1}$  and  $f_{c2}$ .



$f_{c1} \leq f \leq f_{c2}$  will be passed only.


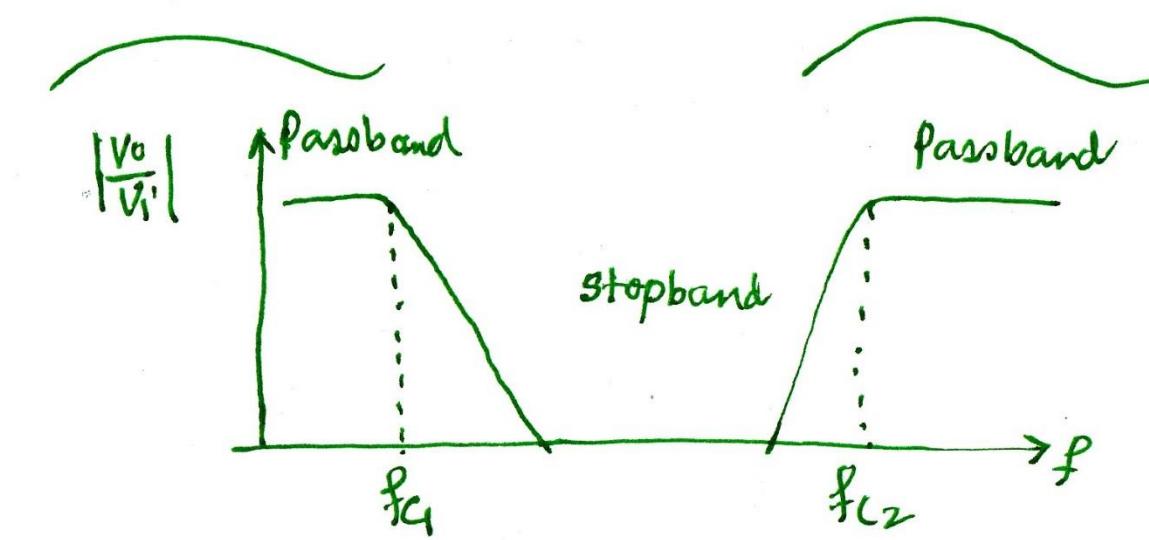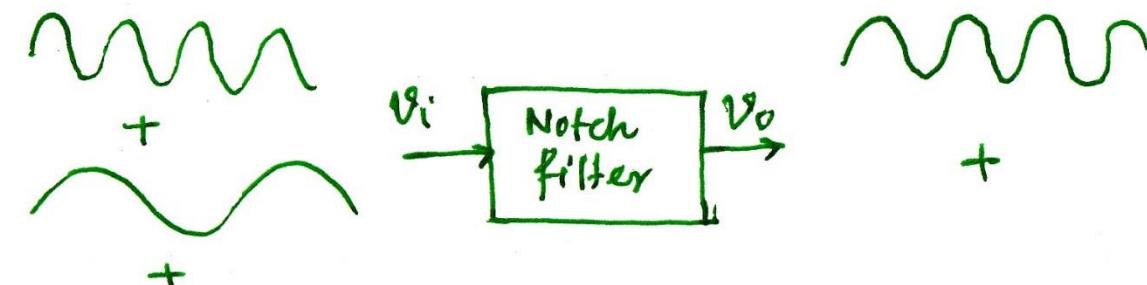
### 4) Band reject filter/notch filter:-


It also has two cut-off frequencies.  $f_{c1}$  &  $f_{c2}$ .

Here all frequency components passed except  $f_{c1} < f < f_{c2}$




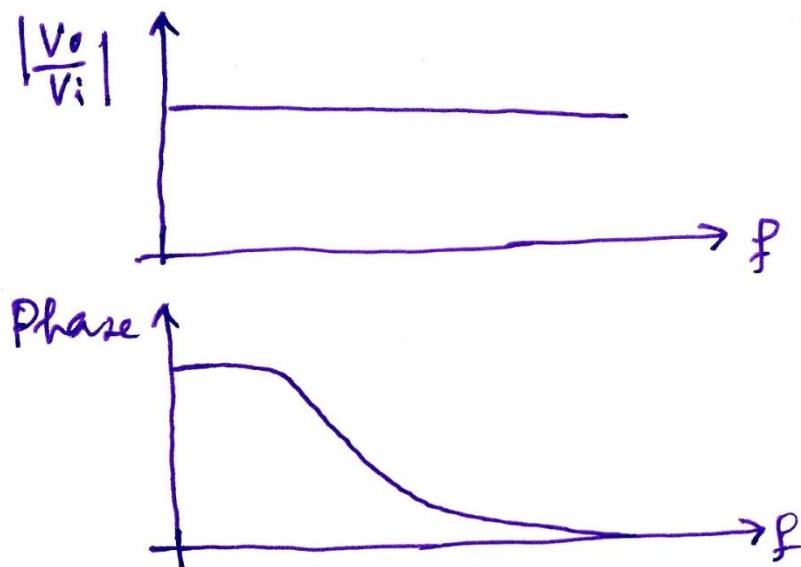5) All-pass filter / delay filter :-

passes all frequency components without equal gain. Introduce delay based on input frequency.




6) Continuous time filter :-

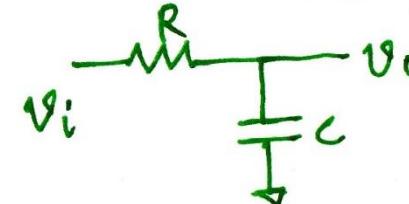


Area consuming

7) Discrete time filter :-

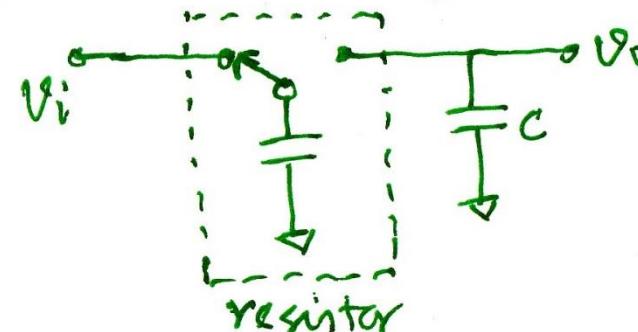


More area efficient.

8) Passive filter :-

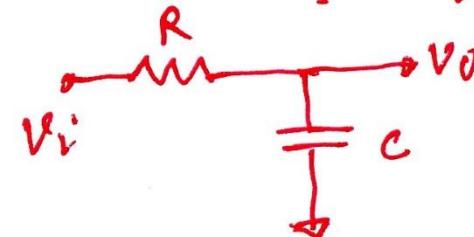

9) Active filter :-

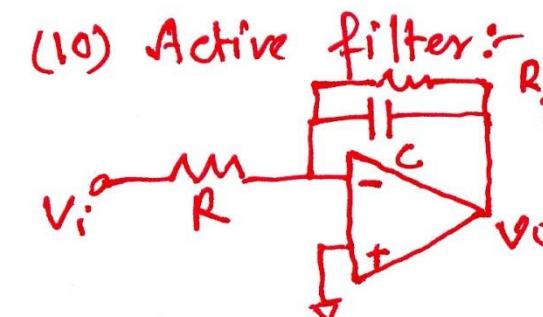



Active implementation provides more design flexibility in filter design.

## Generalised filter transfer function :-

Basic objective is to achieve a sharp transition from passband to stopband (f selectivity)

This is because : ① Interferer frequency may be close to the desired signal band.  
② Interfering level may be higher than the designed signal level.

How to achieve a high selectivity :-

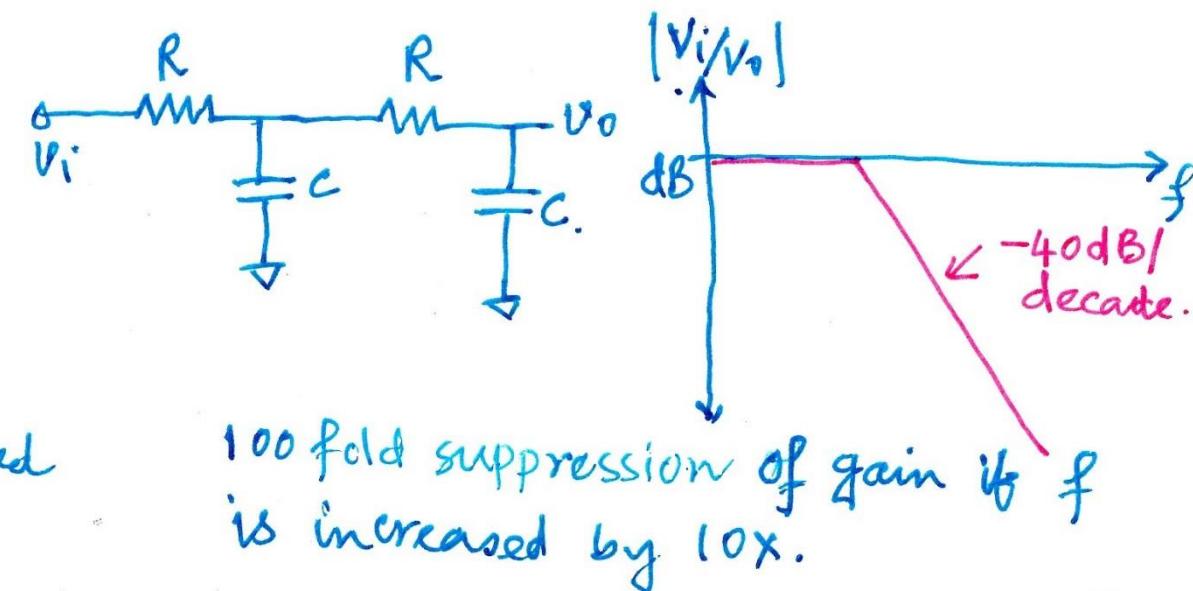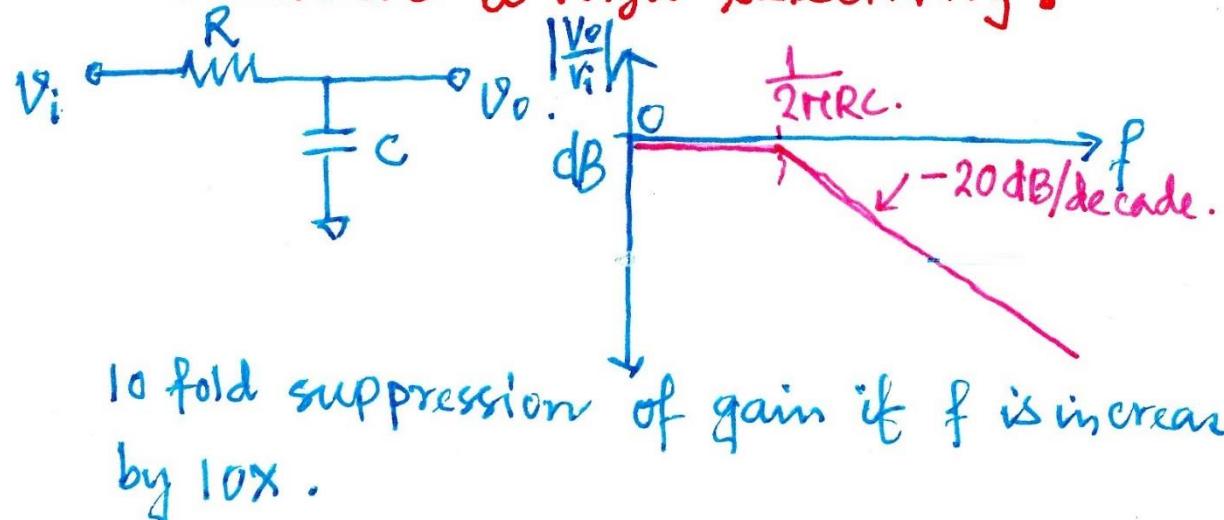

Increasing the 'order' of the transfer function can improve the frequency selectivity.

The generalised transfer function of a  $n$ th order filter :-


$$H(s) = \frac{a_M s^M + a_{M-1} s^{M-1} + \dots + a_0}{b_N s^N + b_{N-1} s^{N-1} + \dots + b_0} = \alpha \frac{(s+z_1)(s+z_2)\dots(s+z_M)}{(s+p_1)(s+p_2)\dots(s+p_N)}$$

where  $z_k$  and  $p_k$  (real or complex) denote zeros and poles respectively.

$z_k$  or  $p_k = \alpha + j\omega$ ,  $\alpha$  = real part,  $j\omega$  = imaginary part.

Few points :-

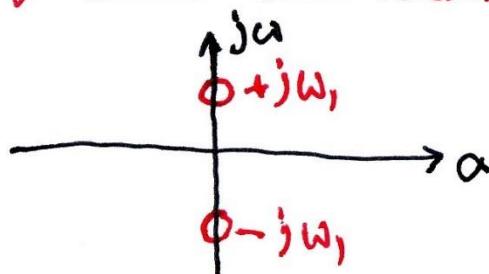- 1)  $n$  is the order of the filter.
- 2)  $n > m$ , otherwise if  $s \rightarrow \infty$ ,  $H(s) \rightarrow \infty$ , not a stable system.
- 3) Complex pole and zeros must occur in conjugate pair for better optimization.  
 $p_1 = \alpha_1 + j\omega_1$  and  $p_2 = \alpha_1 \mp j\omega_1$
- 4) If zeros are located on  $j\omega$  axis in  $s$ -plane, then  $z_{1,2} = \pm j\omega_1$ , then



the numerator will be  $(s-j\omega_1)(s+j\omega_1) = s^2 + \omega_1^2$   
At  $s = j\omega_1$ ,  $|H(s)|$  drops to zero.

Imaginary zeros are placed at stopband.

# EE60032: Analog Signal Processing



**Dr. Ashis Maity**  
**Assistant Professor**

Email: [ashis@ee.iitkgp.ac.in](mailto:ashis@ee.iitkgp.ac.in)  
Department of Electrical Engineering  
Indian Institute of Technology, Kharagpur  
West Bengal, India

## Realization of first order filter:-

$$H(s) = \frac{a_1 s + a_0}{s + \omega_0} = \frac{a_1 (s + \frac{a_0}{a_1})}{s + \omega_0}; \text{ pole} = -\omega_0, \text{ zero} \cdot z_1 = -\frac{a_0}{a_1}.$$


Depending on the location of poles and zero, we get different transfer fns.

### Low pass filter (LPF):

Zero occurs at a very high frequency compared to pole frequency. i.e.  $\omega_0 \gg \omega_p$ .


$$H(s) = \frac{a_1 (s + \frac{a_0}{a_1})}{s + \omega_0} \approx \frac{a_1}{s + \omega_0} \text{ for } \frac{a_0}{a_1} \gg \omega_0 s$$

$$= \frac{\omega_0}{s + \omega_0}, |H(0)| = \frac{\omega_0}{\omega_0}, \text{ and } \omega_p = -\omega_0.$$

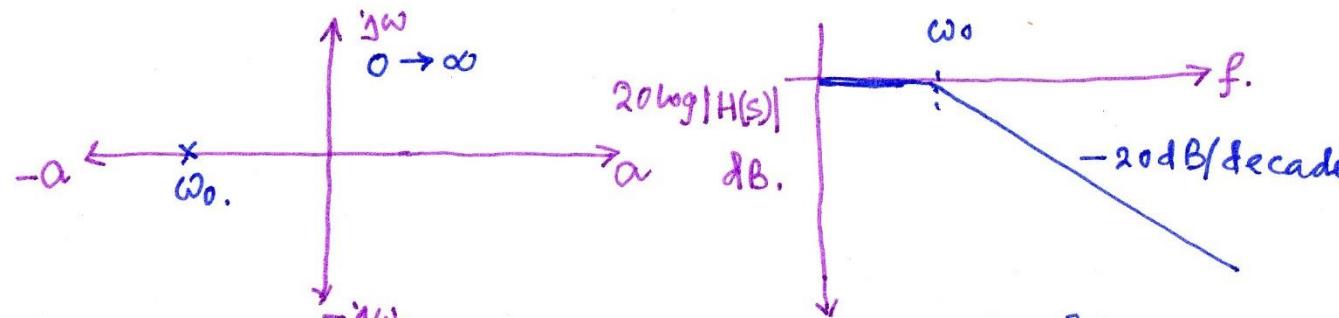


Pole-zero locations at s-plane.

### Passive realization:-

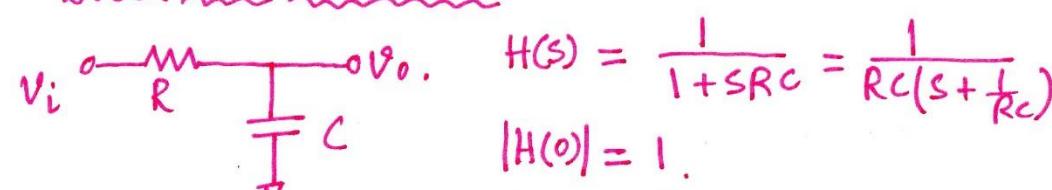

$$\omega_0 = \frac{1}{RC}.$$


### Active realization:-

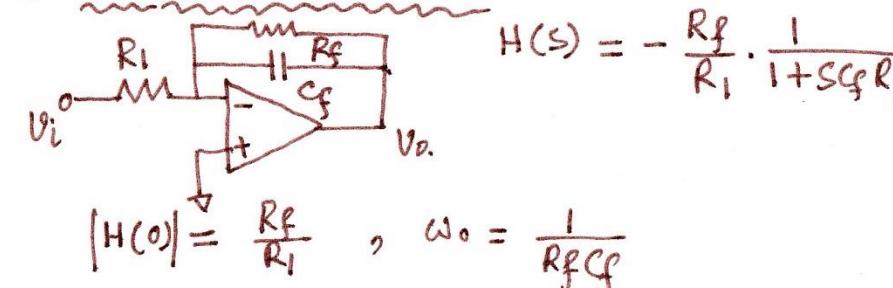

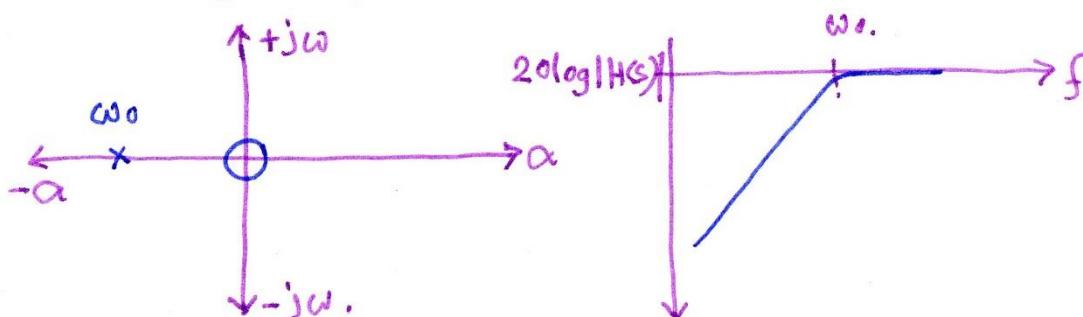
## ① High pass filter : (HPF)

$$H(s) = \frac{a_1(s + \frac{\omega_0}{a_1})}{s + \omega_0} \approx \frac{s a_1(1 + \frac{\omega_0}{a_1}s)}{s + \omega_0} \approx \frac{a_1 s}{s + \omega_0}$$

for  $s \gg \frac{\omega_0}{a_1}$  ;  $\beta_1 = -\omega_0$ ,  $\chi_1 = 0$ .





## ② Active realization :-

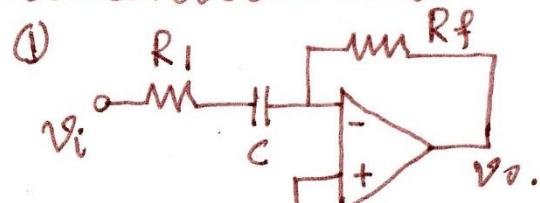


$$H(s) = -\frac{s R_f C}{1 + s R_1 C}.$$

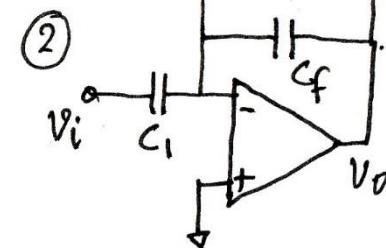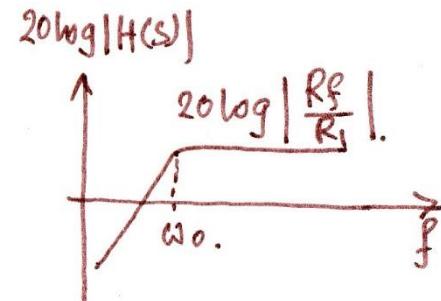High frequency gain =  $\frac{R_f}{R_1}$   
 $\omega_0 = \frac{1}{R_1 C}$ .



$$H(s) = -\frac{s G_f R_f}{1 + s G_f R_f}$$

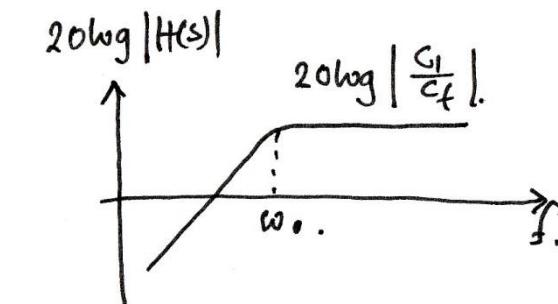
High frequency gain =  $\frac{G_f C_f}{R_f}$   
 $\omega_0 = \frac{1}{R_f C_f}$



④ Note : Band pass and band reject filters can not be realized in first order.

Try yourself :- Generalised structure of low-pass and high-pass filter:

1) Passive implementation :-

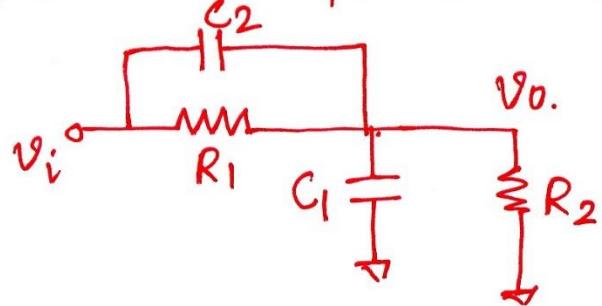


DC gain = ?

High frequency gain = ?


Pole  $\omega_0$  = ?

Zero  $\omega_Z$  = ?

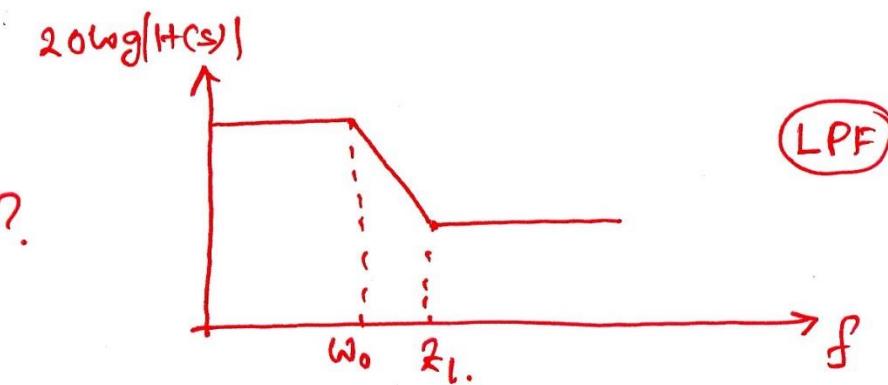


Draw the ~~step~~ relative positions of pole and zero in ~~at~~ s-plane for LPF and HPF characteristic. Also, draw gain characteristic.

2) Active implementation :-

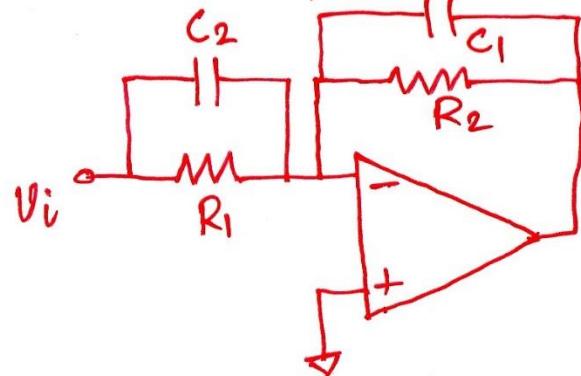


Repeat the same as ~~asked~~ asked in previous problem.

### First order all-pass filter :-

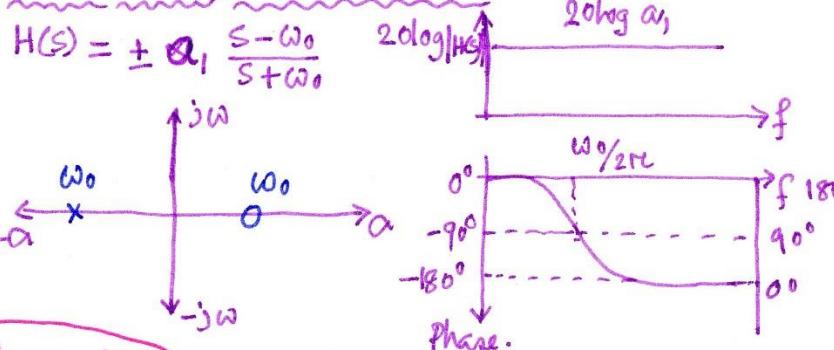

### Phase-lead

#### Passive implementation :-

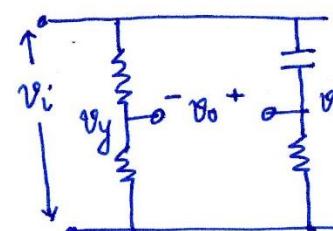

$$V_x = \frac{V_i}{2}$$


$$V_x = \frac{V_i S R C}{1 + S R C}$$

$$V_o = V_x - V_y \\ = -\frac{1}{2} \left[ \frac{1 - S R C}{1 + S R C} \right]$$

$$\text{DC gain} = \frac{1}{2}$$

$$\omega_0 = -\omega_2 = \frac{1}{R C}, \quad \theta = 180^\circ - 2 \tan^{-1} \left( \frac{\omega}{\omega_0} \right)$$

#### Active implementation :-

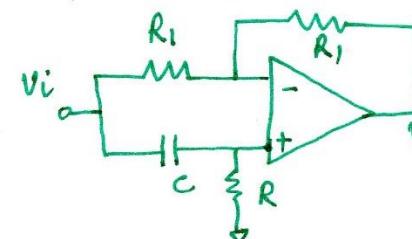


$$H(s) = -\frac{(1 - S R C)}{(1 + S R C)}$$

$$\theta = 180^\circ - 2 \tan^{-1} \left( \frac{\omega}{\omega_0} \right)$$

$$\text{DC gain} = 1, \quad \omega_0 = -\omega_2 = \frac{1}{R C}$$

### Active implementation :-

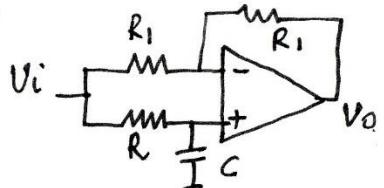

$$H(s) = \frac{1 - S R C}{1 + S R C}$$

$$\theta = -2 \tan^{-1} \left( \frac{\omega}{\omega_0} \right)$$

$$\text{DC gain} = 1, \quad \omega_0 = -\omega_2 = \frac{1}{R C}$$

# EE60032: Analog Signal Processing




**Dr. Ashis Maity**  
**Assistant Professor**

Email: [ashis@ee.iitkgp.ac.in](mailto:ashis@ee.iitkgp.ac.in)  
Department of Electrical Engineering  
Indian Institute of Technology, Kharagpur  
West Bengal, India

## Second order filter :-

Various ways : ① use of LCR resonator    ② cascading first order filter.


### LCR Resonator :-

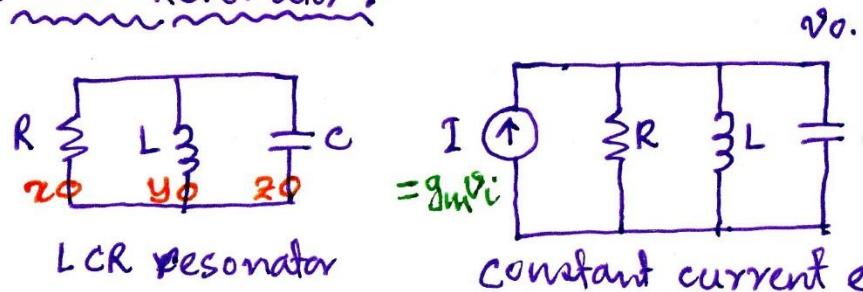

LCR Resonator

constant current excitation.

### Cascading First order filter :-

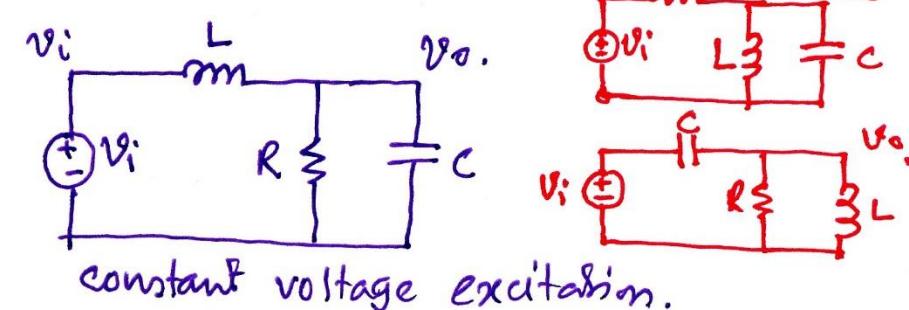

constant voltage excitation.

### Analysis with constant current excitation:-

$$I = \frac{V_o}{R} + \frac{V_o}{1/SC} + \frac{V_o}{sL}$$

$$\text{or, } \frac{V_o}{I} = \frac{s/c}{s^2 + \frac{s}{RC} + \frac{1}{LC}} = \frac{s/c}{s^2 + s \frac{\omega_0}{\alpha} + \omega_0^2}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}, \quad \frac{\omega_0}{\alpha} = \frac{1}{RC} \Rightarrow \alpha = R\sqrt{\frac{C}{L}}$$

### Observations :-

- $\omega_0$  and  $\alpha$  values are same in both the cases; however, the numerator is different.
- In fact, any nodes labelled as x, y, z can be disconnected from ground and connected to  $V_i$  without altering the natural modes  $\omega_0$  and  $\alpha$ . However, the numerator will be changed in these cases.


### Analysis with constant voltage excitation

$$V_o = \frac{V_i}{sL + \frac{R}{1+SCR}} \times \frac{R}{1+SCR}$$

$$\frac{V_o}{V_i} = \frac{1/LC}{s^2 + s \cdot \frac{1}{CR} + \frac{1}{LC}} = \frac{1/LC}{s^2 + s \frac{\omega_0}{\alpha} + \omega_0^2}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}, \quad \frac{\omega_0}{\alpha} = \frac{1}{CR} \Rightarrow \alpha = R\sqrt{\frac{C}{L}}$$
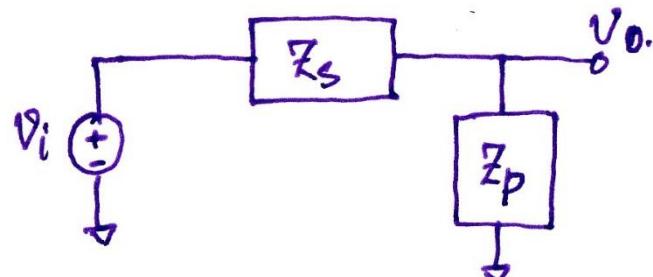
## ② Intuitive understanding of adding transmission zeros:






$$\frac{V_o}{V_i}(s) = \frac{Z_p}{Z_p + Z_s}$$


$Z_p$  and  $Z_s$  do not go to zero/infinity simultaneously.

Different Cases :-

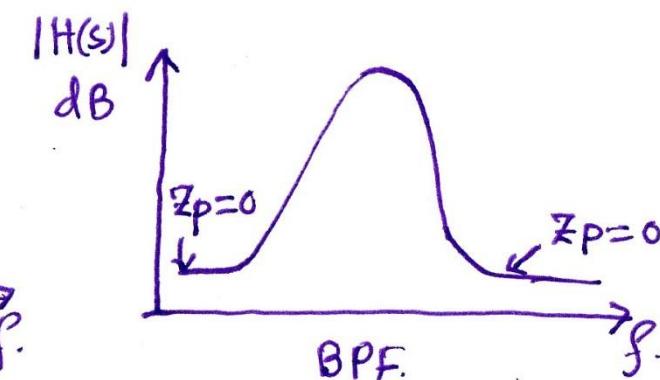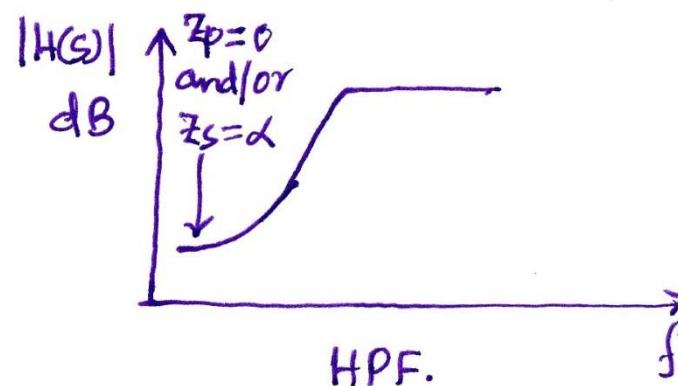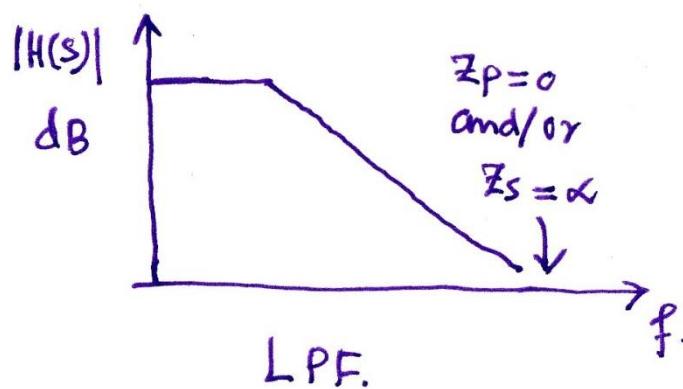- a) If at high frequency,  $Z_p$  gets shorted and/or  $Z_s$  gets infinity, it acts as LPF.
- b) If at ~~high~~<sup>low</sup> frequency,  $Z_s$  becomes infinity and/or  $Z_p$  becomes zero, it acts as HPF.
- c) If  $Z_s$  remains constant, but  $Z_p$  falls to zero at both low & high frequency, then it acts as a BPF.



## Realization of Lowpass filter:-

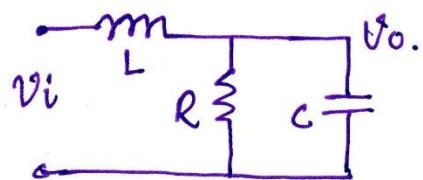



$$Z_S = SL ; s \rightarrow \infty, Z_L \rightarrow \infty$$

$$Z_P = \frac{R}{1+SCR} ; s \rightarrow 0, Z_P \rightarrow 0.$$

$$H(s) = \frac{1}{s^2 + \frac{s}{RC} + \frac{1}{LC}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}, \alpha = R\sqrt{\frac{1}{LC}}, |H(s)| = 1$$
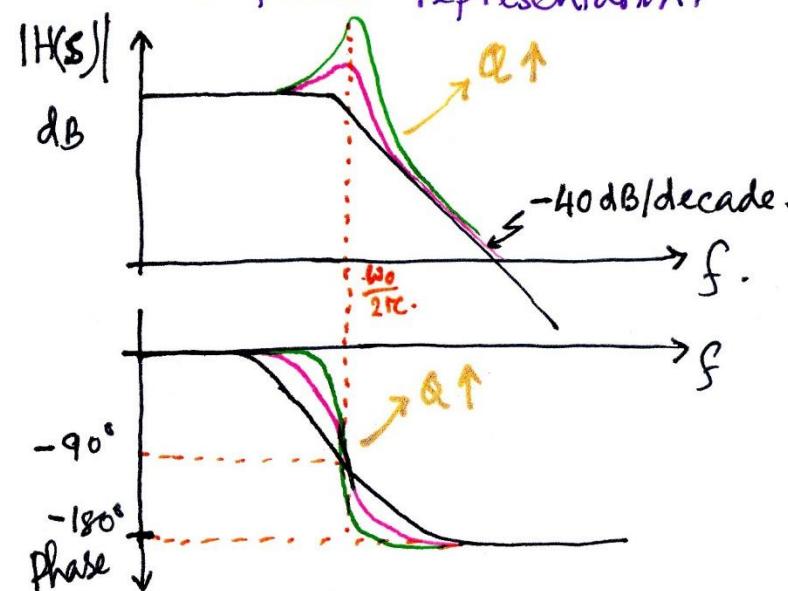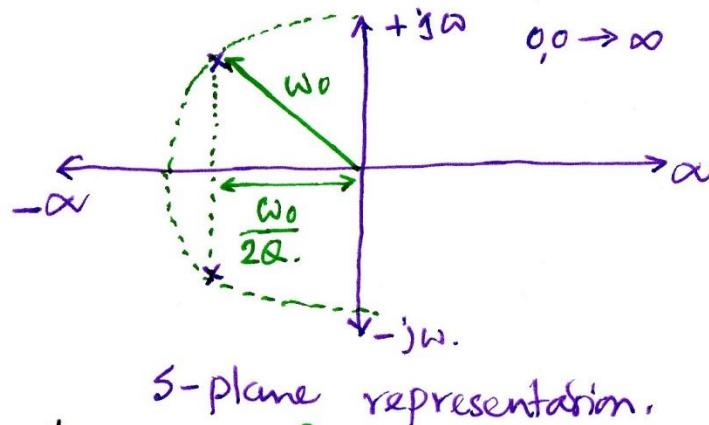
$$H(s) = \frac{\alpha_0}{s^2 + \frac{\alpha \omega_0}{Q} s + \omega_0^2}$$




Important observation :-

- a) If  $\alpha = 0.5$ , poles are real.
- b) If  $\alpha > 0.5$ , poles are complex
- c) The effect of  $\alpha$  will be exploited in filter design.

Important observation :-

- a) If  $Q$  increases, the gain roll-off will be higher than  $-40 \text{ dB/decade}$  even in second order filter.
- b) A high  $Q$  provides better frequency selectivity, sharper transition band.
- c) Play with  $Q$  values.



## Realization of high pass filter :-

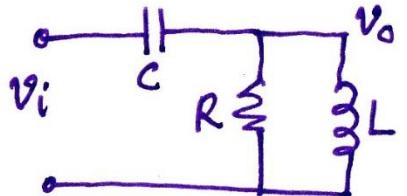


$$S \rightarrow 0, Z_S \rightarrow \infty$$

$$S \rightarrow 0, Z_P \rightarrow 0.$$
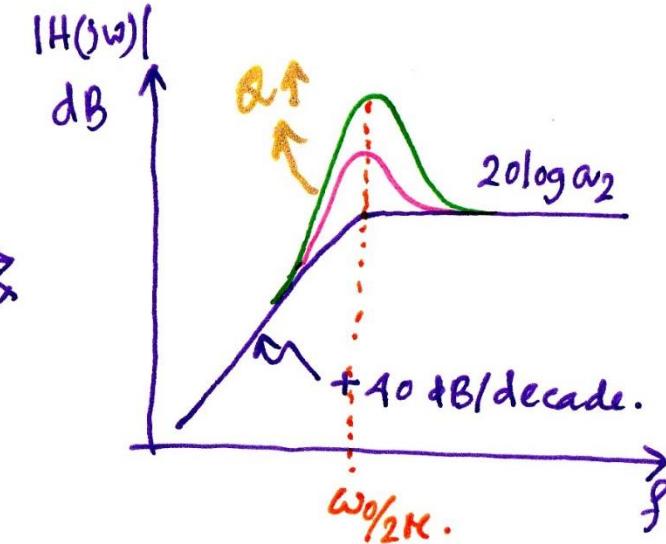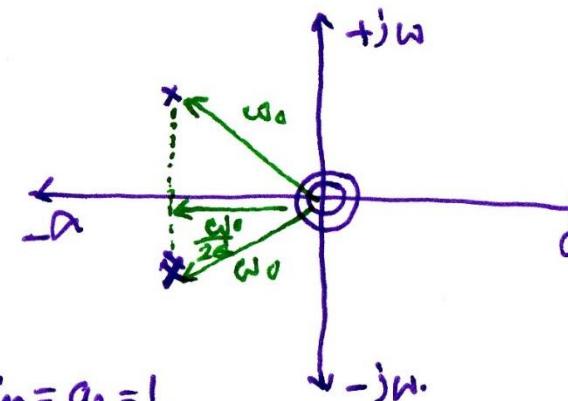
$$\begin{aligned} H(s) &= \frac{s^2}{s^2 + s(\frac{1}{RC}) + \frac{1}{LC}} \\ &= \frac{a_2 s^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2} \\ \omega_0 &= \frac{1}{\sqrt{LC}}, Q = R \sqrt{\frac{C}{L}}, \text{ HF gain } = a_2 = 1. \end{aligned}$$





## Realization of band-Pass filter :-

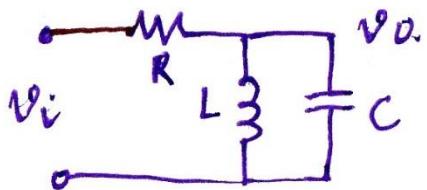

$$S \rightarrow 0, Z_P \rightarrow 0.$$

$$S \rightarrow \infty, Z_P \rightarrow 0.$$
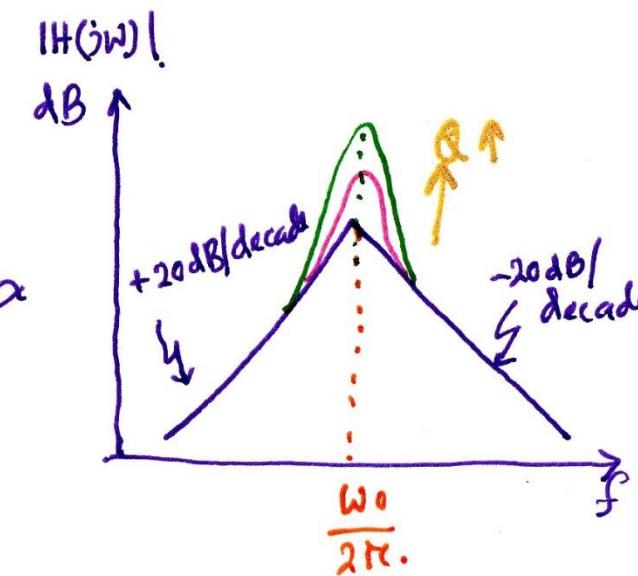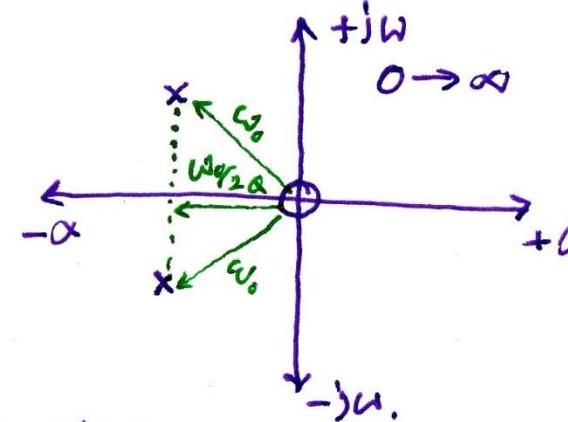
$$\begin{aligned} H(s) &= \frac{s/R}{s^2 + \frac{s}{RC} + \frac{1}{LC}} \\ &= \frac{a_1 s}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2} \\ \omega_0 &= \frac{1}{\sqrt{LC}}, Q = R \sqrt{\frac{C}{L}}, \text{ Intermediate gain } = a_1 = 1. \end{aligned}$$




# EE60032: Analog Signal Processing



**Dr. Ashis Maity**  
**Assistant Professor**

Email: [ashis@ee.iitkgp.ac.in](mailto:ashis@ee.iitkgp.ac.in)  
Department of Electrical Engineering  
Indian Institute of Technology, Kharagpur  
West Bengal, India
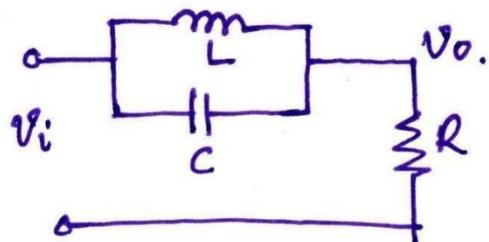
## Realization of notch/band reject filter:-





Required zeros at  $\omega_0$  to create stopband.

$$H(s) = \frac{s^2 + \left(\frac{1}{LC}\right)^2}{s^2 + \frac{s}{RC} + \frac{1}{LC}}$$

$$= Q_2 \frac{(s^2 + \omega_0^2)}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}, Q = R\sqrt{\frac{C}{L}}$$


Low and high freq gain =  $Q_2$

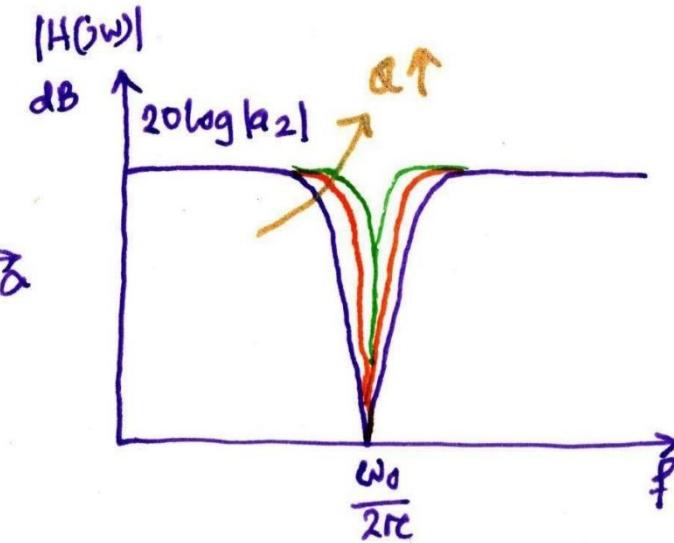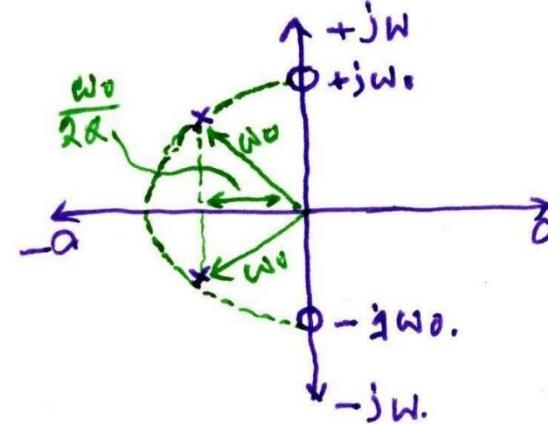

- a) Here Q-factor of the poles is much lower than the same of the zeros. The Q-factor of zeros  $\gg \infty$
- b) If the Q-factor of poles is increased the notch frequency will be more selective.
- c) If the Q-factor of poles is infinity then they coincide with zeros and cancel each other without notching action.

① Realization of all-pass filter :-

② Phase-lag filter :-

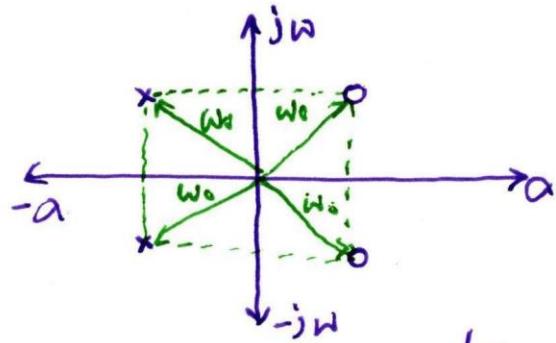


$$H(s) = \frac{a_2[s^2 - s \frac{\omega_0}{Q} + \omega_0^2]}{[s^2 + s \frac{\omega_0}{Q} + \omega_0^2]}$$

$$= 1 - \frac{2s \frac{\omega_0}{Q}}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

BPF

$$H'(s) = \frac{H(s)}{0.5} = 0.5 - \frac{s \frac{\omega_0}{Q}}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

$$= (V_y - V_x)$$

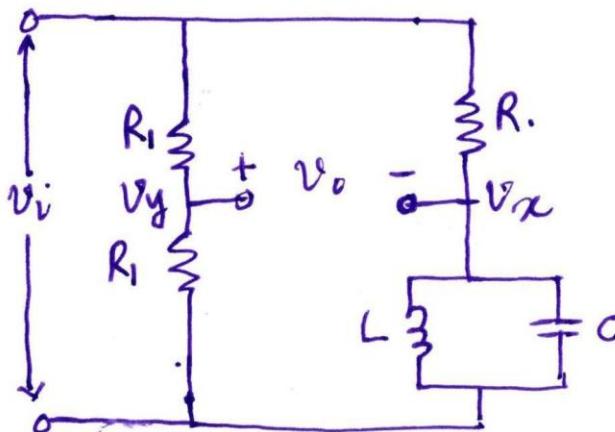


\* Disadvantage :-

Do not have common ground point.


(Generalized expression)

[if  $a_2 = 1$ ]

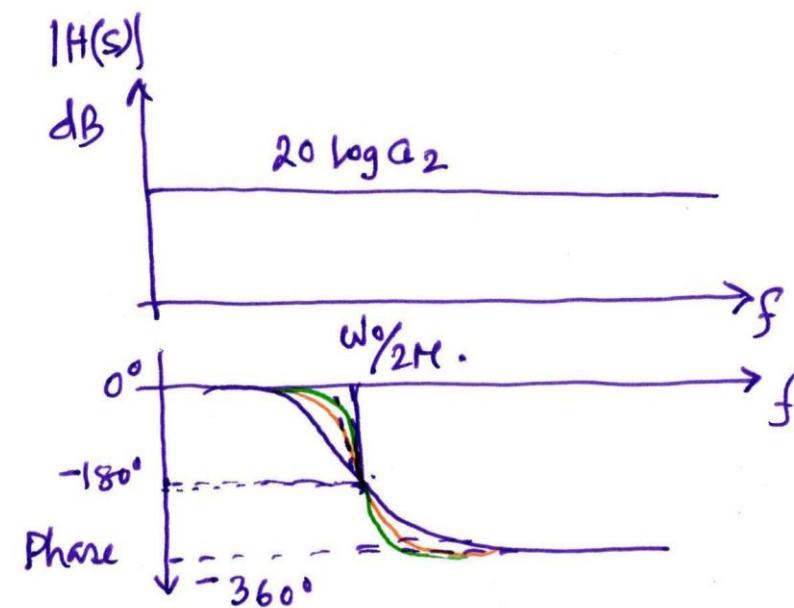

Effect of Q-factor?

### b) Phase-lead filters.

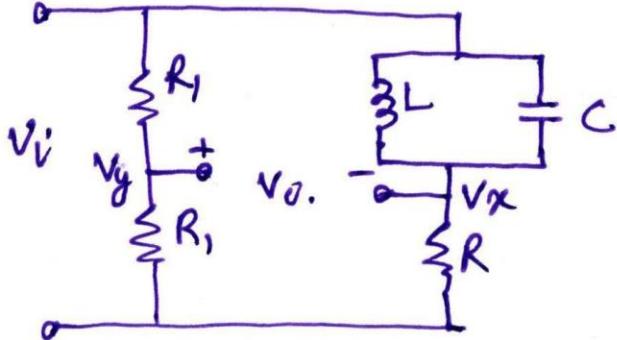


Band reject filter.

$$H(s) = 0.5 - \frac{s^2 + \omega_0^{-2}}{s^2 + 2\frac{\omega_0}{Q}s + \omega_0^2}$$

$$= -0.5 \frac{s^2 - 2\frac{\omega_0}{Q}s + \omega_0^2}{s^2 + 2\frac{\omega_0}{Q}s + \omega_0^2}$$
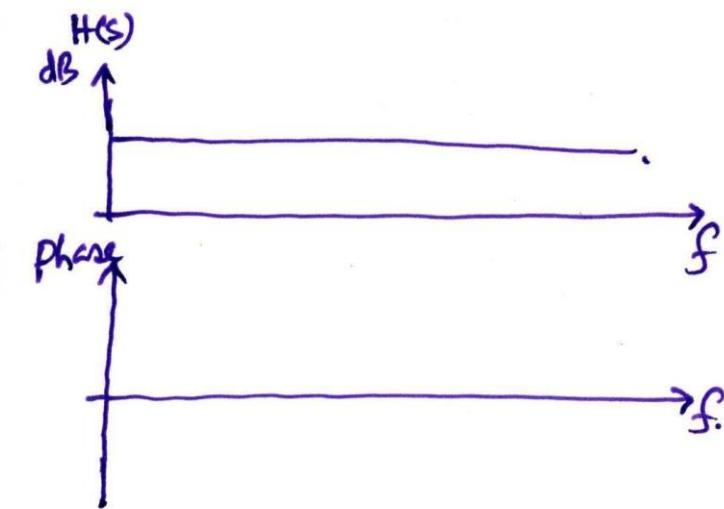
$$\theta = 180^\circ - 4\arctan\left(\frac{\omega}{\omega_0}\right)$$



Initial phase is starting from  $180^\circ$ .

End phase =  $-180^\circ$ .

Phase leading over entire range is not possible.

### Advantages of LCR resonator filter:-

- ① Suitable for high frequency application.
- ② Controlling Q-value provides additional flexibility.

### Disadvantages of LCR resonator filter:-

- ① Not suitable for low frequency application.
- ② Difficult to realize in on-chip implementation.


# EE60032: Analog Signal Processing



**Dr. Ashis Maity**  
**Assistant Professor**

Email: [ashis@ee.iitkgp.ac.in](mailto:ashis@ee.iitkgp.ac.in)  
Department of Electrical Engineering  
Indian Institute of Technology, Kharagpur  
West Bengal, India

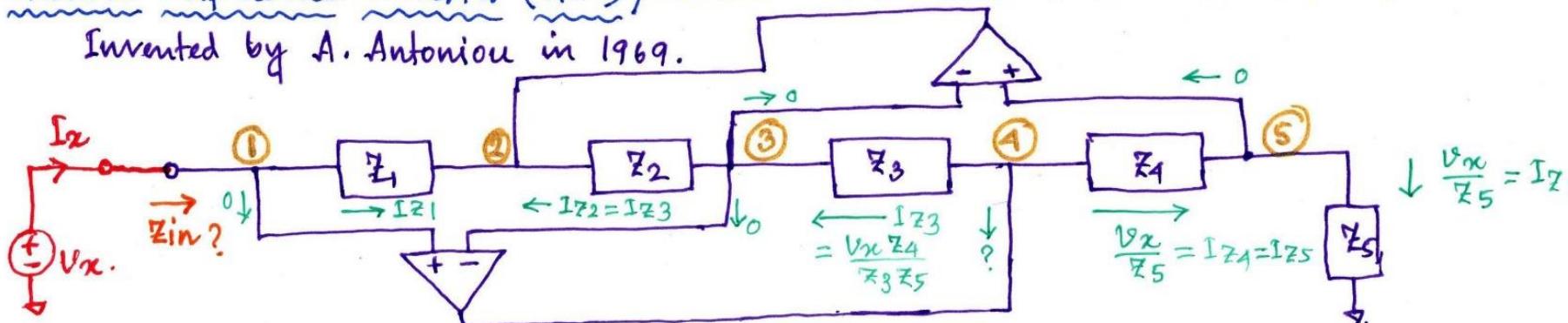General Impedance Converter (GIC) / Antoniou Inductance Simulation circuit :-  
Invented by A. Antoniou in 1969.



$$V_1 = V_3 = V_5 = V_x.$$

$$V_4 = V_x + \frac{V_x}{Z_5} \cdot Z_4$$

$$\begin{aligned} I_{Z3} &= \frac{V_4 - V_3}{Z_3} = \frac{V_x + \frac{V_x}{Z_5} \cdot Z_4 - V_x}{Z_3} \\ &= V_x \cdot \frac{Z_4}{Z_3 Z_5} \end{aligned}$$

$$V_2 = V_3 - I_{Z2} \cdot Z_2 = V_3 - I_{Z3} \cdot Z_2$$

$$= V_x - \frac{V_x Z_4 Z_2}{Z_3 Z_5}$$

$$\begin{aligned} I_{Z1} &= I_x = \frac{V_x - V_2}{Z_1} = \frac{V_x - V_x + \frac{V_x Z_4 Z_2}{Z_3 Z_5}}{Z_1} \\ &= V_x \frac{Z_4 Z_2}{Z_1 Z_3 Z_5} \end{aligned}$$

$$Z_{in} = \frac{V_x}{I_x} = \frac{Z_1}{Z_2} \cdot \frac{Z_3}{Z_4} \cdot Z_5$$

Observations :-

a) Based on the impedance of  $Z_1 - Z_5$ ,  $Z_{in}$  will change.

Examples:

i) If  $Z_1 = R_1$ ,  $Z_3 = R_3$ ,  $Z_4 = R_4$ ,  $Z_5 = R_5$ ,  $Z_2 = \frac{1}{sC_2}$   
then  $Z_{in} = \frac{R_1}{sC_2} \cdot \frac{R_3}{R_4} \cdot R_5 = s C_2 R_1 \cdot \frac{R_3}{R_4} \cdot R_5$


$Z_{in}$  becomes inductive       $\boxed{\boxed{Z_L = C_2 R_1 R_3 \frac{R_5}{R_4}}}$   
Always emulates grounded L

ii) If  $Z_1 = R_1$ ,  $Z_2 = R_2$ ,  $Z_3 = R_3$ ,  $Z_4 = \frac{1}{sC_4}$ ,  $Z_5 = R_5$   
then  $Z_{in} = \frac{R_1}{R_2} \cdot \frac{R_3}{sC_4} \cdot R_5 = s \frac{R_1}{R_2} \cdot R_3 C_4 \cdot R_5$


$Z_{in}$  becomes inductive       $\boxed{\boxed{L = \frac{R_1}{R_2} \cdot R_3 C_4 R_5}}$   
Emulates grounded L.

iii) If  $Z_1/Z_3/Z_5$  are capacitive, then  $Z_{in}$  remains capacitive.


## High pass filter using GIC element :-

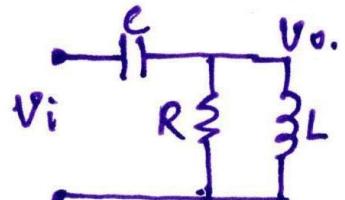
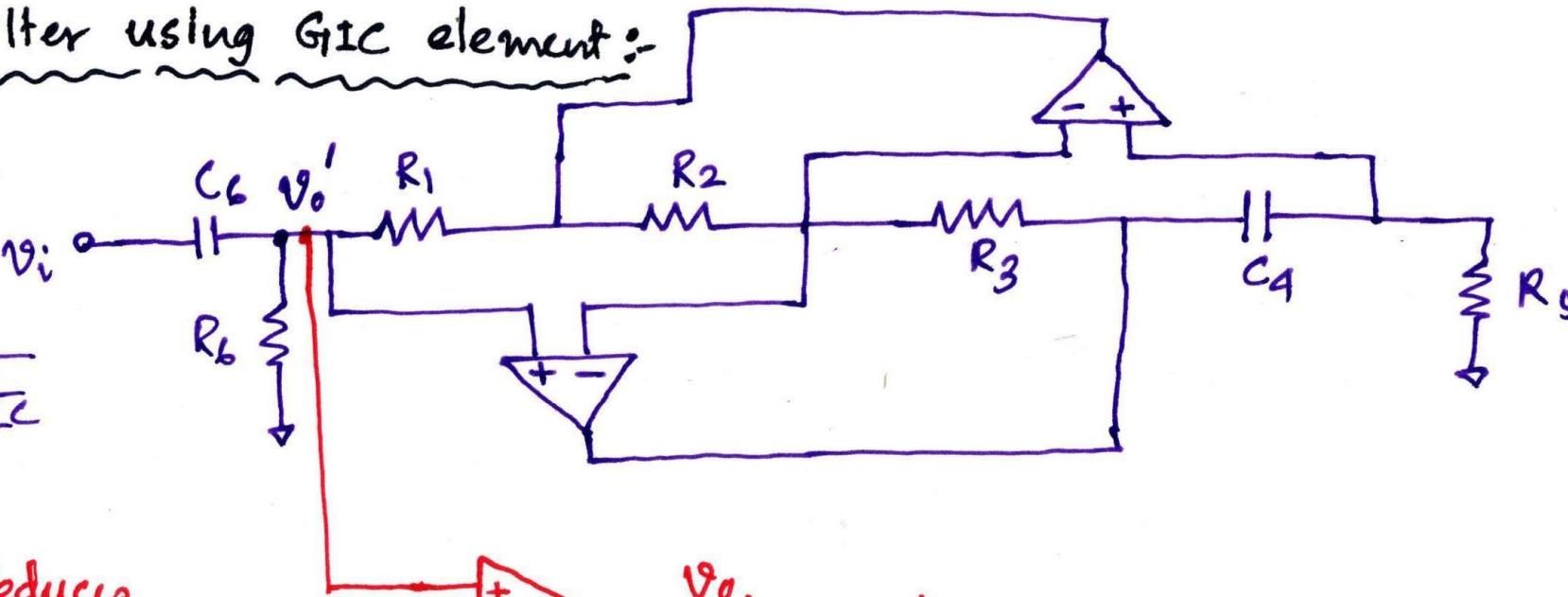
$$H(s) = \frac{\omega^2}{\omega^2 + \omega_{c}^2 R_C + f_C}$$



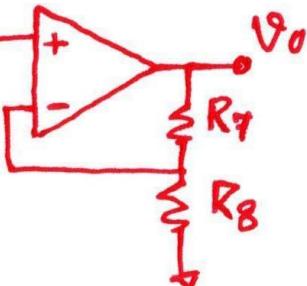- Reduces loading effect.
- Provide additional DC gain of K.



$$K = \left(1 + \frac{R_7}{R_8}\right)$$

$$Z_{T_n} = \frac{R_1}{R_2} \cdot \frac{R_3}{f_{SCA}} \cdot R_5$$


$$L = \frac{R_1}{R_2} R_3 C_A R_5$$

$$H(s) = \frac{K \omega^2}{\omega^2 + \omega_c^2 \frac{1}{R_6 C_6} + \frac{R_2}{C_6 R_1 R_3 C_A R_5}}$$


$$\omega_0 = \sqrt{\frac{R_2}{C_6 R_1 R_3 C_A R_5}}$$

$$\Omega = R_6 \sqrt{\frac{C_6 R_2}{R_1 R_3 C_A R_5}}$$

## Band-Pass filter using GIC :-

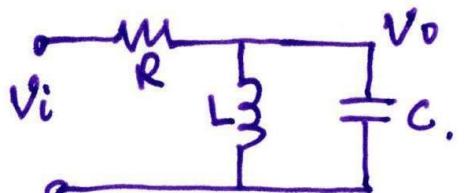

$$H(s) = \frac{s/RC}{s^2 + s/RC + 1/C}$$

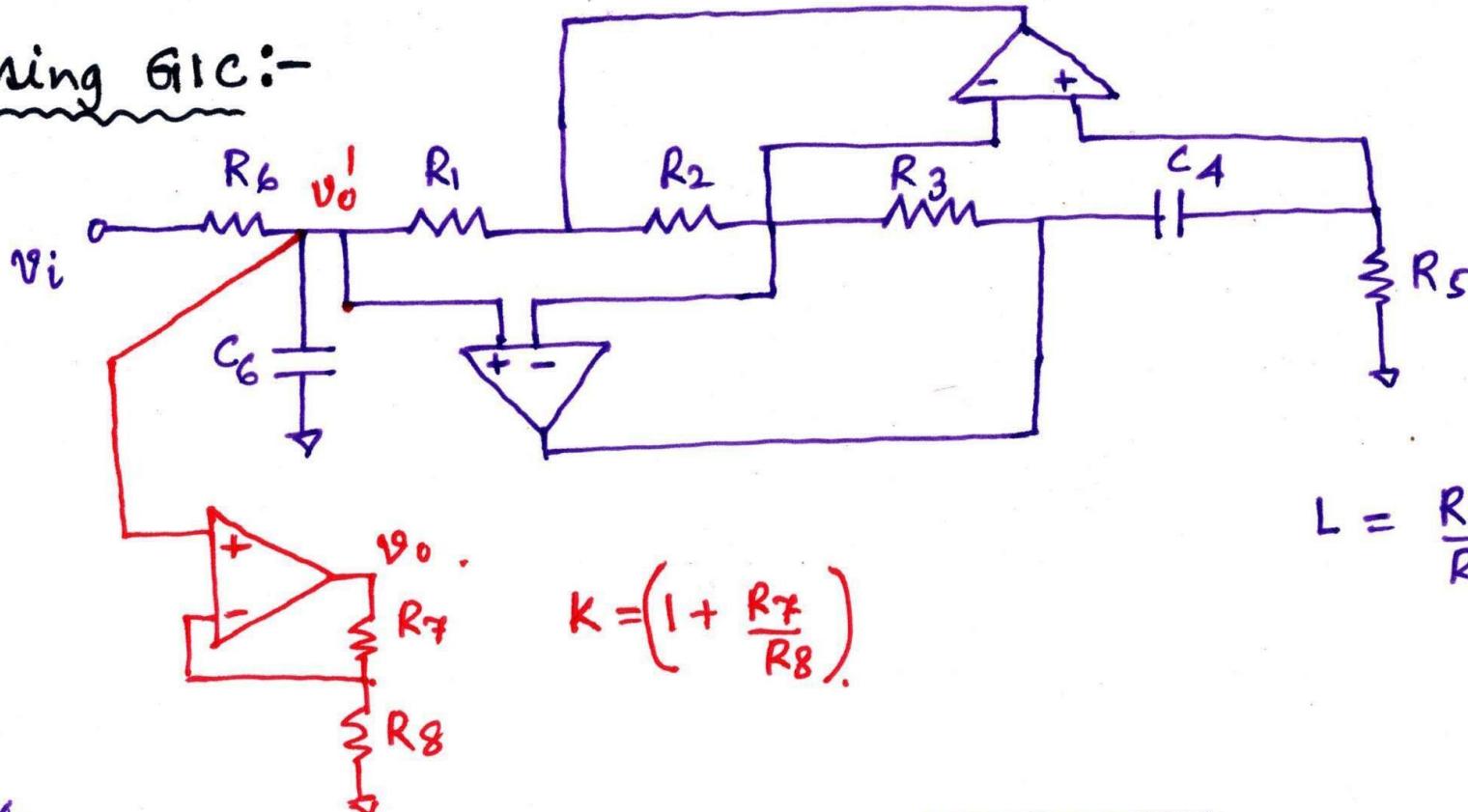

$$K = \left(1 + \frac{R_7}{R_8}\right)$$


$$H(s) = \frac{K s / R_6 C_6}{s^2 + \frac{s}{R_6 C_6} + \frac{R_2}{C_6 R_1 R_3 C_4 R_5}}$$

$$\omega_0 = \sqrt{\frac{R_2}{C_6 R_1 R_3 C_4 R_5}}$$


$$\alpha = R_6 \sqrt{\frac{C_6 R_2}{R_1 R_3 C_4 R_5}}$$

$$L = \frac{R_1}{R_2} R_3 C_4 R_5$$
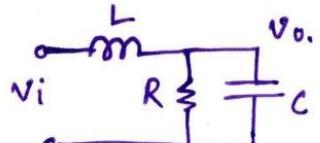
## Q How to develop a Lowpass filter using GIC :-



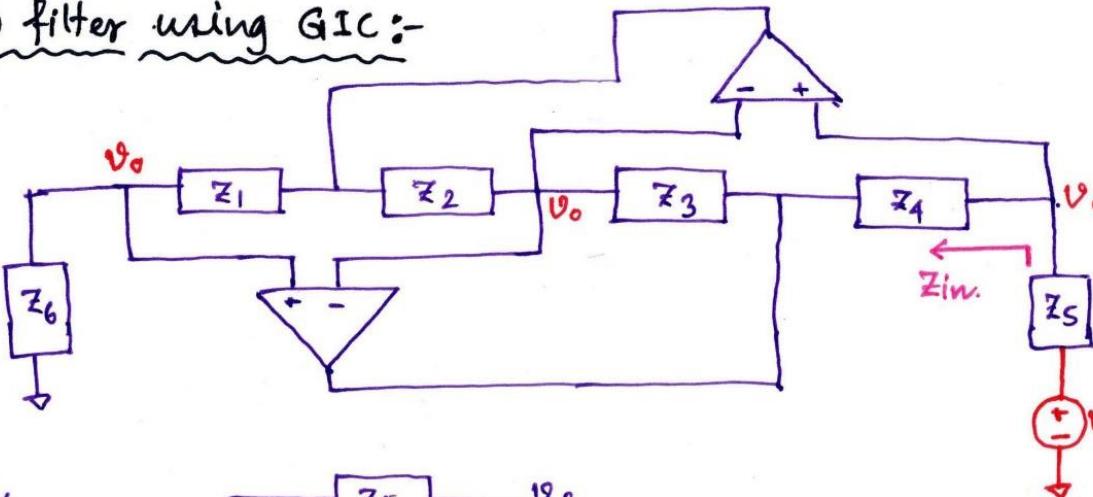
$$H(s) = \frac{1}{s^2 + \frac{1}{RC} + \frac{1}{LC}}$$



$$Z_{in} = \frac{Z_4}{Z_3} \cdot \frac{Z_2}{Z_1} \cdot Z_6$$

$$V_o = \frac{V_i Z_{in}}{Z_5 + Z_{in}}$$
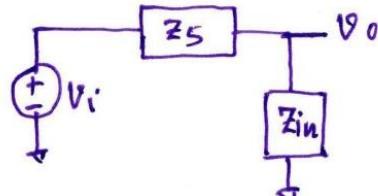
$$\text{or, } \frac{V_o}{V_i} = \frac{Z_{in}}{Z_5 + Z_{in}}$$




$$\frac{V_o}{V_i} = \frac{\frac{R_2 R_6}{R_1 R_3 S C_4 (1 + S C_6 R_6)}}{R_5 + \frac{R_2 R_6}{R_1 R_3 S C_4 (1 + S C_6 R_6)}}$$

$$= \frac{\frac{R_2 R_6}{R_1 R_3 R_5 C_4 C_6 R_6 s^2 + R_1 R_3 R_5 C_4 s + R_2 R_6}}{R_1 R_3 R_5 C_4 C_6 R_6 s^2 + R_1 R_3 R_5 C_4 s + R_2 R_6} = \frac{\frac{R_2}{R_1 R_3 R_5 C_4 C_6}}{s^2 + \frac{s}{R_6 C_6} + \frac{R_2}{R_1 R_3 R_5 C_4 C_6}}$$

denominator is same as HPF & BPF  
numerator is also same.

## Low pass filter (Continued) :-

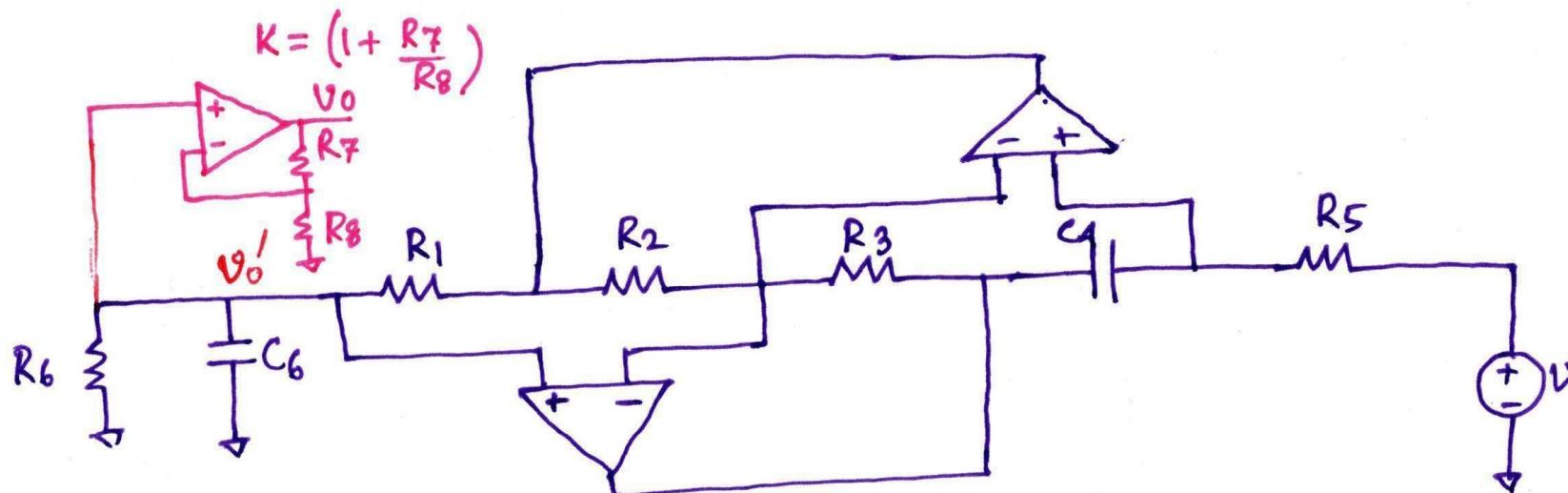

$$\frac{V_o}{V_i} (s) = H(s) = \frac{K \frac{R_2}{R_1 R_3 R_5 C_4 C_6}}{s^2 + \frac{s}{R_6 C_6} + \frac{R_2}{R_1 R_3 R_5 C_4 C_6}}$$

$$\omega_0 = \sqrt{\frac{R_2}{R_1 R_3 R_5 C_4 C_6}}$$

$$Q = R_6 \sqrt{\frac{C_6 R_2}{R_1 R_3 C_4 R_5}}$$



# EE60032: Analog Signal Processing



**Dr. Ashis Maity**  
**Assistant Professor**

Email: [ashis@ee.iitkgp.ac.in](mailto:ashis@ee.iitkgp.ac.in)  
Department of Electrical Engineering  
Indian Institute of Technology, Kharagpur  
West Bengal, India

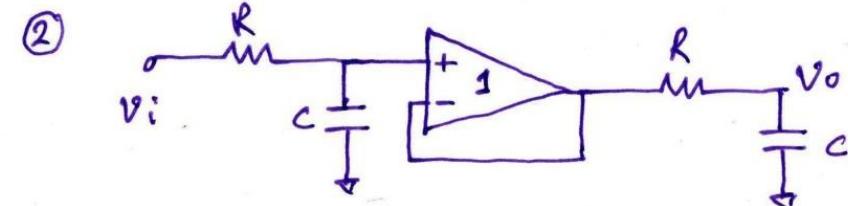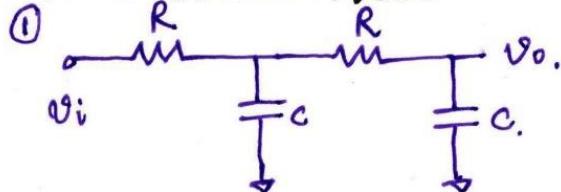Second order filter :- Two first order filter connected in cascade.



Try yourself :-

$$\frac{V_o}{V_i} = \frac{1}{C^2 R^2 \left[ s^2 + s \frac{3}{RC} + \frac{1}{R^2 C^2} \right]}$$


$$\frac{V_o}{V_i} = \frac{1}{C^2 R^2 \left[ s^2 + s \frac{2}{RC} + \frac{1}{R^2 C^2} \right]} = \frac{1}{(1 + sRC)^2}$$

• Cascading passive filter may introduce loading effect.

$$\omega_0 = \frac{1}{RC}$$

$$\frac{\omega_0}{Q} = \frac{3}{RC}$$

$$\text{or, } Q = \frac{1}{3} = 0.33.$$

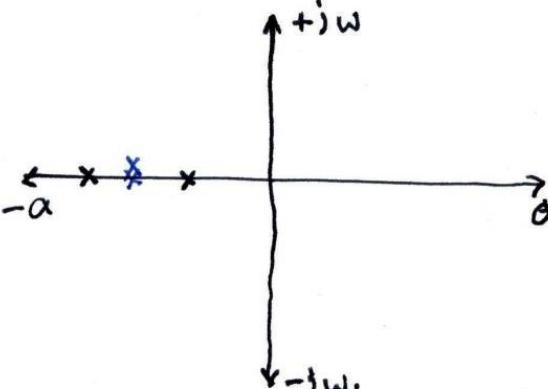

$$\omega_0 = \frac{1}{RC}$$

$$\frac{\omega_0}{Q} = \frac{2}{RC}$$


$$\text{or, } Q = \frac{1}{2} = 0.5.$$

Key observations :-

- Q-factor is fixed.
- Q-factor also changes with loading effect.
- Poles are real ; Case 1 : two different real roots ; Case 2 : same real roots.
- As poles are real, you can't play with Q-factor.




KRC Filter/Sallen Key filter :- Invented by Sallen-Key to improve  $\alpha$ -factor.

Basic concept :-

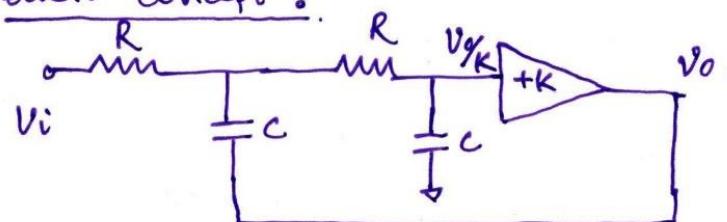


- $V_i$  faces two first order low pass filters
- $V_o$  faces one first order high pass filter and one first order low pass filter.

How? Assume  $V_i = 0$ ,

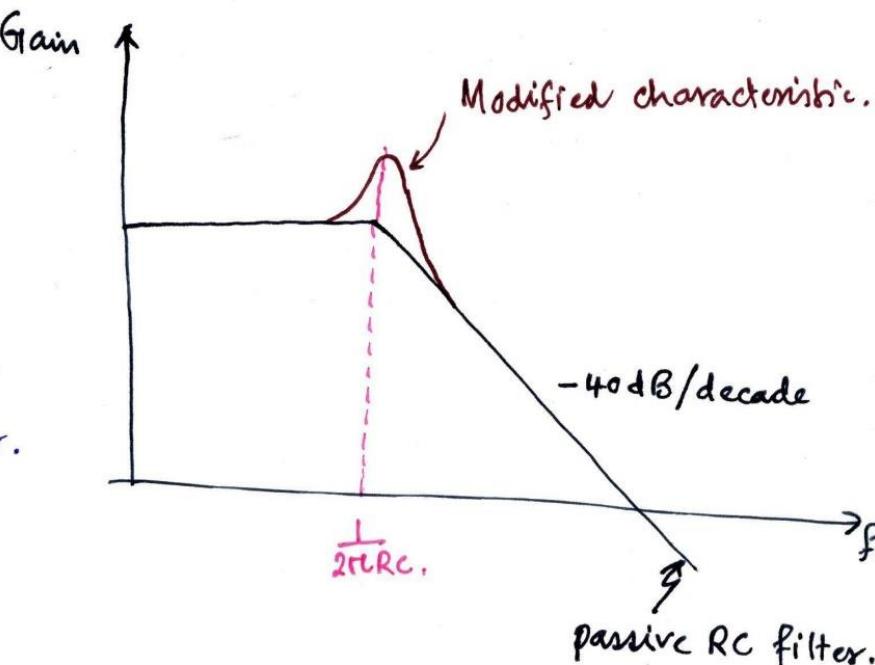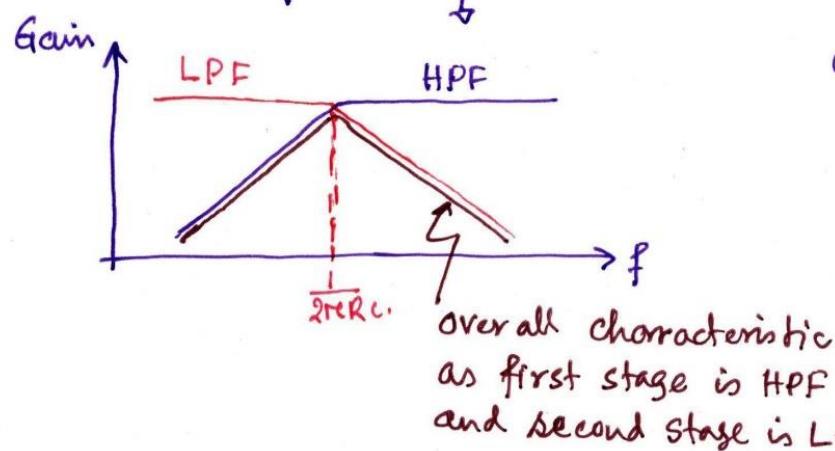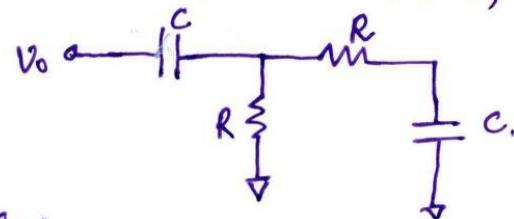

- There is a BPF characteristics from the  $V_o$  and it provides a "positive feedback" at that frequency  $\frac{1}{2\pi RC}$ .
- Increasing  $K$ , will alter the  $\alpha$ -factor.

• Low pass KRC / Sallen-Key filter :-

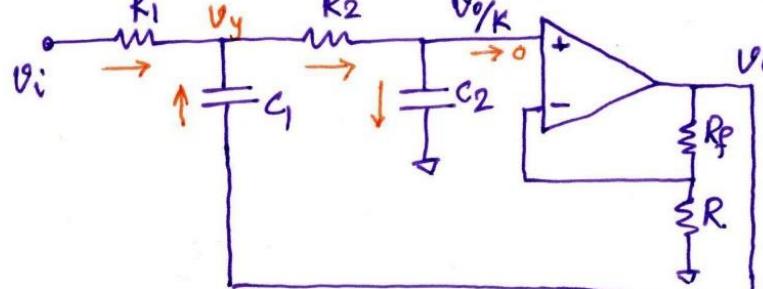

$$K = \left(1 + \frac{R_f}{R}\right)$$

$$\text{Current through } C_2 = \frac{V_o s C_2}{K}$$

$$V_y = \frac{V_o}{K} + \frac{s C_2 V_o}{K} R_2 = \frac{V_o}{K} [1 + s C_2 R_2]$$

Applying KCL at node Vy :-

$$\frac{V_i - V_y}{R_1} + (V_o - V_y) s C_1 = \frac{V_o}{K} s C_2$$

$$\alpha, V_i - \frac{V_o}{K} [1 + s C_2 R_2] + \left[ V_o - \frac{V_o}{K} (1 + s C_2 R_2) \right] s C_1 R_1 = \frac{V_o}{K} s C_2 R_1$$

$$\alpha, \frac{V_o}{V_i} = \frac{K}{s^2 C_1 R_1 C_2 R_2 + s [C_2 R_1 + C_2 R_2 + C_1 R_1 - K C_1 R_1] + 1}$$

$$= \frac{K/C_1 R_1 C_2 R_2}{s^2 + s \frac{C_2 R_1 + C_2 R_2 + C_1 R_1 (1-K)}{C_1 R_1 C_2 R_2} + \frac{1}{C_1 R_1 C_2 R_2}}$$

$$\begin{aligned} \omega_0 &= \frac{1}{\sqrt{C_1 R_1 C_2 R_2}} \\ Q &= \frac{\sqrt{C_1 R_1 C_2 R_2}}{C_2 R_1 + C_2 R_2 + C_1 R_1 (1-K)} \\ &= \frac{1}{\sqrt{\frac{C_2 R_1}{C_1 R_2}} + \sqrt{\frac{C_2 R_2}{C_1 R_1}} + \sqrt{\frac{C_1 R_1}{C_2 R_2}} (1-K)} \end{aligned}$$

Let's assume  $R_1 = R_2, C_1 = C_2$  Equal components.

$$\omega_0 = \frac{1}{R C}$$

$$Q = \frac{1}{2 + 1 - K} = \frac{1}{3 - K}$$

## Low Pass filter (KRC/Sallen-Key) continued :-

$$\omega_0 = \frac{1}{RC}$$



$$Q = \frac{1}{3-K}, \quad \text{where } K = \left(1 + \frac{R_f}{R}\right)$$

Various cases :-

- a) If  $K=1$ ,  $\frac{R_f}{R}=0$ , two passive low pass filters are connected in cascade config.

and op-amp is connected in unity mode,  $Q=0.5$ , poles are real and at same location.

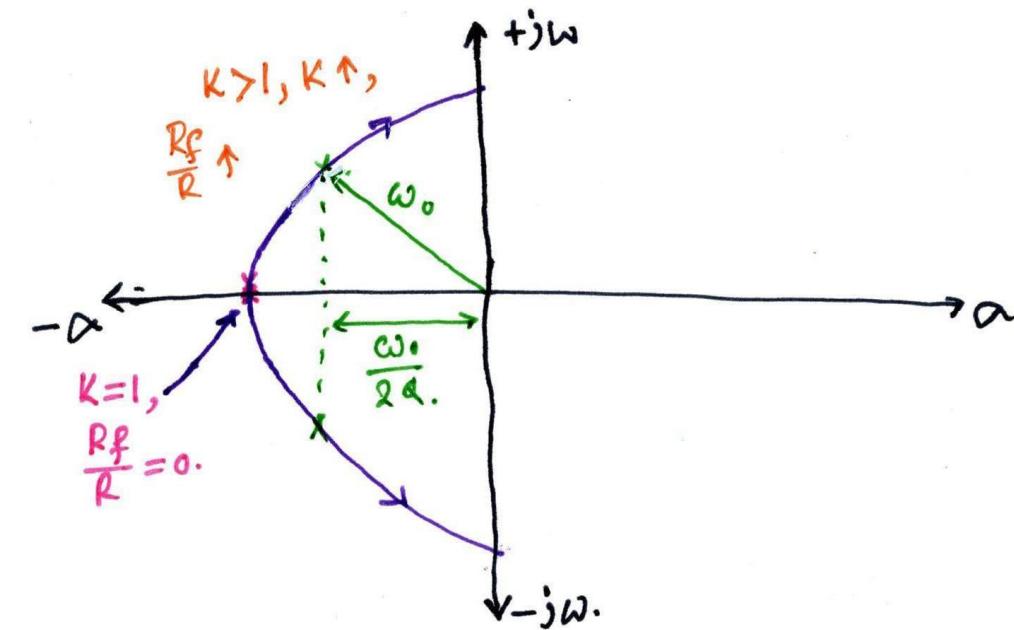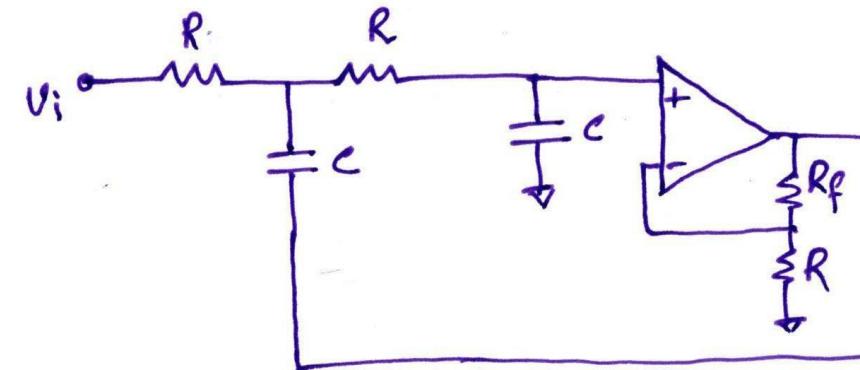- b) For  $K>1$ ,  $Q>0.5$ , poles become complex pair. However,  $\omega_0$  remains unchanged. Filters should offer a more sharp transition.



# EE60032: Analog Signal Processing



**Dr. Ashis Maity**  
**Assistant Professor**

Email: [ashis@ee.iitkgp.ac.in](mailto:ashis@ee.iitkgp.ac.in)  
Department of Electrical Engineering  
Indian Institute of Technology, Kharagpur  
West Bengal, India


## Sensitivity analysis of SK lowpass filter:-

When order of the filter increases, no. of components increases.

Frequency response of analog filter depends on component values.

- In integrated ckt, component values vary with process, voltage, temp (PVT)
- In discrete implementation, component values change with tolerance.

Example :-

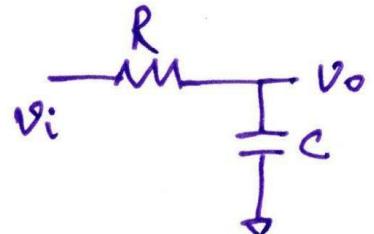

$$\omega_0 = \frac{1}{RC}$$

$$\text{or, } \frac{d\omega_0}{dR} = -\frac{1}{R^2 C}$$

$$\text{or, } \frac{d\omega_0}{\omega_0} = -\frac{dR}{R}$$

If there is a change of +5% in R,  $\omega_0$  varies with -5%.

## Definition of Sensitivity :-

Sensitivity of parameter Y with respect to the component value x is defined

$$\text{as } S_x^Y = \frac{dy/y}{dx/x}$$

Sensitivity substantially higher than unity is undesirable.

## Sensitivity analysis of SK low-pass filter (Continued) :-

$$\omega_0 = \frac{1}{\sqrt{C_1 R_1 C_2 R_2}}$$

or,  $\frac{d\omega_0}{dR_1} = -\frac{1}{2} \frac{1}{R_1 \sqrt{C_1 R_1 C_2 R_2}}$   
 $= -\frac{1}{2} \frac{\omega_0}{R_1}$

or,  $\frac{d\omega_0/dR_1}{dR_1/R_1} = -\frac{1}{2}$

or,  $S_{R_1}^{\omega_0} = -0.5 < 1.$

1% error in  $R_1$  translates in  
-0.5% error in  $\omega_0$ .

$$S_{R_1}^{\omega_0} = S_{R_2}^{\omega_0} = S_{C_1}^{\omega_0} = S_{C_2}^{\omega_0} = -\frac{1}{2}$$

$$\frac{1}{Q} = \sqrt{\frac{C_2 R_1}{C_1 R_2}} + \sqrt{\frac{C_2 R_2}{C_1 R_1}} + \sqrt{\frac{C_1 R_1}{C_2 R_2}} (1-K)$$

or,  $-\frac{dQ}{Q^2} = \frac{dR_1}{2\sqrt{R_1}} \cdot \sqrt{\frac{C_2}{C_1 R_2}} - \frac{dR_1}{2R_1} \sqrt{\frac{C_2 R_2}{C_1 R_1}} + (1-K) \frac{dR_1}{2\sqrt{R_1}} \sqrt{\frac{C_1}{C_2 R_2}}$   
 $= \frac{dR_1}{2R_1} \left[ \sqrt{\frac{R_1 C_2}{C_1 R_2}} - \sqrt{\frac{C_2 R_2}{C_1 R_1}} + (1-K) \sqrt{\frac{R_1 C_1}{R_2 C_2}} \right]$

or,  $S_{R_1}^Q = \frac{dQ/Q}{dR_1/R_1} = -\frac{1}{2} Q \left[ \sqrt{\frac{R_1 C_2}{C_1 R_2}} + \sqrt{\frac{C_2 R_2}{C_1 R_1}} + (1-K) \sqrt{\frac{R_1 C_1}{R_2 C_2}} - 2 \sqrt{\frac{C_2 R_2}{C_1 R_1}} \right]$   
 $= -\frac{1}{2} Q \left[ \frac{1}{Q} - 2 \sqrt{\frac{C_2 R_2}{C_1 R_1}} \right]$   
 $= -\frac{1}{2} + Q \sqrt{\frac{C_2 R_2}{C_1 R_1}}$


Following same procedure, we can have :-

$$S_{R_2}^Q = -S_{R_1}^Q$$

$$S_{C_1}^Q = -S_{C_2}^Q = -\frac{1}{2} + Q \left[ \sqrt{\frac{R_1 C_2}{R_2 C_1}} + \sqrt{\frac{R_2 C_2}{R_1 C_1}} \right]$$

$$S_K^Q = Q K \sqrt{\frac{R_1 C_1}{R_2 C_2}}$$

High pass KRC/Sallen-Key filter :-

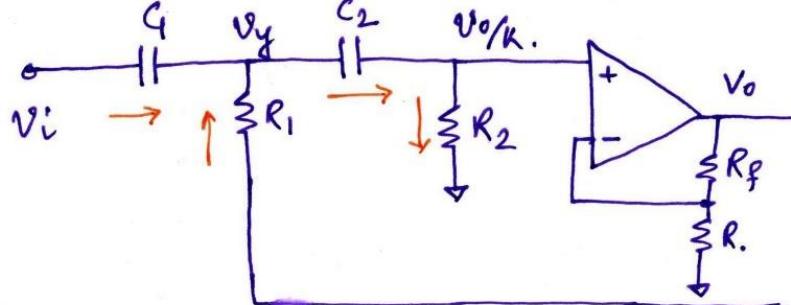

$$V_Y = \frac{V_o}{K} + \frac{V_o}{KR_2} \times \frac{1}{SC_2}$$

$$= \frac{V_o}{K} \left[ \frac{1 + SC_2 R_2}{SC_2 R_2} \right].$$

Applying KCL at  $V_Y$  :-

$$(V_i - V_Y) S C_1 + \frac{V_o - V_Y}{R_1} = \frac{V_o}{KR_2}.$$

$$\text{or, } S C_1 \left[ V_i - \frac{V_o}{K} \left\{ \frac{1 + SC_2 R_2}{SC_2 R_2} \right\} \right] + \frac{1}{R_1} \left[ V_o - \frac{V_o}{K} \left( \frac{1 + SC_2 R_2}{SC_2 R_2} \right) \right] = \frac{V_o}{KR_2}$$


$$\text{or, } \frac{V_o}{V_i} = \frac{K \delta^2 G C_2 R_1 R_2}{G C_2 R_1 R_2 \left[ \delta^2 + \frac{\delta \{ G R_1 + C_2 R_1 + (1-K) G R_2 \}}{G C_2 R_1 R_2} + \frac{1}{G C_2 R_1 R_2} \right]}$$

$$= \frac{\delta^2 + \frac{\delta \{ G R_1 + C_2 R_1 + (1-K) G R_2 \}}{G C_2 R_1 R_2} + \frac{1}{G C_2 R_1 R_2}}{G C_2 R_1 R_2}$$

$$\omega_0 = \frac{1}{\sqrt{G C_2 R_1 R_2}} \quad ; \quad Q = \frac{1}{\sqrt{\frac{G R_1}{G R_2}} + \sqrt{\frac{G R_2}{G R_1}} + \sqrt{\frac{G R_1}{G R_2}} (1-K)}.$$

$$\text{If } R_1 = R_2 = R, \quad G = C_2 = C, \quad \omega_0 = \frac{1}{RC}, \quad Q = \frac{1}{3-K}.$$

## KRC/Sallen Key band-pass filter :-

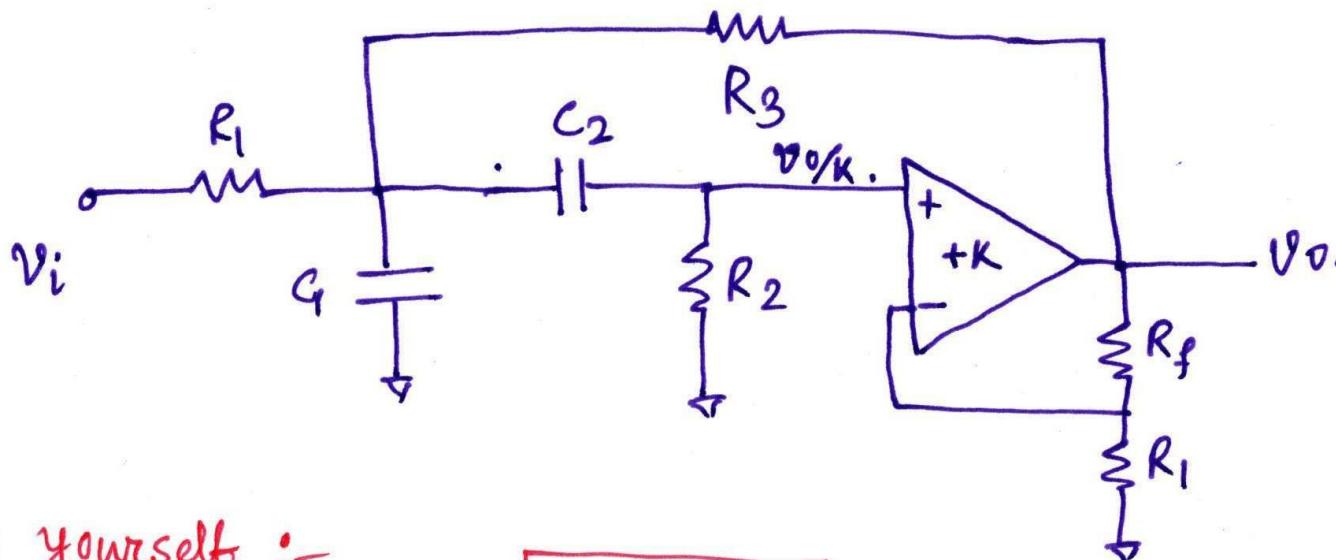

Try yourself :-

$$\omega_0 = \sqrt{\frac{1 + R_1/R_3}{G R_1 C_2 R_2}}$$

$$\alpha = \frac{\sqrt{1 + R_1/R_3}}{\left[1 + (1-K)\frac{R_1}{R_3}\right] \sqrt{\frac{R_2 C_2}{R_1 G}} + \sqrt{\frac{R_1 C_2}{R_2 G}} + \sqrt{\frac{R_1 G}{R_2 C_2}}}.$$

Problem :- Determine the Q-sensitivity of the <sup>LPF</sup> SK filter for the common choice  $R_1 = R_2$ , and  $C_1 = C_2$ .

$$Q = \frac{1}{3-K}$$

$$S_{R1}^Q = -S_{R2}^Q = -\frac{1}{2} + Q = -\frac{1}{2} + \frac{1}{3-K} \rightarrow [S_{R1}^Q = -S_{R2}^Q = -\frac{1}{2} + Q \sqrt{\frac{R_2 C_2}{R_1 C_1}}]$$

$$S_{C1}^Q = -S_{C2}^Q = -\frac{1}{2} + \frac{2}{3-K} \rightarrow [S_{C1}^Q = -S_{C2}^Q = -\frac{1}{2} + Q \left( \sqrt{\frac{R_1 C_2}{R_2 C_1}} + \sqrt{\frac{R_2 C_2}{R_1 C_1}} \right)]$$

$$S_K^Q = QK \sqrt{\frac{R_1 C_1}{R_2 C_2}} = QK = \frac{K}{3-K}$$

If  $K=1$ , then  $|S_{C1}^Q| = |S_{C2}^Q| = |S_K^Q| = \frac{1}{2}$  provides low sensitivity, but limited Q

Advantage of KRC/Sallen-key filter:-

a) Simple structure, only one op-amp is used.

Disadvantage of KRC/Sallen-key filter:-

a) limited Q value.

b) Sensitivity is not good,

# EE60032: Analog Signal Processing



**Dr. Ashis Maity**  
**Assistant Professor**

Email: [ashis@ee.iitkgp.ac.in](mailto:ashis@ee.iitkgp.ac.in)  
Department of Electrical Engineering  
Indian Institute of Technology, Kharagpur  
West Bengal, India

 KHN / State variable filter :- Also known as universal filter

Invented by Kerwin, Huelsman and Newcomb in 1967.

Basic principle : Realize biquadratic transfer function by means of integrators.


Generalized transfer function of a HPF :  $\frac{V_o}{V_i}(s) = \frac{\alpha s^2}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$ .

$$\Rightarrow V_o(s) \left[ 1 + \frac{\omega_0}{Qs} + \frac{\omega_0^2}{s^2} \right] = \alpha V_i(s)$$


$$\Rightarrow V_o(s) = \alpha V_i(s) - \frac{\omega_0}{Qs} V_o(s) - \frac{\omega_0^2}{s^2} V_o(s)$$

Observations :-

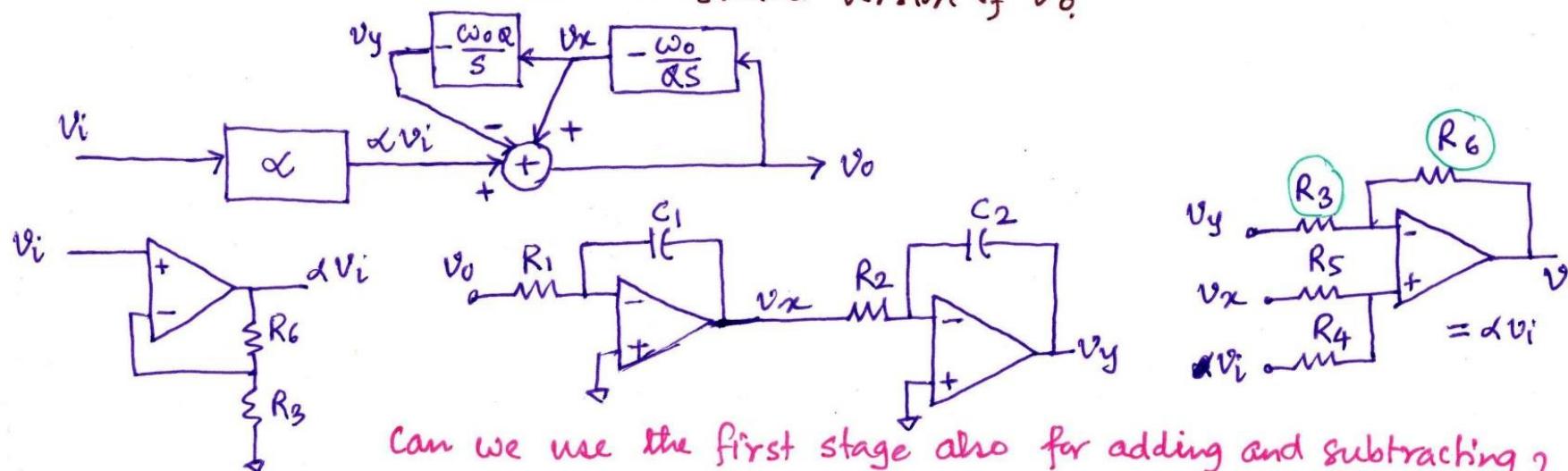- a)  $V_o(s)$  can be generated by summing three terms.
- b) First term is the scaled version of  $V_i$ .
- c) Second term is the integrated version of  $V_o$ .
- d) Third term is the double integrated version of  $V_o$ .


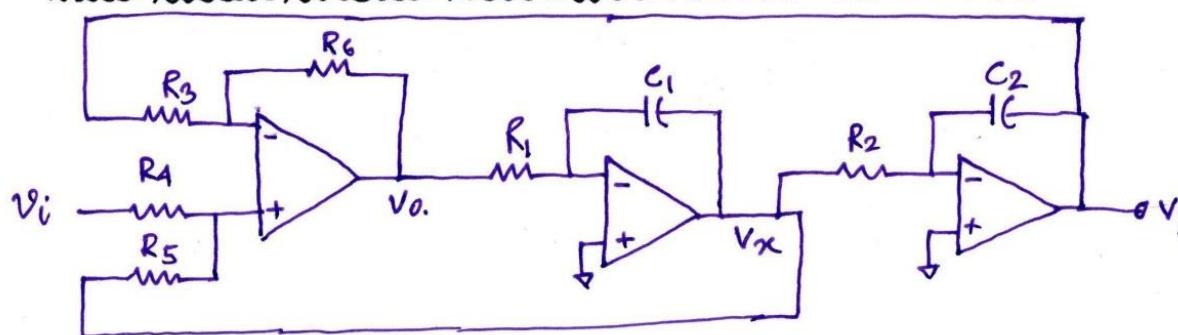
## Overall implementation of KHN/state variable filter:-



$$V_x = -\frac{V_o}{R_1 G s}$$

$$V_y = -\frac{V_x}{R_2 C_2 s} = \frac{V_o}{R_1 R_2 G C_2 s^2}$$

Using voltage superposition, we can calculate  $V_o$ .

$$\begin{aligned} V_o &= \left(1 + \frac{R_6}{R_3}\right) \frac{R_5}{R_4 + R_5} \cdot V_i + \left(1 + \frac{R_6}{R_3}\right) \frac{R_4}{R_4 + R_5} V_x - \frac{R_6}{R_3} \cdot V_y \\ &= \left(1 + \frac{R_6}{R_3}\right) \frac{R_5}{R_4 + R_5} V_i - \left(1 + \frac{R_6}{R_3}\right) \frac{R_4}{R_4 + R_5} \cdot \frac{V_o}{R_1 G s} + \frac{R_6}{R_3} \cdot \frac{V_o}{R_1 R_2 G C_2 s^2} \end{aligned}$$

$$\text{or, } \frac{V_o}{V_i}(s) = \frac{\left(1 + \frac{R_6}{R_3}\right) \frac{R_5}{R_4 + R_5} s^2}{s^2 + \frac{R_4}{R_5 + R_4} \left(1 + \frac{R_6}{R_3}\right) \frac{s}{R_1 G} + \frac{R_6}{R_1 R_2 R_3 G C_2}} \quad \langle \text{HPF} \rangle$$

$$\alpha = \left(1 + \frac{R_6}{R_3}\right) \frac{R_5}{R_4 + R_5}, \quad \omega_0 = \sqrt{\frac{R_6}{R_1 R_2 R_3 G C_2}}, \quad Q = \frac{R_5 + R_4}{R_4(R_3 + R_6)} \sqrt{\frac{R_1 G R_3 R_6}{R_2 C_2}}$$

How to get BPF :-

$$\begin{aligned} \frac{V_x}{V_i}(s) &= \frac{V_o}{V_i} \times \frac{V_x}{V_o} = \frac{\alpha s^2}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2} \times \frac{(-1)}{R_1 G s} \\ &= -\frac{8 \frac{\alpha}{R_1 C_1}}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2} \end{aligned}$$

How to get LPF :-

$$\begin{aligned} \frac{V_y}{V_i}(s) &= \frac{V_o}{V_i} \cdot \frac{V_y}{V_o} = \frac{\alpha s^2}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2} \times \frac{1}{R_1 R_2 G C_2 s^2} \\ &= \frac{\alpha / R_1 R_2 C_1 C_2}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2} \end{aligned}$$

Three cascaded stages may raise a concern of stability. Careful design and simulation are required to avoid oscillation.

## Sensitivity analysis of the KHN/state variable filter:-

$$\alpha = \frac{R_5 + R_4}{R_4(R_3 + R_6)} \sqrt{\frac{R_1 G R_3 R_6}{R_2 C_2}}$$

or,  $\frac{d\alpha}{dR_1} = \frac{R_5 + R_4}{R_4(R_3 + R_6)} \cdot \sqrt{\frac{G R_3 R_6}{R_2 C_2}} \cdot \frac{1}{2\sqrt{R_1}}$   
 $= \frac{\alpha}{2R_1}$

or,  $\frac{d\alpha/\alpha}{dR_1/R_1} = \frac{1}{2} = S_{R_1}^{\alpha}$

Similarly,  $S_{C_2}^{\alpha} = \frac{1}{2}$ .

$$\frac{d\alpha}{dR_2} = -\frac{R_5 + R_4}{R_4(R_3 + R_6)} \sqrt{\frac{R_1 G R_3 R_6}{C_2}} \cdot \frac{1}{2R_2\sqrt{R_2}}$$
  
 $= -\frac{\alpha}{2R_2}$

$S_{R_2}^{\alpha} = \frac{d\alpha/\alpha}{dR_2/R_2} = -\frac{1}{2}$ .

Similarly,  $S_{C_1}^{\alpha} = -\frac{1}{2}$

$$|S_{R_1, R_2, C_1, C_2}^{\alpha}| = \frac{1}{2}$$

$$\frac{d\alpha}{dR_5} = \frac{1}{R_4(R_3 + R_6)} \cdot \sqrt{\frac{R_1 G R_3 R_6}{R_2 C_2}} = \frac{\alpha}{R_5 + R_4}$$

or,  $\frac{d\alpha/\alpha}{dR_5/R_5} = \frac{R_5}{R_5 + R_4} < 1$ .

or,  $S_{R_5}^{\alpha} = \frac{R_5}{R_5 + R_4} < 1$ .

$$\alpha = \frac{R_5}{R_4(R_3 + R_6)} \sqrt{\frac{R_1 G R_3 R_6}{R_2 C_2}} + \frac{1}{(R_3 + R_6)} \sqrt{\frac{R_1 G R_3 R_6}{R_2 C_2}}$$

or,  $\frac{d\alpha}{dR_4} = -\frac{R_5}{R_4^2(R_3 + R_6)} \sqrt{\frac{R_1 G R_3 R_6}{R_2 C_2}} = -\frac{\alpha R_5}{R_4(R_5 + R_4)}$

or,  $\frac{d\alpha/\alpha}{dR_4/R_4} = -\frac{R_5}{R_5 + R_4}$  (Ans).

or,  $S_{R_4}^{\alpha} = -\frac{R_5}{R_5 + R_4}$ .

or,  $|S_{R_4}^{\alpha}| < 1$ .

## Sensitivity analysis of KHN/state variable filter :- (Continued)

$$\alpha = \frac{R_5 + R_4}{R_4(R_3 + R_6)} \sqrt{\frac{R_1 C_1 R_3 R_6}{R_2 C_2}}$$

$$\begin{aligned} \frac{d\alpha}{dR_3} &= \frac{R_5 + R_4}{R_4(R_3 + R_6)} \cdot \frac{1}{2\sqrt{R_3}} \sqrt{\frac{R_1 C_1 R_6}{R_2 C_2}} - \frac{R_5 + R_4}{R_4(R_3 + R_6)^2} \cdot \sqrt{\frac{R_1 C_1 R_3 R_6}{R_2 C_2}} \\ &= \frac{\alpha}{2R_3} - \frac{\alpha}{R_3 + R_6} = \alpha \left[ \frac{R_6 - R_3}{2R_3(R_3 + R_6)} \right] \end{aligned}$$

$$\frac{d\alpha/\alpha}{dR_3/R_3} = S_{R_3}^\alpha = \frac{R_6 - R_3}{2(R_3 + R_6)}$$

Similarly  $S_{R_6}^\alpha = \frac{R_6 - R_3}{2(R_3 + R_6)}$

If  $R_3 = R_6$ ,  $S_{R_6}^\alpha = S_{R_3}^\alpha = 0$ .

- Advantages :-
- KHN biquads have low sensitivity to the component value.
  - Act as an universal filter.
  - Have more independent control of filter parameters.

- Disadvantages :-
- Three op-amps in the feedback loop, which may give stability issue.
  - More components are required.

# EE60032: Analog Signal Processing




**Dr. Ashis Maity**  
**Assistant Professor**

Email: [ashis@ee.iitkgp.ac.in](mailto:ashis@ee.iitkgp.ac.in)  
Department of Electrical Engineering  
Indian Institute of Technology, Kharagpur  
West Bengal, India
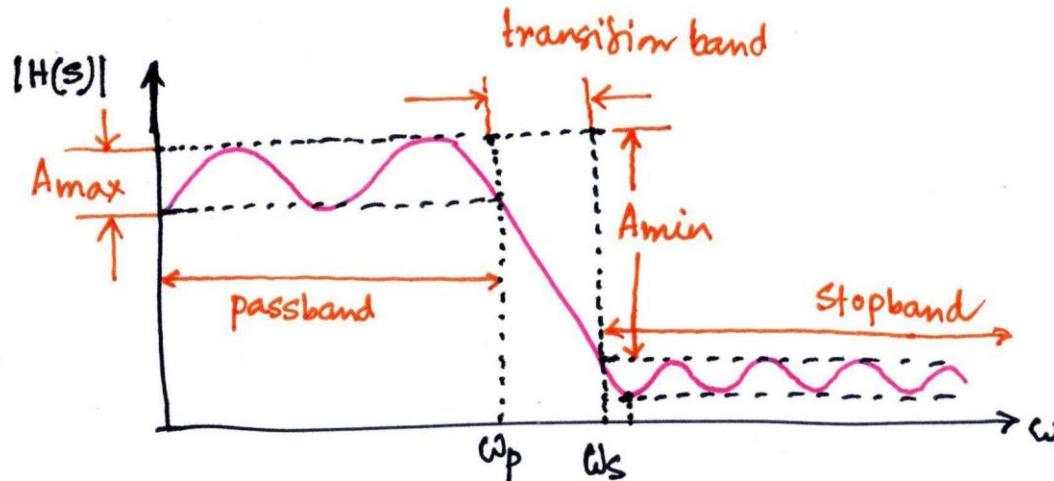
## Approximation of filter functions :-

- Based on the signal and the interference amplitude levels, we decide stopband attenuation.
- Depending on how close the signal frequency and interference freq. We choose the slope of transition band.
- Depending on the nature of desired signal (audio/video), we select tolerance in the passband ripple.



### Basic objective :-

- How to determine order of the filter?
- How to get a desired frequency response?
- How to choose various trade-off?

This tasks are performed using approximation functions.

Although, these approximation functions are applied on low pass filter, they are equally applicable to develop other filter types.

## Butterworth Approximation functions :- (Introduced by S. Butterworth in 1930)

✓ Monotonically decreasing transmission with all transmission zeros at  $\omega \rightarrow \infty$ .

✓ It provides all poles filter.

✓ Nth order Butterworth approximation functions:

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \epsilon^2 \left(\frac{\omega}{\omega_p}\right)^{2N}}}$$

where  $\omega_p$  = passband freq.

$\epsilon$  = determines max. variation  
in pass band.

At  $\omega \ll \omega_p$ ,  $|H(j\omega)| = 1$ .

At  $\omega = \omega_p$ ,  $|H(j\omega_p)| = \frac{1}{\sqrt{1 + \epsilon^2}}$

Maximum variation in passband in dB =  $20 \log \left[ \frac{1}{\sqrt{1 + \epsilon^2}} \right]$  dB


Passband attenuation  $\rightarrow A_{max} = +10 \log(1 + \epsilon^2)$  dB.

Conversely, for given  $A_{max}$ ,  $\epsilon = \sqrt{10 \frac{A_{max}/10 - 1}{10}}$

At  $\omega = \omega_s$ ,  $|H(j\omega_s)| = \frac{1}{\sqrt{1 + \epsilon^2 \left(\frac{\omega_s}{\omega_p}\right)^{2N}}}$

Gain  $\rightarrow |H(j\omega_s)|_{dB} = -10 \log \left[ 1 + \epsilon^2 \left( \frac{\omega_s}{\omega_p} \right)^{2N} \right]$ .

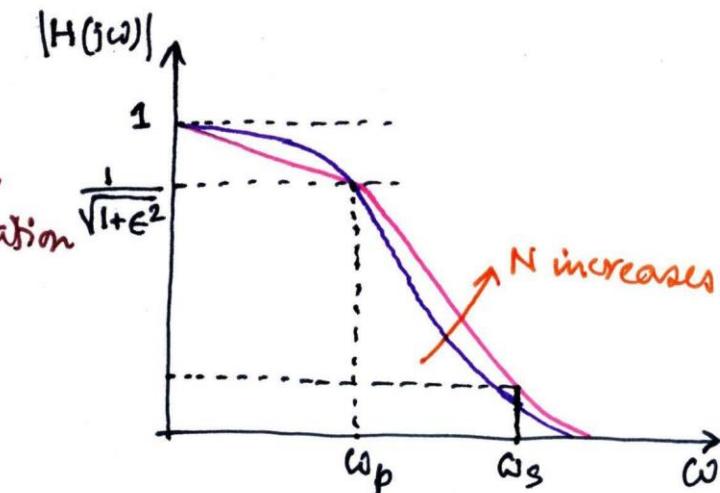
Attenuation  $\rightarrow = 10 \log \left[ 1 + \epsilon^2 \left( \frac{\omega_s}{\omega_p} \right)^{2N} \right] \geq A_{min} \rightarrow$  provides required order N.



- provides a flat response in passband.
- Degree of flatness increases as N increases.
- Provides maximally flat response.
- As N increases, the attenuation also increases in stopband.
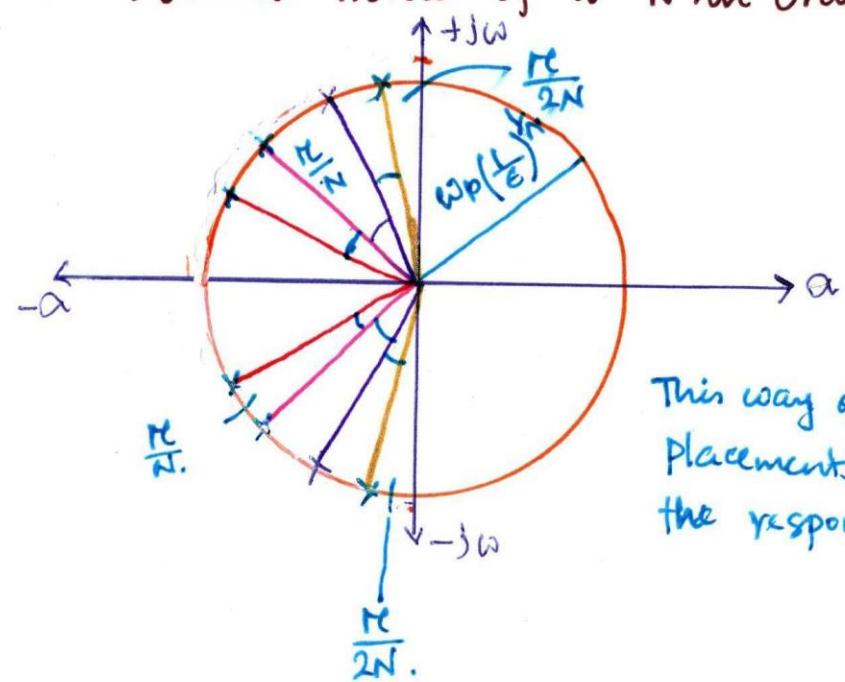
## ④ Butterworth Approximation functions (Continued) :-

The natural modes of an  $N$ th order Butterworth filter can be determined graphically.



This way of pole placements optimizes the response.

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \epsilon^2 \left(\frac{\omega}{\omega_p}\right)^{2N}}} = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_p(\frac{1}{\epsilon})^{1/N}}\right)^{2N}}}$$

$$\omega_0 = \omega_p \left(\frac{1}{\epsilon}\right)^{1/N}.$$




$$\omega_{p1,2} = -\omega_0 [\cos \theta \pm j \sin \theta]$$

$$\omega_{p3,4} = \dots$$

$$H(j\omega) = \frac{K \omega_0}{(s + \omega_{p1})(s + \omega_{p2}) \dots (s + \omega_{pn})}^N$$

$K$  = constant gain

Few examples :-

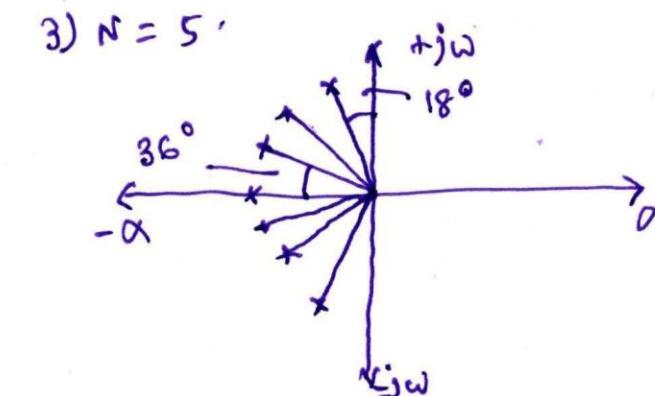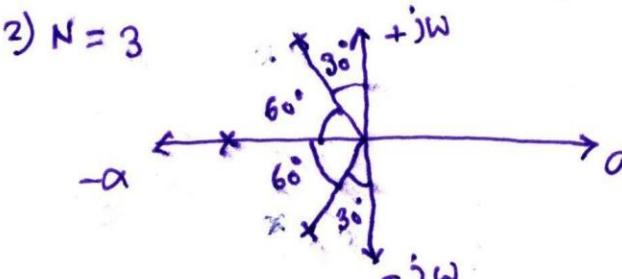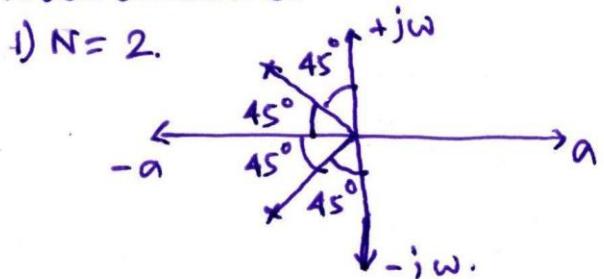

Example :- Find the Butterworth transfer function that meets the following low pass filter specifications:  $f_p = 10 \text{ kHz}$ ,  $A_{\max} = 1 \text{ dB}$ ,  $f_s = 15 \text{ kHz}$ ,  $A_{\min} = 25 \text{ dB}$ , degain  $K=1$ .

$$A_{\max} = 10 \log(1 + \epsilon^2) = 1.$$

$$\text{or, } \log(1 + \epsilon^2) = 0.1 \Rightarrow \epsilon = 0.5088$$

$$A_{\min} = 10 \log \left[ 1 + \epsilon^2 \left( \frac{\omega_s}{\omega_p} \right)^{2N} \right] = 25.$$

$$\text{or, } \log \left[ 1 + \epsilon^2 \left( \frac{\omega_s}{\omega_p} \right)^{2N} \right] = 2.5.$$

$$\text{or, } 1 + \epsilon^2 \left( \frac{\omega_s}{\omega_p} \right)^{2N} = 10^{2.5} = 316.22$$

$$\text{or, } \epsilon^2 \left( \frac{\omega_s}{\omega_p} \right)^{2N} = 315.22.$$

$$\text{or, } \left( \frac{\omega_s}{\omega_p} \right)^{2N} = 1217.7$$

$$\text{or, } (1.5)^{2N} = 1217.7$$


$$\text{For } N=8, (1.5)^{16} = 656.8$$

$$\text{For } N=9, (1.5)^{18} = 1477.9.$$

$$\text{So, } \boxed{N \approx 9.}$$

$$H(s) = \frac{\omega_0^9}{(s + \omega_0)(s + \omega_1)(s + \omega_2) \dots (s + \omega_8)}$$
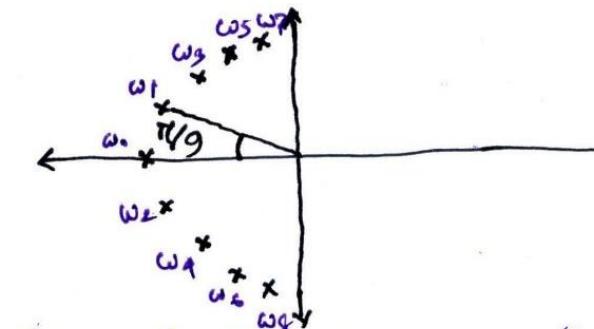
$$\begin{aligned} \omega_0 &= \omega_p \left( \frac{1}{\epsilon} \right)^{1/N} \\ &= 2\pi \cdot f_p \left( \frac{1}{\epsilon} \right)^{1/N} \\ &= 2\pi \cdot 10 \times 10^3 \left( \frac{1}{0.5088} \right)^{1/9} \\ &= 6.733 \times 10^4 \text{ rad/s.} \end{aligned}$$



One real pole  $\omega_0 = 6.733 \times 10^4 \text{ rad/s.}$

$$\omega_{1,2} = \omega_0 (\cos 20^\circ \pm j \sin 20^\circ)$$

$$\omega_{3,4} = \omega_0 (\cos 40^\circ \pm j \sin 40^\circ)$$

$$\omega_{5,6} = \omega_0 (\cos 60^\circ \pm j \sin 60^\circ)$$

$$\omega_{7,8} = \omega_0 (\cos 80^\circ \pm j \sin 80^\circ)$$

# EE60032: Analog Signal Processing



**Dr. Ashis Maity**  
**Assistant Professor**

Email: [ashis@ee.iitkgp.ac.in](mailto:ashis@ee.iitkgp.ac.in)  
Department of Electrical Engineering  
Indian Institute of Technology, Kharagpur  
West Bengal, India

## The Chebyshov Approximation function :- (P. L. Chebyshov introduced in 1899)

- \* Exhibits an equiripple response in passband.
- \* Monotonically decreasing transmission in stopband.

The magnitude response of a Chebyshov filter is.

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \epsilon^2 \cos^2 \left\{ N \cosh^{-1} \left( \frac{\omega}{\omega_p} \right) \right\}}} \quad \text{for } \omega \leq \omega_p$$

and

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \epsilon^2 \cosh^2 \left\{ N \cosh^{-1} \left( \frac{\omega}{\omega_p} \right) \right\}}} \quad \text{for } \omega > \omega_p$$

At passband,  $\omega = \omega_p$

$$|H(j\omega_p)| = \frac{1}{\sqrt{1 + \epsilon^2}}$$

Same as Butterworth fn.

$$A_{max} = 10 \log (1 + \epsilon^2) \Rightarrow \epsilon = \sqrt{10^{A_{max}/10} - 1}$$

Overall filter transfer fn.  $H(s) =$

$$\frac{\omega_p^N}{\epsilon^{2^{N-1}} (s + \omega_1)(s + \omega_2) \dots (s + \omega_n)}$$

At stopband,  $\omega = \omega_s$ .

$$|H(j\omega_s)| = 10 \log \left[ 1 + \epsilon^2 \cosh^2 \left\{ N \cosh^{-1} \left( \frac{\omega_s}{\omega_p} \right) \right\} \right]$$

Order of the filter will be decided based on the attenuation requirement in the stopband.


The poles of the Chebyshov filter :-

$$\omega_k = -\omega_p \sin \left[ \frac{2k-1}{N} \cdot \frac{\pi}{2} \right] \sinh \left[ \frac{1}{N} \cdot \sinh^{-1} \frac{1}{\epsilon} \right]$$


$$+ j \omega_p \cos \left[ \frac{2k-1}{N} \cdot \frac{\pi}{2} \right] \cosh \left[ \frac{1}{N} \cdot \sinh^{-1} \frac{1}{\epsilon} \right]$$

where  $k = 1, 2, 3, \dots, N$ .
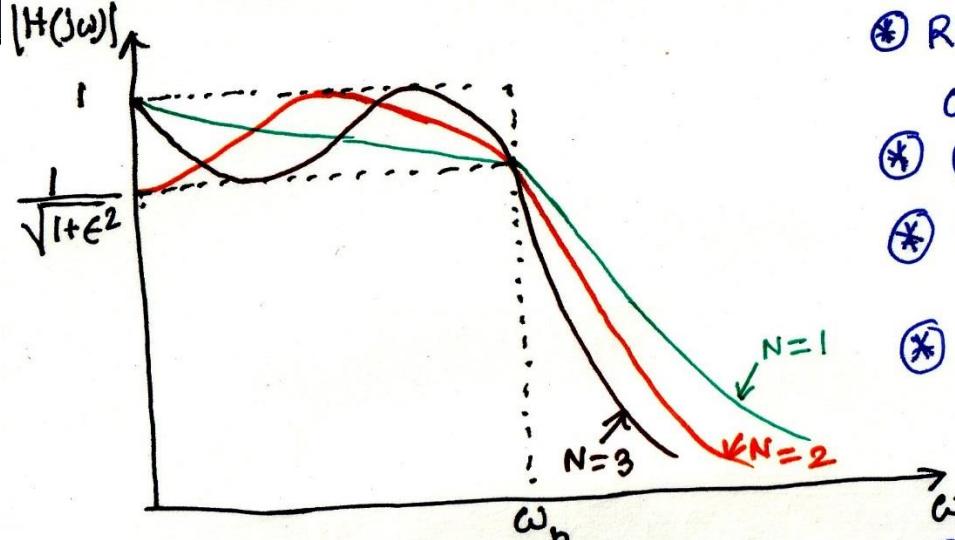
## The Chebyshev Approximation function (Continued)



- \* Ripples confined in a band, does not change with order.
- \* Odd order provides  $|H(0)| = 1$ .
- \* Even order provides  $|H(0)| = \frac{1}{\sqrt{1+\epsilon^2}}$ , max. deviatn at  $\omega_0$ .
- \* Total no. of passband maxima and minima equals to the order of the filter  $N$ .
- \* All zeros are placed at  $\infty$ , all pole filter.

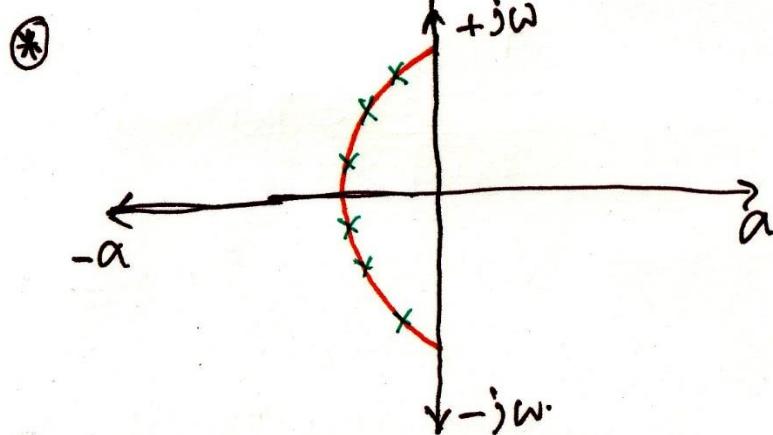

Here, poles move in elliptical path

(In Butterworth, poles move in circular path)

- \* Chebyshev provides a better approximation than the Butterworth fn.
- \* Chebyshev provides a greater stopband attenuation than the Butterworth filter if their order are same.
- \* For same attenuation in stopband, Chebyshev requires lower order than the Butterworth fn.

Problems :- Find the Chebyshov approximation functions that meets the low-pass filter specifications :  $f_p = 10 \text{ kHz}$ ,  $A_{\max} = 1 \text{ dB}$ ,  $f_s = 15 \text{ kHz}$ ,  $A_{\min} = 25 \text{ dB}$ , dc gain = 1.

$$\epsilon = \sqrt{10^{A_{\max}/10} - 1} = \sqrt{10^{10} - 1} = 0.5088.$$

At stopband  $\omega = \omega_s$ ,

$$|H(i\omega_s)| = 10 \log \left[ 1 + \epsilon^2 \cosh^2 \left\{ N \cosh^{-1} \left( \frac{\omega_s}{\omega_p} \right) \right\} \right] = 25.$$

$$\text{or, } 10 \log \left[ 1 + (0.5088)^2 \cosh^2 \left\{ N \cosh^{-1}(1.5) \right\} \right] = 25.$$

$$\text{or, } \log \left[ 1 + 0.2589 \cosh^2 \left\{ N \times 0.9624 \right\} \right] = 2.5.$$

$$\text{or, } \cosh^2 \left\{ N \times 0.9624 \right\} = 1217.565.$$

$$N = 4.411$$

The required order of the Chebyshov fn. will be 5 (nearest higher integer).

For same attenuation, the order of Butterworth fn. was 9. Whereas in Chebyshov approximation, the order becomes 5 at the expense of equiripple.

$$\omega_k = -\omega_p \sin \left[ \frac{2k-1}{N} \cdot \frac{\pi}{2} \right] \sinh \left[ \frac{1}{N} \sinh^{-1} \left( \frac{1}{\epsilon} \right) \right] + j \omega_p \cos \left[ \frac{2k-1}{N} \cdot \frac{\pi}{2} \right] \cosh \left[ \frac{1}{N} \cosh^{-1} \left( \frac{1}{\epsilon} \right) \right].$$

$$\text{For } k=1, \quad \frac{2k-1}{N} \cdot \frac{\pi}{2} = \frac{1}{5} \cdot \frac{\pi}{2}, \quad \text{For } k=5, \quad \frac{2k-1}{N} \cdot \frac{\pi}{2} = \frac{9}{5} \times \frac{\pi}{2} = \pi - \frac{1}{5} \pi/2$$

$$\omega_{p1} = \omega_p [-0.0893 + j 0.9833] \quad \text{and} \quad \omega_{p5} = \omega_p [-0.0893 - j 0.9833]$$

$$\omega_{p2} = \omega_p [-0.2342 + j 0.6199] \quad \text{and} \quad \omega_{p4} = \omega_p [-0.2342 - j 0.6199]$$

$$\omega_{p3} = -\omega_p \times 0.289 \quad \text{as} \quad \frac{2k-1}{N} \cdot \frac{\pi}{2} = \pi/2$$

Q Problem :- A low pass filter must provide a passband flatness of 0.45 dB for  $f_p = 1 \text{ MHz}$  and a stopband attenuation of 9 dB at  $f_s = 2 \text{ MHz}$ . Determine the order of the Butterworth approximation satisfying these requirements. Using a Sallen-Key topology as core, design the Butterworth approximation fns.

$$\epsilon = \sqrt{10^{\frac{A_{\max} - 1}{10}} - 1} = \sqrt{10^{0.045} - 1} = 0.3303.$$

$$10 \log \left[ 1 + \epsilon^2 \left( \frac{\omega_s}{\omega_p} \right)^{2N} \right] = A_{\min}$$

$$\text{or, } \log \left[ 1 + (0.3303)^2 (2)^{2N} \right] = 0.9.$$

$$\text{or, } (2)^{2N} = 63.64$$

$$\text{or, } 4^N = 63.64 \quad 4^3 = 64.$$



$$\text{or, } N \approx 3.$$

Minimum 3rd order filter is required.

1 real pole and one complex pole pair.

$$\begin{aligned} \omega_0 &= \frac{\omega_p}{\epsilon^N} = \frac{2\pi \cdot f_p}{\epsilon^N} = \frac{2\pi \times 1 \text{ Hz}}{(0.3303)^{1/3}} \\ &= 2\pi (1.45 \text{ MHz}) \end{aligned}$$

$$f_0 = 1.45 \text{ MHz.}$$

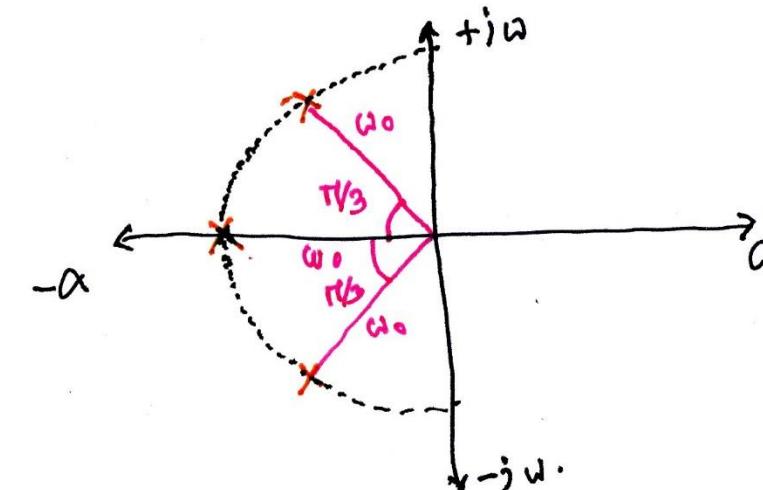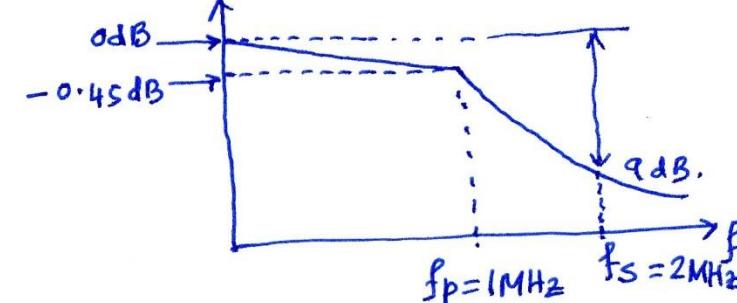

# EE60032: Analog Signal Processing



**Dr. Ashis Maity**  
**Assistant Professor**

Email: [ashis@ee.iitkgp.ac.in](mailto:ashis@ee.iitkgp.ac.in)  
Department of Electrical Engineering  
Indian Institute of Technology, Kharagpur  
West Bengal, India

Q Problem :- A low pass filter must provide a passband flatness of 0.45 dB for  $f_p = 1 \text{ MHz}$  and a stopband attenuation of 9 dB at  $f_s = 2 \text{ MHz}$ . Determine the order of the Butterworth approximation satisfying these requirements. Using a Sallen-Key topology as core, design the Butterworth approximation fns.

$$\epsilon = \sqrt{10^{\frac{A_{\max} - 1}{10}} - 1} = \sqrt{10^{0.045} - 1} = 0.3303.$$

$$10 \log \left[ 1 + \epsilon^2 \left( \frac{\omega_s}{\omega_p} \right)^{2N} \right] = A_{\min}$$

$$\text{or, } \log \left[ 1 + (0.3303)^2 (2)^{2N} \right] = 0.9.$$

$$\text{or, } (2)^{2N} = 63.64$$

$$\text{or, } 4^N = 63.64 \quad 4^3 = 64.$$



$$\text{or, } N \approx 3.$$

Minimum 3rd order filter is required.


1 real pole and one complex pole pair.

$$\begin{aligned} \omega_0 &= \frac{\omega_p}{\epsilon^N} = \frac{2\pi \cdot f_p}{\epsilon^N} = \frac{2\pi \times 1 \text{ Hz}}{(0.3303)^{1/3}} \\ &= 2\pi (1.45 \text{ MHz}) \end{aligned}$$

$$f_0 = 1.45 \text{ MHz.}$$

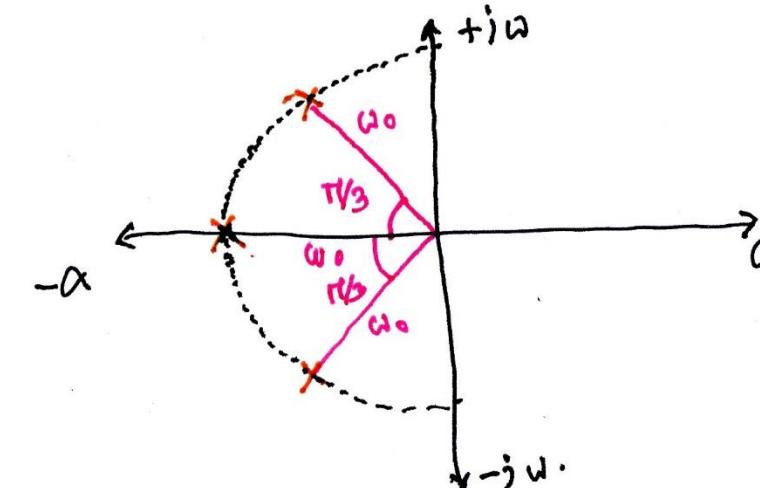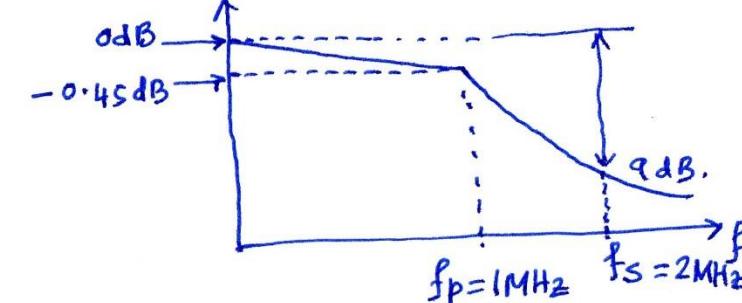

## Sallen-Key filter implementation :-

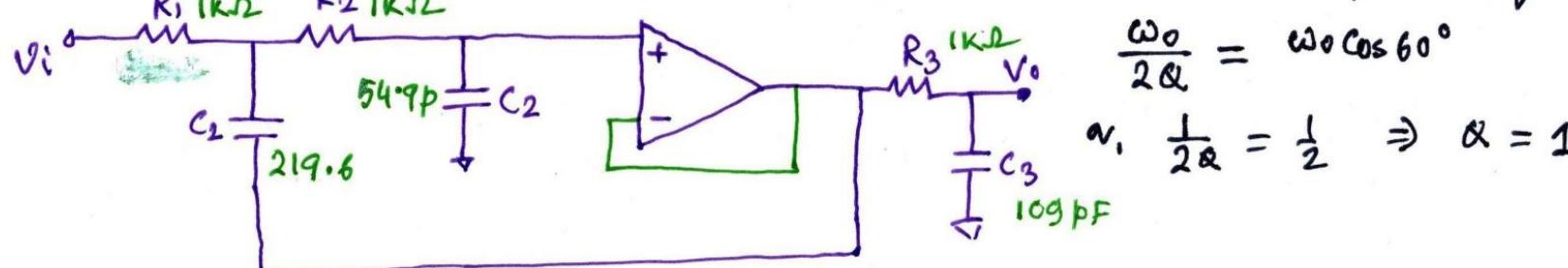

what is the Q-factor required?

$$\frac{\omega_0}{2\alpha} = \omega_0 \cos 60^\circ$$

$$\alpha, \frac{1}{2\alpha} = \frac{1}{2} \Rightarrow \alpha = 1.$$

Different design strategies can be adopted :-

- 1) For equal component choice,  $R_1 = R_2, C_1 = C_2, \alpha = \frac{1}{3-K}$ . If  $K=2, \alpha=1$ . Try yourself.
- 2) For equal resistance choice,  $R_1 = R_2, C_1 \neq C_2, K=1$ .
- 3) For equal capacitance choice,  $C_1 = C_2, R_1 \neq R_2, K=1$ .
- Generalised expression of  $\alpha = \frac{1}{\sqrt{\frac{C_2 R_1}{C_1 R_2}} + \sqrt{\frac{C_2 R_2}{C_1 R_1}} + \sqrt{\frac{C_1 R_1}{C_2 R_2}} (1-K)}$

$$\text{If } K=1, \alpha = \frac{1}{\sqrt{\frac{C_2 R_1}{C_1 R_2}} + \sqrt{\frac{C_2 R_2}{C_1 R_1}}}$$

$$\text{If } R_1 = R_2, \alpha = \frac{1}{2\sqrt{\frac{C_2}{C_1}}} = 1$$

$$\text{or, } \frac{1}{2}\sqrt{\frac{C_1}{C_2}} = 1$$

$$\text{or, } C_1 = 4C_2.$$

$$\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} = \frac{1}{R \sqrt{4C_2^2}} = \frac{1}{2RC_2} = 2\pi \times 1.45 \text{ MHz}$$


$$\text{If } R = 1\text{k}\Omega, C_2 = \frac{1}{2\pi \times 1.45 \text{ MHz} \times 1\text{k}\Omega} = 54.9 \text{ pF}$$

$$Q = 4C_2 = 4 \times 54.9 \text{ pF} = 219.6 \text{ pF.}$$

$$\omega_3 = \frac{1}{R_3 C_3} = 2\pi \times 1.45 \text{ MHz}$$

$$\text{If } R_3 = 1\text{k}\Omega, C_3 = \frac{1}{2\pi \times 1.45 \text{ MHz} \times 1\text{k}\Omega} = 109 \text{ pF.}$$

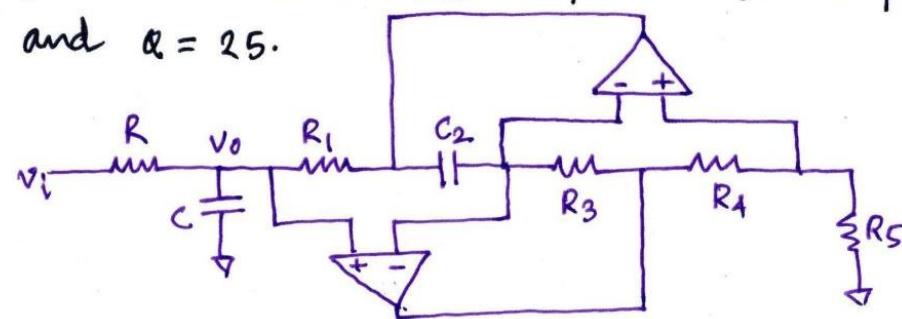Problem: Draw a second order bandpass filter using GIC block. Derive its transfer function. Find out the components values for a band-pass response with  $f_0 = 100$  kHz, and  $\alpha = 25$ .



$$\frac{v_o}{v_i} = H(s) = \frac{s/RC}{s^2 + s/RC + \frac{1}{LC}}$$

$$\frac{\omega_0}{\alpha} = \frac{1}{RC}$$

$$\text{or, } \frac{2\pi \times 100K}{25} = \frac{1}{RC}$$

Assuming  $C = 1 \text{ nF}$ ,  $R = 39.79 \text{ k}\Omega$ .

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow \frac{1}{\sqrt{LC}} = 2\pi(100K)$$

$$\text{or, } \frac{1}{\sqrt{L \cdot 1n}} = 2\pi(100K)$$

$$\text{or, } L = \frac{1}{(2\pi \cdot 100K)^2 \cdot 1n}$$

$$\text{or, } L = \underline{2.533 \text{ mH}}$$

$$SL = \frac{R_1}{1/SC_2} \cdot \frac{R_3}{R_4} \cdot R_5$$

$$= S \frac{C_2 R_1 R_3 R_5}{R_4}$$

$$L = \frac{C_2 R_1 R_3 R_5}{R_4}$$

If  $R_1 = R_3 = R_5 = R_4 = R_x$ ,

$$L = R_x^2 C_2$$

$$L = R_x^2 C_2$$


Assume  $C_2 = 1 \text{ nF}$ .

$$\text{or, } R_x = \sqrt{\frac{L}{C_2}}$$

$$= \sqrt{\frac{2.533}{1n}}$$

$$= \underline{1.592 \text{ k}\Omega}$$

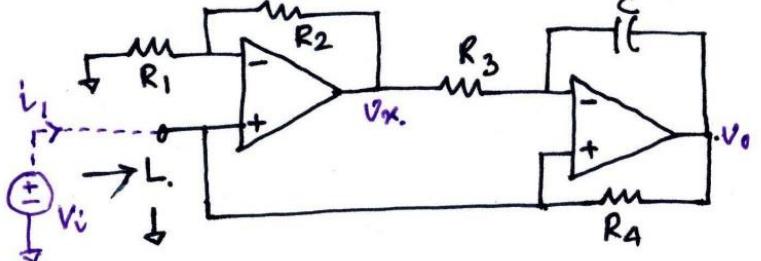Problem :- Show that the following ckt simulates a ground inductance  $L = R_1 R_3 R_4 C / R_2$ .



$$\begin{cases} i_1 = \frac{V_i - V_o}{R_4} \\ \text{or } V_x = \left(1 + \frac{R_2}{R_1}\right)V_i \quad \text{--- (1)} \\ \Rightarrow V_i - V_o = i_1 R_4 \quad \text{--- (2)} \end{cases}$$

$$\frac{V_x - V_i}{R_3} = SC(V_i - V_o)$$

$$\text{or, } \left(1 + \frac{R_2}{R_1}\right)V_i - V_i = R_3 SC \left\{ V_i - V_o \right\}$$

$$\text{or, } \frac{R_2 V_i}{R_1} = R_3 SC V_i - R_3 SC V_o.$$

$$\text{or, } R_3 SC V_o = R_3 SC V_i - \frac{R_2}{R_1} V_i$$

$$\text{or, } (V_i - i_1 R_4) R_3 SC = R_3 SC V_i - \frac{R_2}{R_1} V_i \quad [\text{using (2)}]$$

$$\text{or, } +i_1 R_4 R_3 SC = +\frac{R_2}{R_1} V_i$$


$$\text{or, } \frac{V_i}{i_1} = +\frac{S R_1 R_4 R_3 C}{R_2}$$

$$\text{or, } Z_{in} = S \frac{R_1 R_4 R_3 C}{R_2}$$

$$L = \frac{R_1 R_4 R_3 C}{R_2}$$

## Try Yourself!

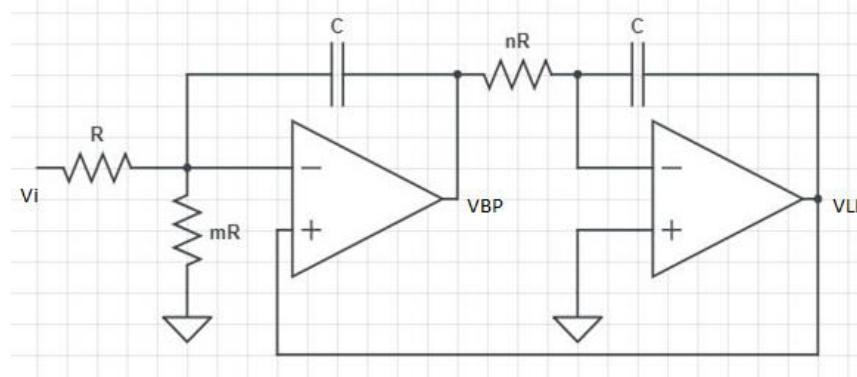1. The simplified state variable filter shown in figure provides the low pass and band pass response using only two op-amps. Derive the overall transfer function  $V_{BP}/V_i$  and  $V_{LP}/V_i$ . Prove that  $Q = \sqrt{n(1+1/m)}$  and  $\omega_o = Q/nRC$ .



2. Design a second order KRC low pass filter with equal component design. Find out the component values to achieve  $f_o = 10$  kHz and  $Q=5$ . Find out the DC gain.

# EE60032: Analog Signal Processing




**Dr. Ashis Maity**  
**Assistant Professor**

Email: [ashis@ee.iitkgp.ac.in](mailto:ashis@ee.iitkgp.ac.in)  
Department of Electrical Engineering  
Indian Institute of Technology, Kharagpur  
West Bengal, India

## Switched Capacitor Filter

- ① Issues of continuous time filter:- Filter parameters are sensitive to parameter variations.
- ② Key features of the switched capacitor filter:-
  - a) Key elements used : switches and capacitor.
  - b) Operates as a discrete time signal processor (without using A/D or D/A converter)
  - c) Filter co-efficients are determined by capacitance ratio, which can be controlled precisely in IC design.
  - d) Provides an accurate frequency response.
  - e) Provides good linearity.
  - f) Provides good dynamic range.
  - g) Analysis is done using Z-transform.
  - h) Very popular in IC design.

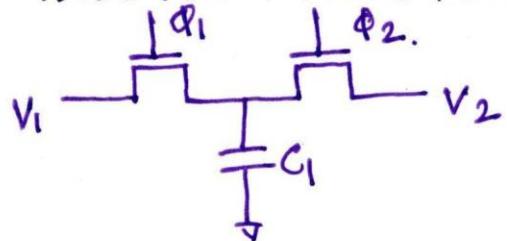
## Basic operation of the switched capacitor ckt:-



Basic formula  $Q = CV$  and charge conservation are used.

$$\text{At } \phi_1 \text{ phase : } Q_1 = C_1 V_1.$$
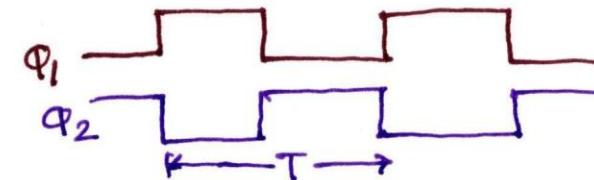
$$\text{At } \phi_2 \text{ phase : } Q_2 = C_1 V_2$$



$$\text{Charge transfer over one clock period : } \Delta Q = C(V_1 - V_2)$$

Charge transfer is repeated in every clock period  $T$ .

$$\text{If } I_{avg} \text{ is the average op current, } I_{avg} \cdot T = C(V_1 - V_2)$$

$$\text{or, } I_{avg} = f_s C(V_1 - V_2) \quad \text{where } f_s = \frac{1}{T}.$$

$$\text{or, } \frac{V_1 - V_2}{I_{avg}} = \frac{1}{f_s C}$$

$$R_{eq} = \frac{1}{f_s C}$$

Example :-

$$f_s = 100 \text{ KHz}, C = 1 \text{ pF}$$

$$R_{eq} = \frac{1}{100 \text{ K} \times 1 \text{ pF}} = 10 \text{ M}\Omega$$

- When  $f_s \uparrow$ , same charge transfer occurs at a faster rate,  $R_{eq} \downarrow$ .

- If  $C_1 \uparrow$ , large amount of charge transfer occurs in each period,  $I_{avg} \uparrow$ ,  $R_{eq} \downarrow$ .


Important to note :- ✓ Resistor approximation assumes the charge transfer per cycle is constant over many cycles. Mimics low frequency behavior.  
✓ For moderate frequency, discrete time analysis is required.

## Different elements of switched capacitor circuits :-

### a) Switch :-

- ✓ Very high resistance in off-state.
- ✓ Very low resistance in on-state, to provide small time constant & high speed operation.
- ✓ No dc offset, otherwise accuracy will be degraded.


### Different options :-

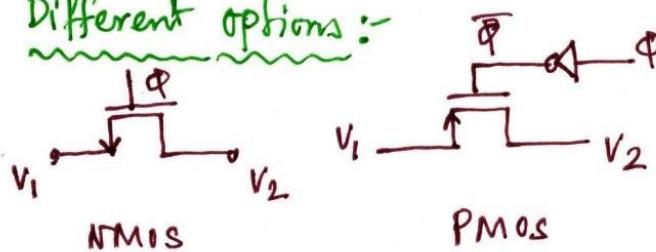

\* NMOS introduces offset when  $V_1 = V_{DD}$

\* PMOS introduces offset when  $V_1 = 0$

### A transmission gate :-

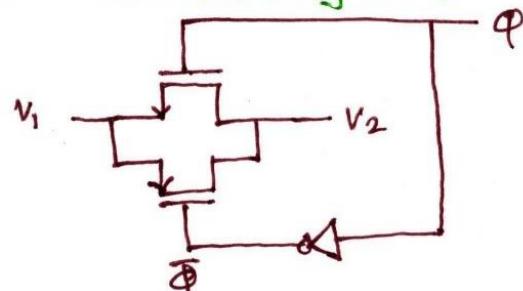


### b) Capacitor :-

Different capacitor options are available in IC.


- ✓ MOS gate capacitance
- ✓ MIM - Cap : Metal-Insulator-Metal.

### Mos gate capacitance :-

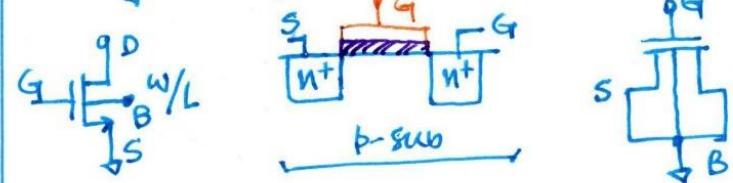


$$C_g = C_{ox} W L$$



### MIM - Capacitance :-

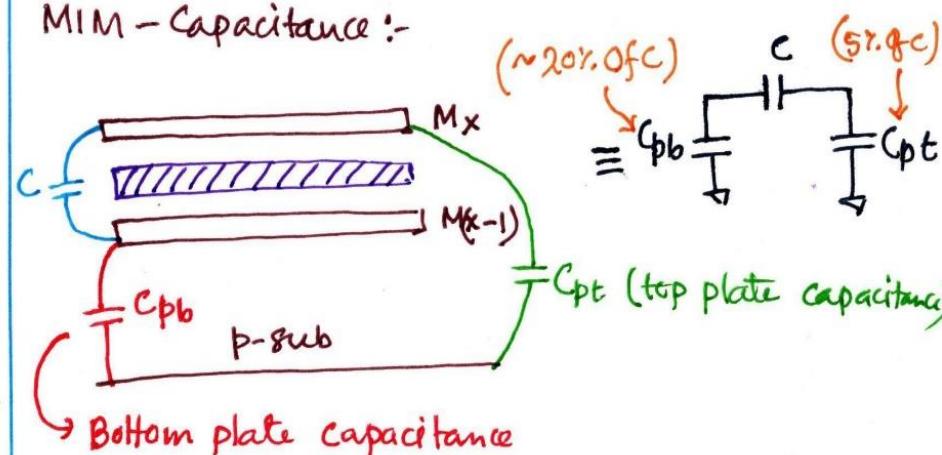
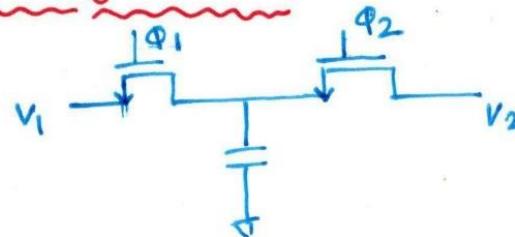
### c) Non-overlapping clock generator :-




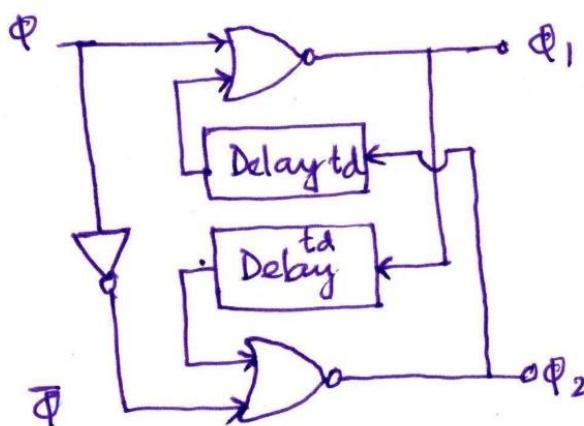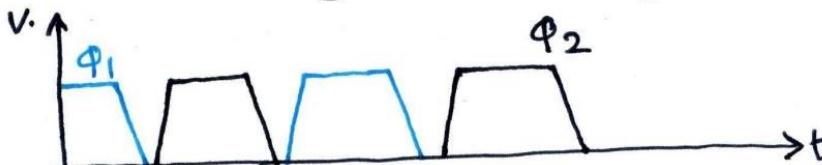- $\phi_1$  and  $\phi_2$  should be non-overlapping clock to guarantee no charge loss.
- Principle used : "Break before Make".
- $\phi_1$  and  $\phi_2$  clock should have same frequency and complementary.
- Non-overlapping means they never be high at same time.



NOR Gate


1	0	0
0	1	0
1	1	0
0	0	1

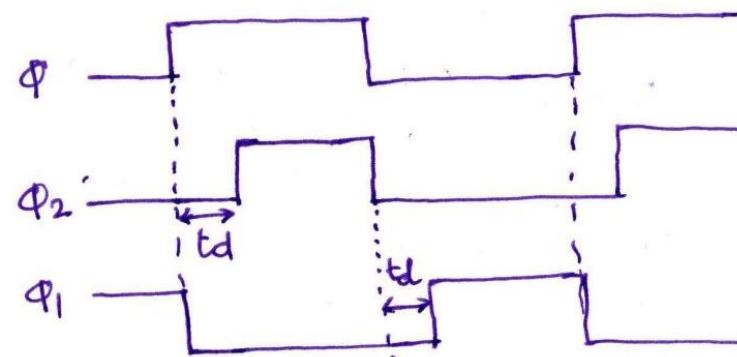
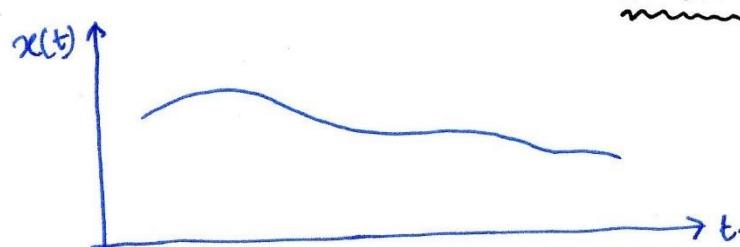
# EE60032: Analog Signal Processing



**Dr. Ashis Maity**  
**Assistant Professor**  
Email: [ashis@ee.iitkgp.ac.in](mailto:ashis@ee.iitkgp.ac.in)  
Department of Electrical Engineering  
Indian Institute of Technology, Kharagpur  
West Bengal, India




Continuous time, continuous amplitude signal.  $x(t)$

Laplace transform

$$X(s) = \int_0^{\infty} e^{-st} x(t) dt.$$

Z-transform

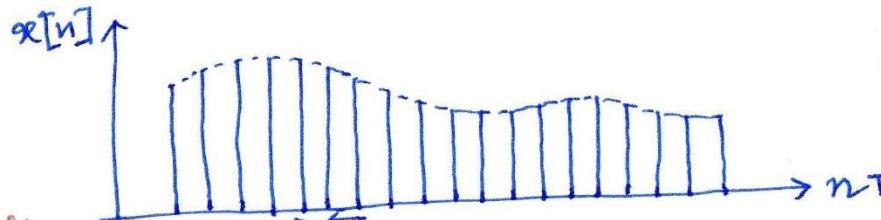

Sampling  
T.

Discrete time, continuous amplitude signal.

$x[n]$

Z-transform.

- Fourier transform of a sequence  $x[n]$ :

$$X(e^{j\omega}) = \sum_{n=-\infty}^{\infty} x[n] e^{-jn\omega}$$

- 2-transform of a sequence  $x[n]$ :

$$X(z) = \sum_{n=-\infty}^{\infty} x[n] z^{-n} \quad \text{where } z = e^{j\omega}.$$

$$x[n] \longleftrightarrow X(z)$$

$$x[n-1] \longleftrightarrow ?$$

$$X(z) = \sum_{n=-\infty}^{\infty} x[n] z^{-n}.$$

$$\text{Let's assume } m = n-1$$

$$n = m+1$$

$$\text{if } n \rightarrow -\infty, m \rightarrow -\infty$$



$$n \rightarrow +\infty, m \rightarrow +\infty$$

$$x[n-1] \longleftrightarrow \sum_{n=-\infty}^{\infty} x[n-1] 2^{-n} = \sum_{m=-\infty}^{\infty} x[m] 2^{-(m+1)}$$

$$= z^{-1} \sum_{m=-\infty}^{\infty} x[m] z^{-m}$$

$$x[n-1] \leftrightarrow z^{-1} X(z)$$

An integrator Circuit :-

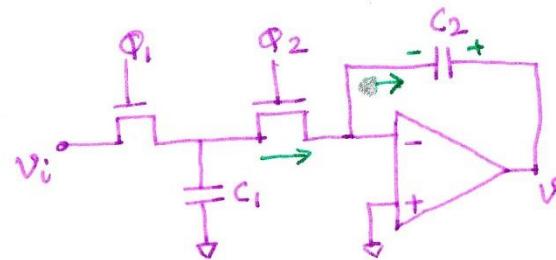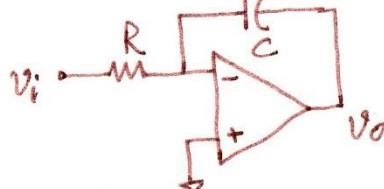

Continuous time integrator

Switched Capacitor integrator.

At  $\Phi_1$  phase : charge stored in  $C_1 = V_i[n-1] C_1$ .

charge stored in  $C_2 = V_o[n-1] C_2$ .

At  $\Phi_2$  phase :  $C_1$  and  $C_2$  both are loosing charges.

Final charge stored in  $C_2 = V_o[n-\frac{1}{2}] C_2$ .

Charge transferred =  $V_o[n-1] C_2 - V_o[n-\frac{1}{2}] C_2$ .

Charge conservation:  $V_o[n-1] C_2 - V_o[n-\frac{1}{2}] C_2 = -V_i[n-1] C_1$ .

$$\text{Or, } V_o[n-\frac{1}{2}] C_2 = V_o[n-1] C_2 - V_i[n-1] C_1.$$

$$\text{Or, } V_o[n] C_2 = V_o[n-1] C_2 - V_i[n-1] C_1 \quad \text{As, } V_o[n-\frac{1}{2}] = V_o[n].$$

$$\text{Or, } V_o[n] = V_o[n-1] - \frac{C_1}{C_2} V_i[n-1].$$


Taking Z-transform :-  $V_o[z] = z^{-1} V_o[z] - \frac{C_1}{C_2} z^{-1} V_i[z]$ .

$$\text{Or, } \frac{V_o[z]}{V_i[z]} = -\frac{C_1}{C_2} \frac{z^{-1}}{1-z^{-1}} = -\frac{C_1}{C_2} \frac{1}{(z-1)}$$

$\uparrow$  Inverting  
 $\uparrow$   $z^{-1} \rightarrow \text{delay}$

If matching is perfect, it comes as ratioed form.

## Parasitic Effects :

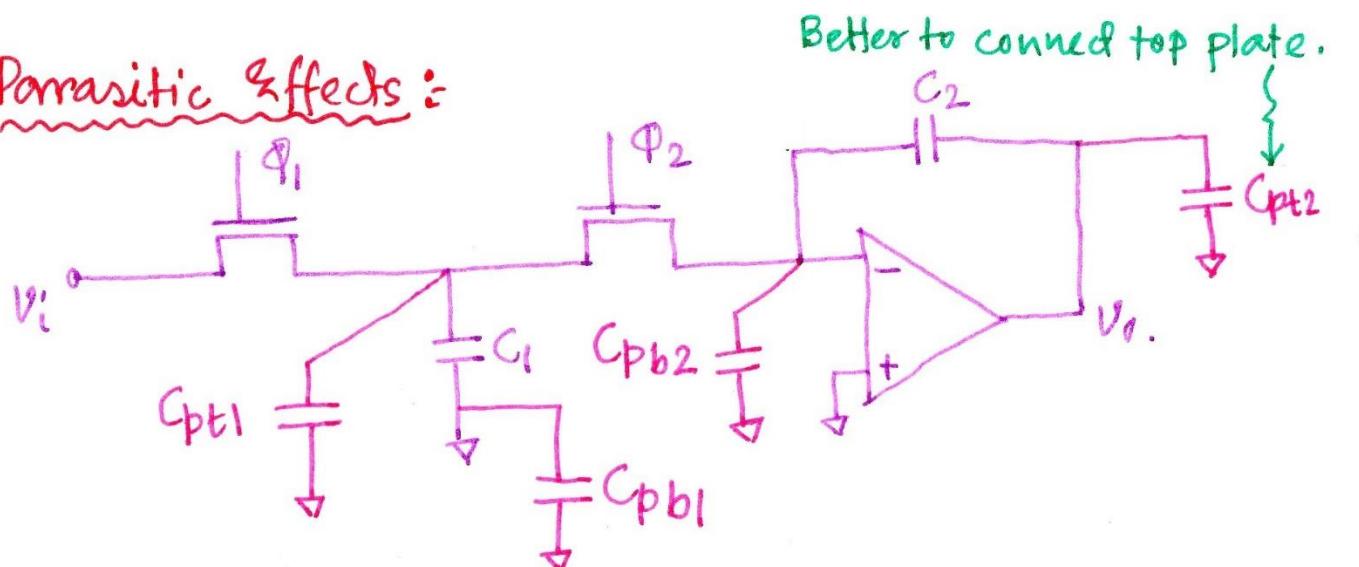


- ✓  $C_{pb1}$  and  $C_{pb2}$  does not have any effect.
- ✗  $C_{pt1}$  comes in parallel to  $C_1$ .
- $C_{pt2}$  acts as an output parasitic/load capacitance. It limits the speed of response. However, it does not change final settling value.

Modified transfer function :  $\frac{V_o[z]}{V_i[z]} = - \frac{(G + C_{pt1})}{C_2} \cdot \frac{1}{z-1}$ .

parasitic  
sensitive.

## Parasitic Insensitive Integrator :-

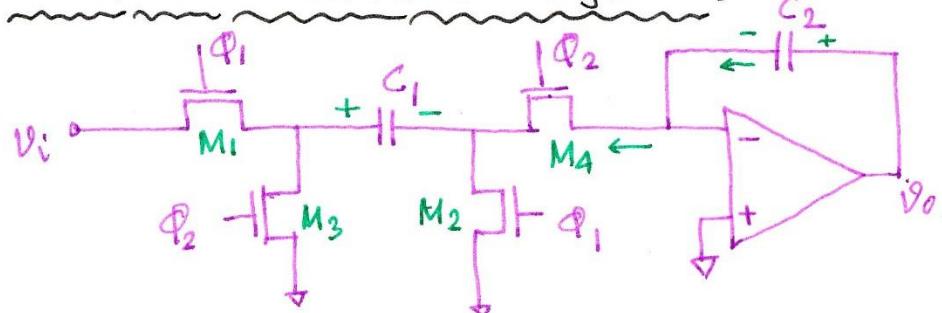

At  $\Phi_1$  phase : charge stored at  $Q = V_i[n-1]C_1$ .

charge stored at  $C_2 = V_o[n-1]C_2$ .

At  $\Phi_2$  phase :-  $C_1$  losses charge and  $C_2$  gain charge.

Final charge at  $C_2 = V_o[n-\frac{1}{2}]C_2 = V_o[n]C_2$

Charge transferred =  $V_o[n]C_2 - V_o[n-1]C_2$

Charge conservation :-  $V_o[n]C_2 - V_o[n-1]C_2 = V_i[n-1]Q$


$$\text{Or, } V_o[n]C_2 = V_o[n-1]C_2 + V_i[n-1]Q$$

Taking Z-transform :-  $V_o[z]C_2 = z^{-1}V_o[z]C_2 + z^{-1}V_i[z]Q$

$$\text{Or, } V_o[z][1-z^{-1}]C_2 = z^{-1}V_i[z]Q$$

$$\text{Or, } \frac{V_o[z]}{V_i[z]} = \frac{z^{-1}Q}{C_2(1-z^{-1})} = \frac{Q}{C_2} \frac{z^{-1}}{1-z^{-1}} = \frac{Q}{C_2(z-1)}.$$

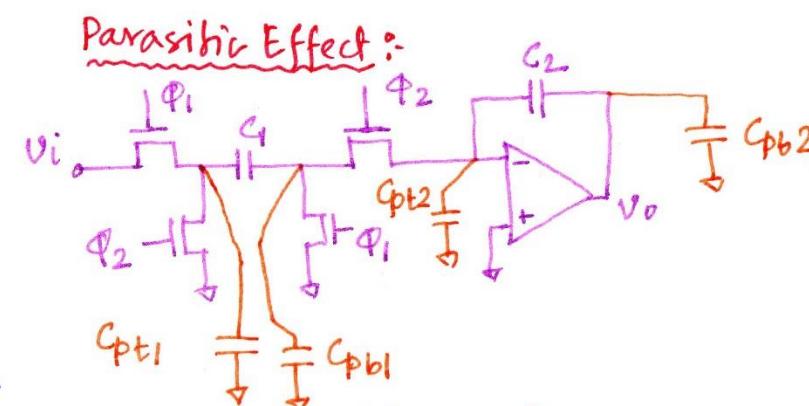(noninverting)  $z^{-1} \rightarrow \text{delay}$



At  $\Phi_1$  :  $\begin{cases} C_{pt1} \rightarrow V_i \\ C_{pb1} \rightarrow \text{grounded} \end{cases}$  } no effect

At  $\Phi_2$  :  $\begin{cases} C_{pt1} \rightarrow \text{grounded} \\ C_{pb1} \rightarrow \text{grounded} \end{cases}$

$C_{pt2} \rightarrow \text{grounded}$

$C_{pb2} \rightarrow \text{provides delay.}$

It gives parasitic insensitive tr. fn.


# EE60032: Analog Signal Processing



**Dr. Ashis Maity**  
**Assistant Professor**

Email: [ashis@ee.iitkgp.ac.in](mailto:ashis@ee.iitkgp.ac.in)  
Department of Electrical Engineering  
Indian Institute of Technology, Kharagpur  
West Bengal, India

## Parasitic Insensitive Integrator :-

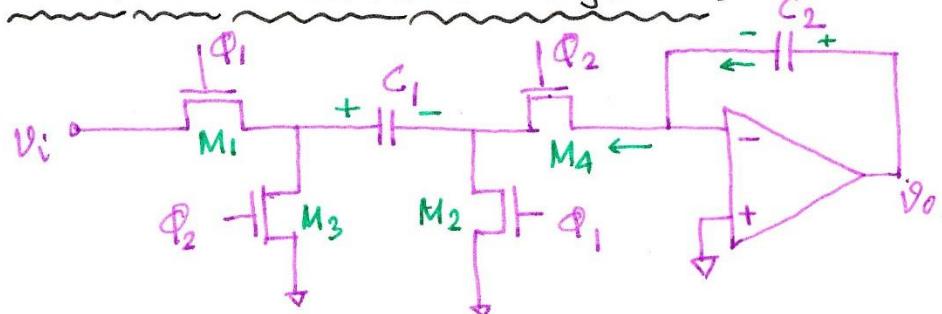

At  $\Phi_1$  phase : charge stored at  $Q = V_i[n-1]C_1$ .

charge stored at  $C_2 = V_o[n-1]C_2$ .

At  $\Phi_2$  phase :-  $C_1$  losses charge and  $C_2$  gain charge.

Final charge at  $C_2 = V_o[n-\frac{1}{2}]C_2 = V_o[n]C_2$

Charge transferred =  $V_o[n]C_2 - V_o[n-1]C_2$

Charge conservation :-  $V_o[n]C_2 - V_o[n-1]C_2 = V_i[n-1]Q$


$$\text{or, } V_o[n]C_2 = V_o[n-1]C_2 + V_i[n-1]Q$$

Taking Z-transform :-  $V_o[z]C_2 = z^{-1}V_o[z]C_2 + z^{-1}V_i[z]Q$

$$\text{or, } V_o[z][1-z^{-1}]C_2 = z^{-1}V_i[z]Q$$

$$\text{or, } \frac{V_o[z]}{V_i[z]} = \frac{z^{-1}Q}{C_2(1-z^{-1})} = \frac{Q}{C_2} \frac{z^{-1}}{1-z^{-1}} = \frac{Q}{C_2(z-1)}.$$

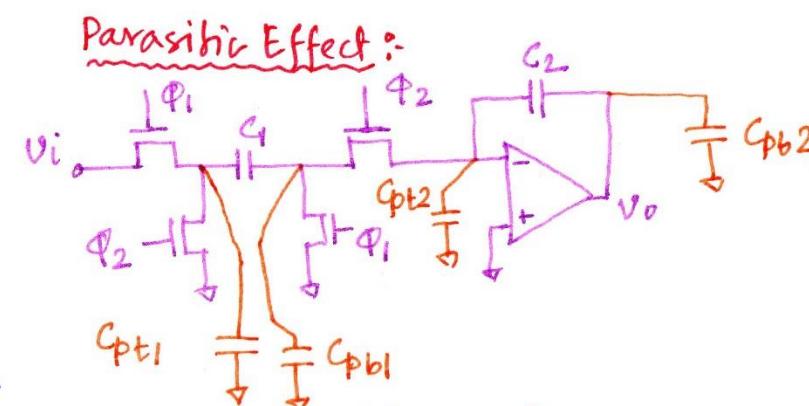(noninverting)  $z^{-1} \rightarrow \text{delay}$





At  $\Phi_1$  :  $\begin{cases} C_{pt1} \rightarrow V_i \\ C_{pb1} \rightarrow \text{grounded} \end{cases}$  } no effect

At  $\Phi_2$  :  $\begin{cases} C_{pt1} \rightarrow \text{grounded} \\ C_{pb1} \rightarrow \text{grounded} \end{cases}$  }  $C_{pt2} \rightarrow \text{grounded}$

$C_{pb2} \rightarrow \text{provides delay.}$

It gives parasitic insensitive tr. fn.

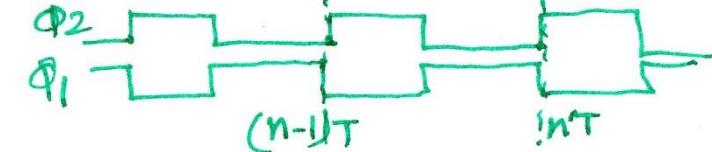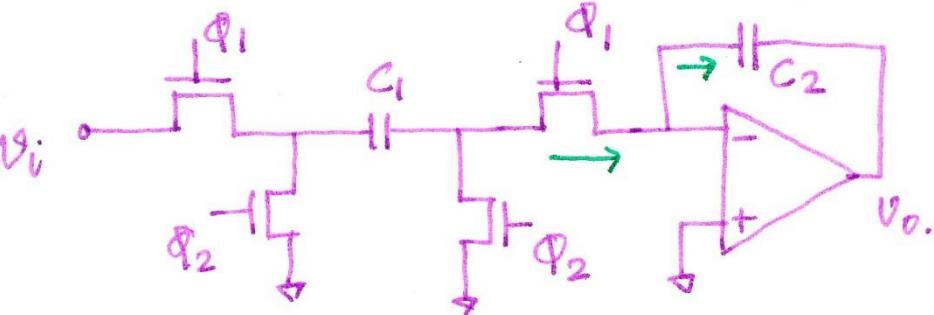Q A delay free, parasitic insensitive, inverting integrator:-



At  $\Phi_2$  phase: charge stored at  $C_2 = C_2 V_o[n-1]$ .

At  $\Phi_1$  phase: charge stored at  $C_1 = 0$ .

At  $\Phi_1$  phase: charge stored at  $C_1 = V_i[n] Q$ .

charge stored at  $C_2 = V_o[n] C_2$ .

$C_2$  loses charge

Charge conservation: Total charge at  $\Phi_1$  and  $\Phi_2$  phases are same.

$$V_i[n] Q + V_o[n] C_2 = C_2 V_o[n-1].$$

$$Q + V_o[n] C_2 - C_2 V_o[n-1] = -V_i[n] Q$$

$$Q + V_o[n] - V_o[n-1] = -\frac{Q}{C_2} V_i[n].$$

$$Q + V_o[z] - z^{-1} V_o[z] = -\frac{Q}{C_2} V_i[z].$$

$$Q + V_o[z] [1 - z^{-1}] = -\frac{Q}{C_2} V_i[z]$$

$$\frac{V_o[z]}{V_i[z]} = -\frac{Q/C_2}{1-z^{-1}} = -\frac{Q}{C_2} \frac{z}{(z-1)}$$

Delay free, inverting, parasitic insensitive.

Q How can we approximate the integrator transfer function as an ideal continuous time integrator?

Transfer function of an integrator.

$$H(z) = -\frac{C_1}{C_2} \frac{z^{-1}}{1-z^{-1}} = -\frac{C_1}{C_2} \frac{z^{-1/2}}{z^{1/2} - z^{-1/2}}$$

$$z = e^{sT} = e^{j\omega T} = \cos(\omega T) + j\sin(\omega T) \quad \text{where } T = \text{sampling period.} = 1/f_s$$

$$z^{1/2} = e^{j\omega T/2} = \cos\left(\frac{\omega T}{2}\right) + j\sin\left(\frac{\omega T}{2}\right) \quad \omega = \text{input signal frequency.}$$

$$z^{-1/2} = e^{-j\omega T/2} = \cos\left(\frac{\omega T}{2}\right) - j\sin\left(\frac{\omega T}{2}\right).$$

$$H(z) = -\frac{C_1}{C_2} \frac{z^{-1/2}}{2j\sin\frac{\omega T}{2}}$$

To get an integral action,  
ckt will act as a resistor.

$\omega \ll 1/T$ . or  ~~$\omega T \ll 1$~~   $\omega T \ll 1$ , then the switched capacitor

$$H(z) \approx -\frac{C_1}{C_2} \frac{z^{-1/2}}{2j\frac{\omega T}{2}} = -\frac{C_1}{C_2} \frac{z^{-1/2}}{j\omega T}$$

$z^{-1/2}$  is just a delay term; it has nothing to do with integral action.


$$\text{Integrator gain } K_i = \frac{C_1}{C_2 T}$$

In continuous time  $\rightarrow \frac{1}{s}$ .

In discrete time  $\rightarrow \frac{1}{1-z^{-1}}$
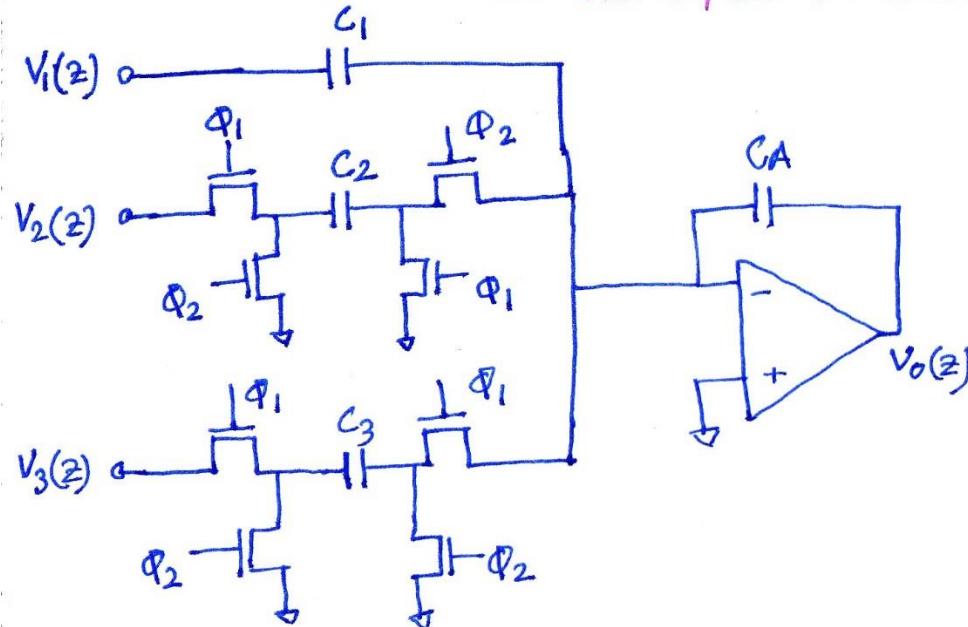
## Signal flow graph analysis :-


- Charge transfer equation for larger circuit may be tedious.
- Few rules can be developed to analyse the circuit graphically. Similar to block diagram.



$$\frac{V_{01}(z)}{V_1(z)} = -\frac{C_1}{CA}$$

$$\frac{V_{02}(z)}{V_2(z)} = \frac{C_2}{CA} \cdot \frac{z^{-1}}{1-z^{-1}}$$
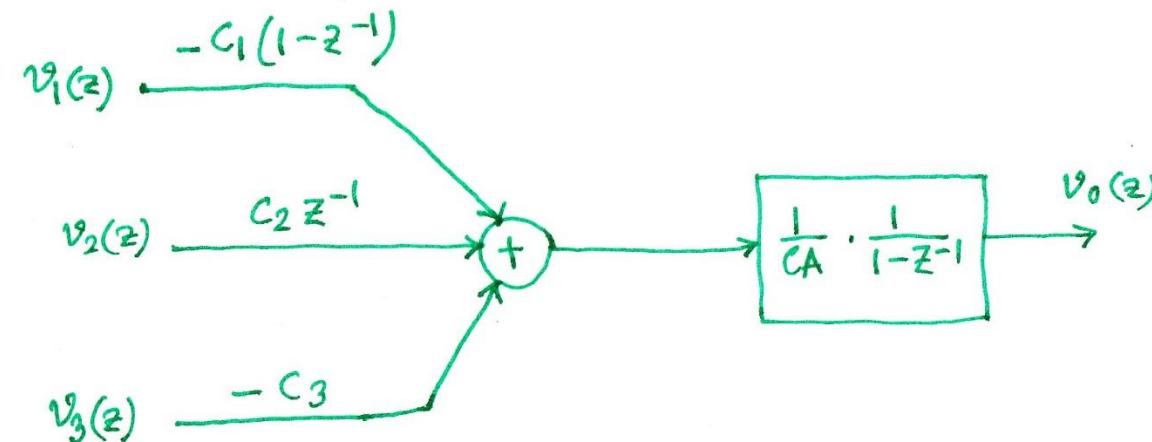
$$\frac{V_{03}(z)}{V_3(z)} = -\frac{C_3}{CA} \cdot \frac{1}{1-z^{-1}}$$



Applying voltage superposition:-

$$V_0(z) = -\frac{C_1}{CA} V_1(z) + \frac{C_2}{CA} \cdot \frac{z^{-1}}{1-z^{-1}} V_2(z) + \frac{C_3}{CA} \cdot \frac{1}{1-z^{-1}} V_3(z)$$


# EE60032: Analog Signal Processing



**Dr. Ashis Maity**  
**Assistant Professor**


Email: [ashis@ee.iitkgp.ac.in](mailto:ashis@ee.iitkgp.ac.in)  
Department of Electrical Engineering  
Indian Institute of Technology, Kharagpur  
West Bengal, India

### First Order Filter :-

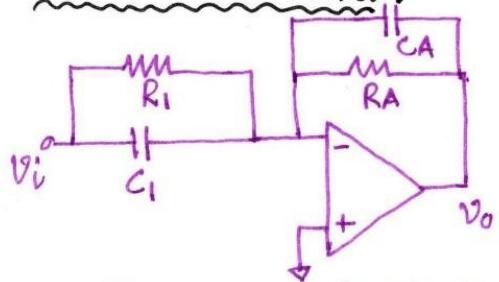


$$\frac{V_o}{V_i} = - \frac{RA}{R_1} \cdot \frac{(1 + SR_1G)}{(1 + SRA(A))}$$

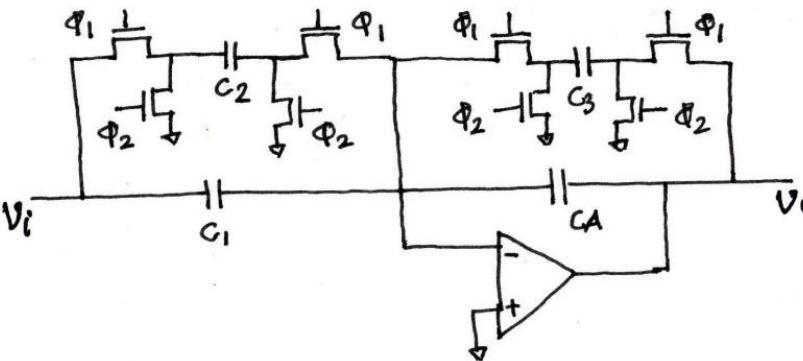First order, continuous time,  
Active RC filter.



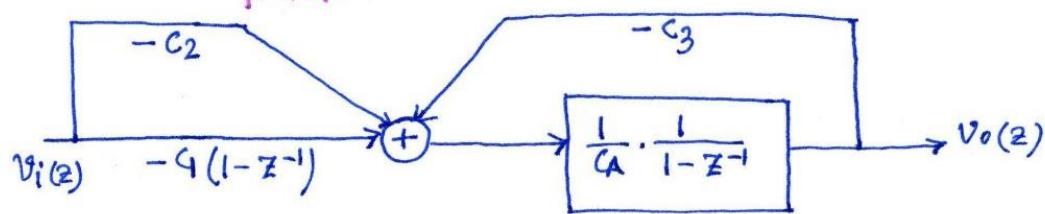First order, switched capacitor, delay free, active RC filter.



$$-\frac{G(1-z^{-1})}{CA(1-z^{-1})} Vi(2) + C_2 Vi(2) + C_3 V_o(2) = V_o(2)$$

$$\text{or, } -G(1-z^{-1}) Vi(2) - C_2 Vi(2) = C_A(1-z^{-1}) V_o(2) + C_3 V_o(2)$$

$$\begin{aligned} H(z) &= \frac{V_o(2)}{V_i(2)} = -\frac{C_A(1-z^{-1}) + C_2}{C_3 + C_A(1-z^{-1})} \\ &= -\frac{\left(\frac{C_1+C_2}{C_A}\right)z - \frac{C_1}{C_A}}{\left(1 + \frac{C_3}{C_A}\right)z - 1} \end{aligned}$$


$$\text{Pole } Z_p = \frac{C_A}{C_A + C_3} < 1$$

$$\text{Zero } Z_z = \frac{C_1}{C_1 + C_2} < 1$$

As,  $z = e^{j\omega T}$ ,  $\omega \rightarrow 0$ ,  $z \rightarrow 1$

So, DC gain can be found by setting  $z = 1$ .

$$H(1) = -\frac{C_2}{C_3}$$

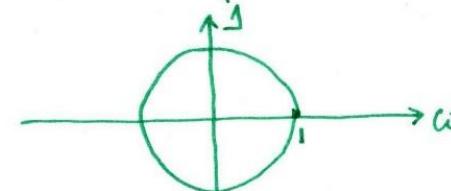

Pole and zero are inside the unit circle, hence always stable.

How to get pole and zero locations under  $\omega T \ll 1$ .

$$H(z) = \frac{V_o(z)}{V_i(z)} = -\frac{\left(\frac{C_1 + C_2}{CA}\right)z - \frac{C_1}{CA}}{\left(1 + \frac{C_3}{CA}\right)z - 1} = -\frac{\frac{C_L}{CA}(z-1) + \frac{C_2}{CA}z}{z-1 + \frac{C_3}{CA}z} = -\frac{\frac{C_1}{CA}(z^{1/2} - z^{-1/2}) + \frac{C_2}{CA}z^{1/2}}{z^{1/2} - z^{-1/2} + \frac{C_3}{CA}z^{1/2}}$$

$$\begin{aligned} H(j\omega T) &= \frac{V_o(e^{j\omega T})}{V_i(e^{j\omega T})} = -\frac{\frac{C_1}{CA} 2j \sin \frac{\omega T}{2} + \frac{C_2}{CA} (\cos \frac{\omega T}{2} + j \sin \frac{\omega T}{2})}{2j \sin \frac{\omega T}{2} + \frac{C_3}{CA} (\cos \frac{\omega T}{2} + j \sin \frac{\omega T}{2})} \\ &= -\frac{\frac{2C_1 + C_2}{CA} j \sin \frac{\omega T}{2} + \frac{C_2}{CA} \cos \frac{\omega T}{2}}{\left(2 + \frac{C_3}{CA}\right) j \sin \frac{\omega T}{2} + \frac{C_3}{CA} \cos \frac{\omega T}{2}} \end{aligned}$$


When  $\omega T \ll 1$ , input signal is changing very slowly compared to the sampling freq.

$$z = \frac{\frac{2C_1 + C_2}{CA} j \frac{\omega T}{2} + \frac{C_2}{CA}}{\left(2 + \frac{C_3}{CA}\right) j \frac{\omega T}{2} + \frac{C_3}{CA}}$$

Zero,  $\omega_{ZT} = \frac{2C_2/CA}{2C_1 + C_2/CA} = \frac{C_2/C_1}{(1 + \frac{C_2}{2C_1})}$

Pole,  $\omega_{PT} = \frac{C_3/CA}{(1 + C_3/2CA)}$

Switch Sharing :-

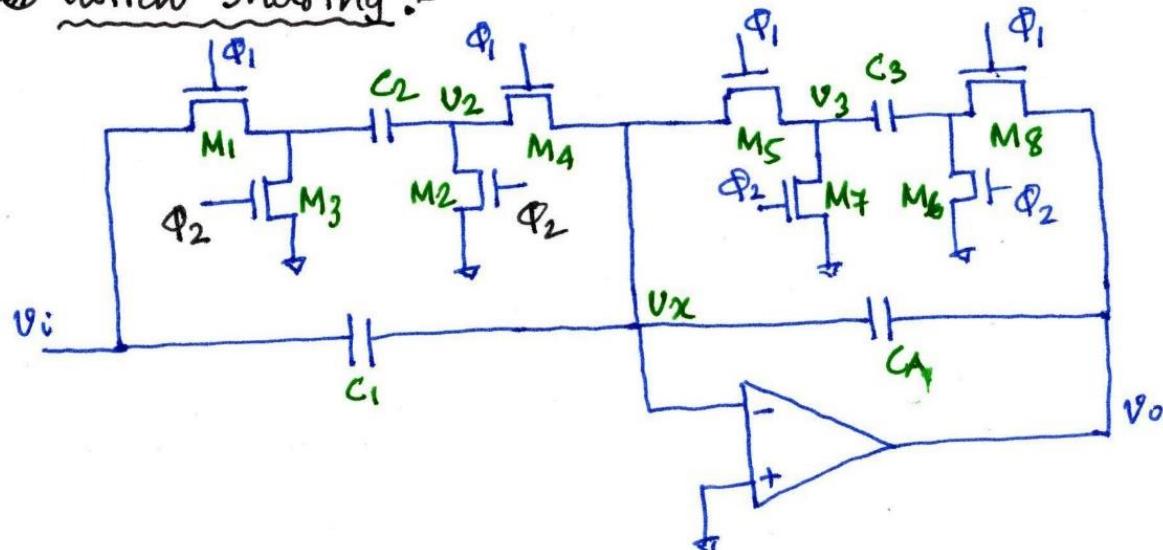


At  $\Phi_1$  phase:  $V_2 = V_3$

At  $\Phi_2$  phase:  $V_2 = V_3 = 0$

So,  $V_2$  and  $V_3$  can be shorted.

However,  $V_x$  is floating,  $V_x \neq (V_2, V_1)$  at  $\Phi_2$ .

Modified structure :-

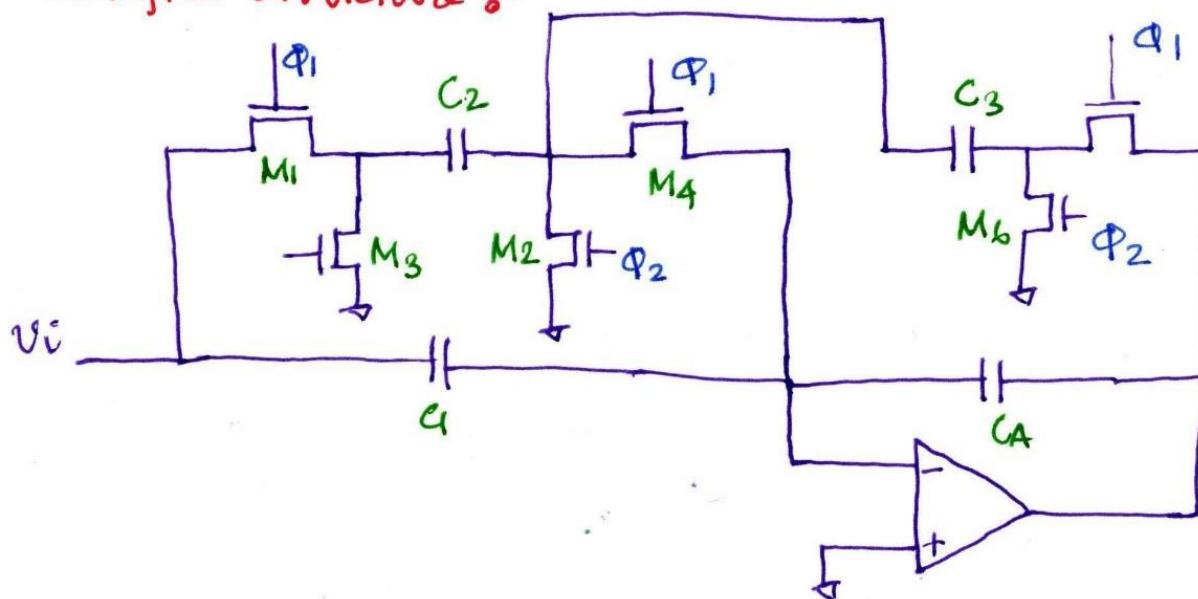

$M_7$  &  $M_8$  are removed.

Problem: The first order filter as shown in the previous slide, find the value of  $C_2$  needed for a first order low pass filter, that has  $G=0$  and a pole at  $\frac{1}{64}$  th of the sampling frequency using approximate equation. The low frequency gain should be 1.

$$\text{Generalised expression : } H(z) = - \frac{\left(\frac{C_1 + C_2}{CA}\right)z - \frac{C_1}{CA}}{\left(1 + \frac{C_3}{CA}\right)z - 1}$$

$$\begin{aligned} \text{DC gain } H(1) &= - \frac{\frac{C_1 + C_2}{CA} - \frac{C_1}{CA}}{\left(1 + \frac{C_3}{CA}\right) - 1} = - \frac{C_2/CA}{C_3/CA} \quad \text{if } G=0. \\ &= - \frac{C_2/C_3}{1-1} = 1-1 \quad \text{if } C_2 = C_3. \end{aligned}$$

$$\omega_p T = + \frac{C_3/CA}{\left(1 + \frac{C_3/2}{CA}\right)}$$

$$\text{As } f_p = \frac{2\pi}{64} = \frac{1}{64T}. \quad \left| \quad \frac{2\pi}{64} = \frac{C_3/CA}{1 + \frac{C_3/2}{CA}} \right.$$

$$\text{or, } \frac{\omega_p}{2\pi} = \frac{1}{64T}.$$

$$\text{or, } \omega_p T = \frac{2\pi}{64}$$

$$\text{or, } \frac{2\pi}{64} + \frac{2\pi}{64} \cdot \frac{C_3}{2CA} = \frac{C_3}{CA}.$$

$$\text{or, } \frac{C_3}{CA} \left[ 1 - \frac{2\pi}{128} \right] = \frac{2\pi}{64}.$$

$$\text{or, } \frac{C_3}{CA} = \left[ \frac{2\pi/64}{1 - 2\pi/128} \right] = 0.1032$$

If  $CA = 10 \mu F$ ,  $C_3 = 1.032 \mu F$ ,  $C_2 = 1.032 \mu F$ .

## Try Yourself!

1. A low-pass Butterworth filter must provide a passband flatness of 0.5 dB for  $f < f_1 = 1$  MHz. If the order of the filter must not exceed 5, what is the greatest stopband attenuation at  $f_2 = 2$  MHz?
2. A Chebyshev filter must provide an attenuation of 25 dB at 5 MHz. If the order of the filter must not exceed 5, what is the minimum ripple that can be achieved across a bandwidth of 2 MHz?
3. Design the SK filter for  $\omega_n = 2\pi(50$  MHz),  $Q = 1.5$ , and low-frequency gain of 2. Assume capacitor values must fall in the range of 10 pF to 100 pF.