

Test 1

Preetyush Jaiswal
18EE35014

Q1.

Given conditions:

$$R_2 = 0.18 \Omega \text{ (referred to stator)}$$

The IM produces rated torque at $\frac{1}{2}$ rated speed.

$$\omega_{syn} = 2\pi \times \frac{2f}{p} = 2\pi \times \frac{2 \times 50}{4} = 50\pi \text{ rad/s}$$

$$s_{rated} = 0.03$$

$$s\omega_{syn} = 0.03 \times 50\pi = 1.5\pi$$

$$\omega_{rotor, rated} = 50\pi - 1.5\pi = 48.5\pi$$

Operated at $\frac{1}{2}$ speed } Given above

$$\therefore \omega_{rotor, rated} = \frac{48.5\pi}{2} = 24.25\pi$$

$$T \propto s\omega = \text{constant}$$

$$\omega_{syn} = 24.25\pi + 1.5\pi = 25.75\pi$$

ϕ is same

$$V_{L-L} = \frac{415 \times 25.75\pi}{50} = 213.725 \text{ V}$$

$$\therefore V_{\text{per phase}} = \frac{213.725}{\sqrt{3}} \text{ V} = 123.39 \text{ V} \approx 123.4 \text{ V}$$

$$f_{\text{stator}} = \frac{25.75\pi}{2\pi} = 12.875 \text{ Hz}$$

(1°)

$$\begin{aligned} V_{L-L} &= 213.725 \text{ V} \\ f_{\text{stator}} &= 12.875 \text{ Hz} \end{aligned}$$

(2°)

$$\begin{aligned} \frac{V_{DC}}{2} \propto m &= \frac{V_{L-L}}{\sqrt{3}} \times \sqrt{2} \\ \Rightarrow \frac{750}{2} \propto m &= \frac{213.725}{\sqrt{3}} \times \sqrt{2} \end{aligned}$$

$$\Rightarrow m = 0.46534$$

$$\therefore \frac{V_m}{V_T} = m$$

$$\begin{aligned} \Rightarrow V_m = m V_T &= 0.46534 \times 10 \text{ V} \\ &= 4.6534 \text{ V} \end{aligned}$$

$$\left. \begin{aligned} \therefore V_m &= 10 \text{ V} \\ &(\text{given}) \end{aligned} \right\}$$

$$\therefore V_m = 4.653 \text{ V}$$

(iii)

Here, duty cycle $= D = \frac{1}{2} (1 + m \sin \omega t)$
 $\Rightarrow D = \frac{1}{2} (1 + 0.4653 \sin \omega t)$

Since phase sequence is RYB.

$$V_y = \frac{m V_{\Delta L}}{2} \sin(\omega t - \frac{2\pi}{3})$$

To maximize V_y ,

$$\omega t - \frac{2\pi}{3} = \frac{\pi}{2} \Rightarrow \boxed{\omega t = \frac{7\pi}{6}}$$

Then, $D = \frac{1}{2} (1 + 0.4653 \sin(\frac{7\pi}{6}))$
 $= \frac{1}{2} (1 + 0.4653 (-\frac{1}{2}))$
 $= 0.383675$

Also, $D = \frac{T_{ON}}{T_s}$ & $f_s = 10 \text{ kHz}$

$$T_{ON} \times f_s = D$$
$$T_{ON} = \frac{D}{f_s} = D \times T_s = \frac{0.383675}{10 \times 10^3} \text{ s}$$
$$= 38.3675 \mu\text{s}$$

$$T_{OFF} = T_s - T_{ON} = \frac{(1 - 0.383675)}{10 \times 10^3} \text{ s}$$
$$= 61.6325 \mu\text{s}$$

Q20: Given, the IM produces the rated torque at $\frac{2}{3}$ rd the rated speed.

$$(9) \quad \left. \begin{aligned} \omega_{syn} &= 50\pi \\ \omega_{motor, rated} &= (50 - 1.5)\pi = 48.5\pi \end{aligned} \right\} \text{from Q1.}$$

$$T \propto \omega_s$$

$$\omega_B = 1.5\pi$$

$$\text{at } T = \frac{2}{3}$$

$$\omega_B = \left(1.5 \times \frac{2}{3}\right)\pi = \pi$$

$$\therefore \omega_{syn} = \omega_{motor} + \omega_B = (48.5 + 1)\pi = 49.5\pi \text{ rad/s}$$

V_{input} for the IM

$$= 415 \times \frac{49.5}{50} = 410.85 \text{ V} = V_{LL}(\text{rms})$$

$$f_{stator} = \frac{49.5\pi}{2\pi} = 24.25 \text{ Hz}$$

Now, since ϕ is constant,

$$|V| = \frac{3}{2} \times 410.85 \times \frac{\sqrt{2}}{\sqrt{2}} = \boxed{503.186 \text{ V}}$$

$$b = \boxed{24.25 \text{ Hz}}$$

2a (ii)

$$|V_{SVM}|_{max} = V_{dc} \times \frac{\sqrt{3}}{2}$$

$$V_{LL, max} = V_{dc} \times \frac{\sqrt{3}}{2} \times \frac{2}{3} \times \sqrt{2}$$

$$V_{LL, rms} = V_{dc} \times \frac{\sqrt{3}}{2} \times \frac{2}{3} \times \frac{1}{\sqrt{2}} \times \sqrt{2}$$

$$= \frac{V_{dc}}{\sqrt{2}}$$


$$\frac{V_{dc, min}}{\sqrt{2}} = V_{LL, rms}$$

$$V_{dc, min} = 410.85 \times \sqrt{2}$$


$$V_{dc, min} = 581.03 \text{ V}$$

2b

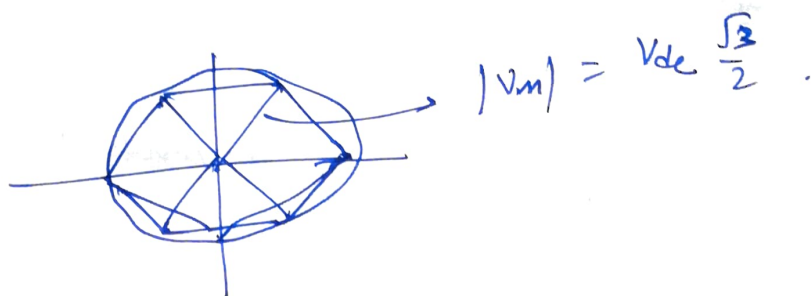for minimum V_{dc} we consider maximum of SVM.



(2c)

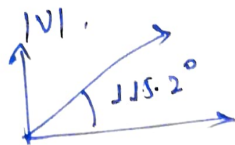

$$T_s = 100 \mu s, \rightarrow T_s = 100 \times 10^{-6}$$

$$f = 43.5 \text{ Hz}, \rightarrow T = 0.025$$

$$\text{Steps} = \frac{0.02}{100 \times 10^{-6}} = 200 \text{ steps}$$

$$\Delta\phi = \frac{360}{200} = 1.8^\circ$$

$$\star^\circ = \frac{11.5}{1.8} = 63.88.$$

$$\theta = 64 \times 1.8 = 115.2$$

$$|V| \cos 58.2^\circ = |V_2| T_1 + |V_2| \cos 68^\circ T_2$$

$$|V| \sin 58.2^\circ T_1 = |V_2| \sin 60^\circ T_2$$

$$T_2 = \frac{50.2 \times 10^6 \sin 58.2^\circ}{581.03 \sin 60^\circ} T_1$$

$$= 0.821 T_1$$

$$= 82.1 \mu s.$$

$$58.2 T_1 = |V_2| T_1 - |V_2| \cos 15^\circ T_2$$


$$T_1 = 8.375 \mu s.$$

$$T_{01} = \frac{T_0}{2} = 4.7625 \mu s.$$

$$T_{02} \text{ switch of } R \text{ is on for } = \cancel{92.53}$$

$$\frac{92.2}{95.237} \mu s.$$

Q40
= (i)

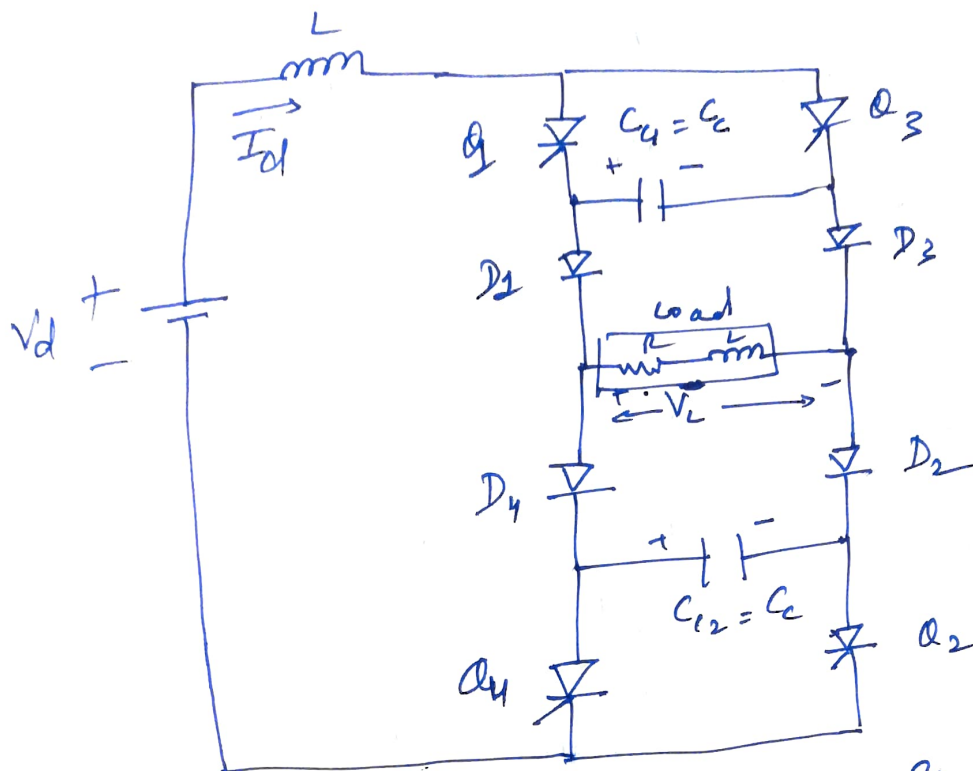



~~The~~ Circuit Schematic of Single Phase Full Bridge ASCI.

(ii)

Mode - 1

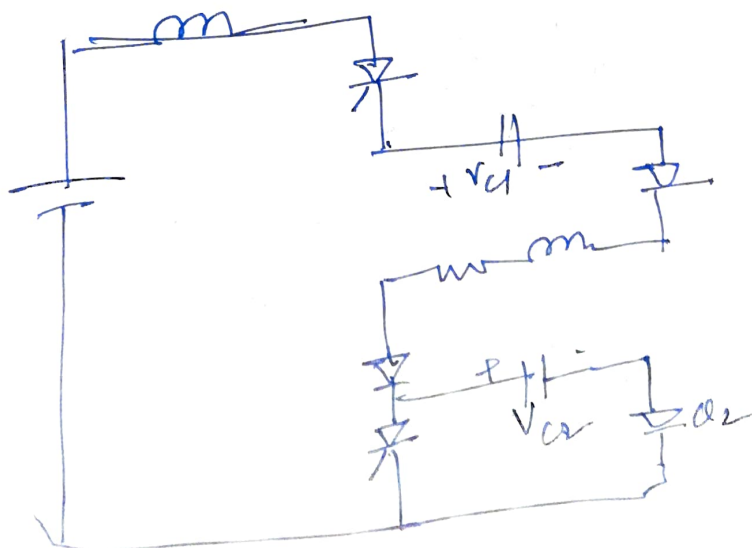Thyristor pairs a_3 & a_4 are ~~conducting~~ ^{turn OFF} (ON)
& a_1 & a_2 turn ON.



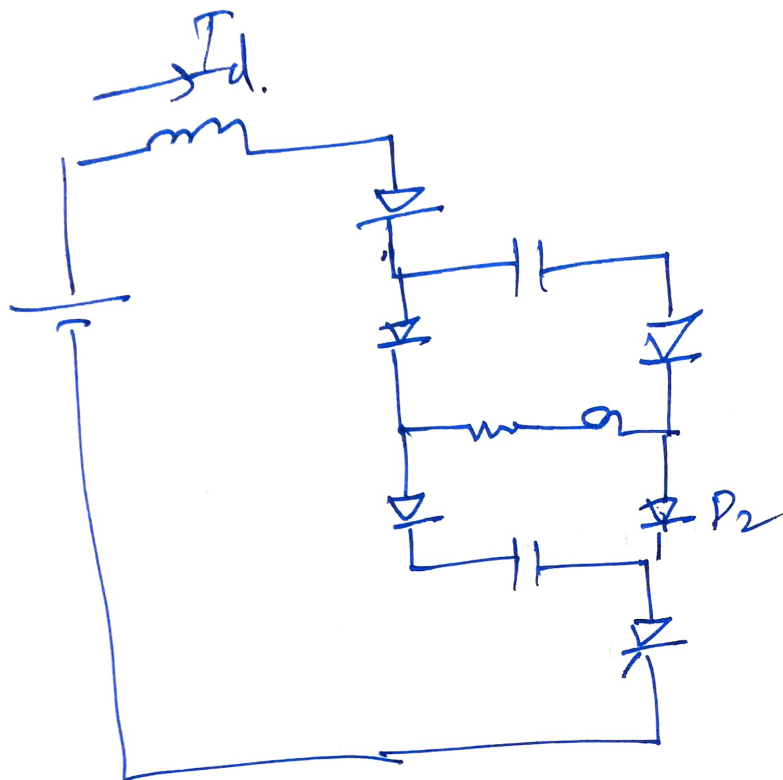

$$V_u = V_{c2}$$

$$= V_{cD} + \frac{I_d t}{C_c}$$

$$V_L = -I_d R$$

$$0 = V_{cD} + \frac{I_d t_1}{C} + I_d R$$

$$V_c = -I_d R \quad \text{at } t = t_1$$

Mode 2:
When,