
ASSIGNMENT-1

17EE35004 J. Kalyan Raman


$$\frac{I(s)}{V(s)} = RI(s) + sLI(s) + \frac{1}{sC}I(s)$$
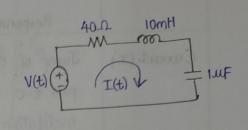
$$\frac{I(s)}{V(s)} = \frac{1}{R+sL+\frac{1}{sC}} = \frac{sC}{sLC+sRC+1}$$




$$\xi = \frac{R}{2} \sqrt{\frac{C}{L}} = 0.2$$
, $\omega_0 = \frac{1}{\sqrt{LC}} = 10^{\frac{4}{5}} \text{ sad/sec} \Rightarrow \frac{4}{\xi \omega_0} \approx 2 \text{ ms}$

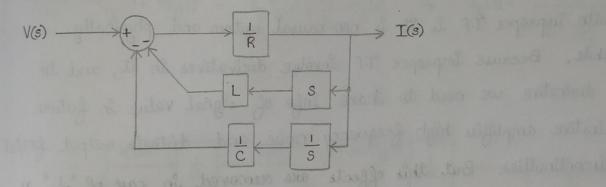
$$\frac{\overline{I(s)}}{V(s)} = \frac{1}{R(1+\frac{1}{R}(sL+\frac{1}{sC}))} = \frac{\frac{1}{R}}{1+\frac{1}{R}(sL+\frac{1}{sC})}$$



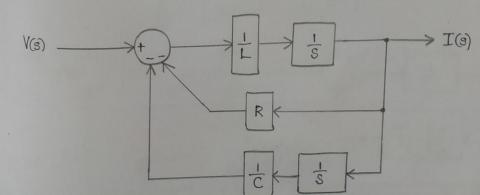
$$\frac{T(s)}{V(s)} = \frac{1}{sL(1+\frac{1}{sL}(R+\frac{1}{sC}))} = \frac{1}{1+\frac{1}{sL}(R+\frac{1}{sC})}$$




Block Diagram representation:

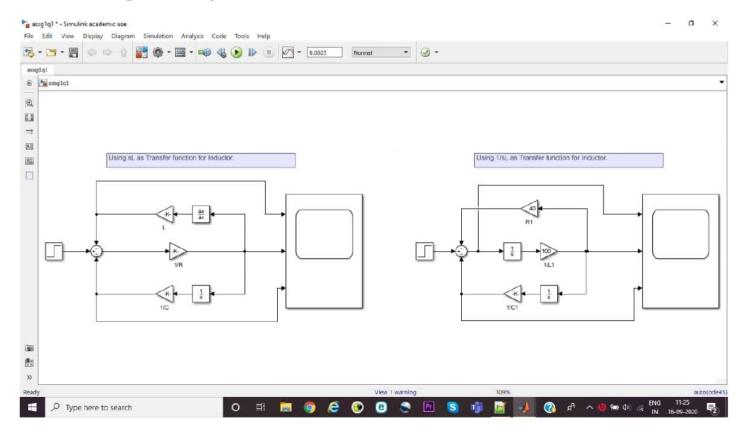

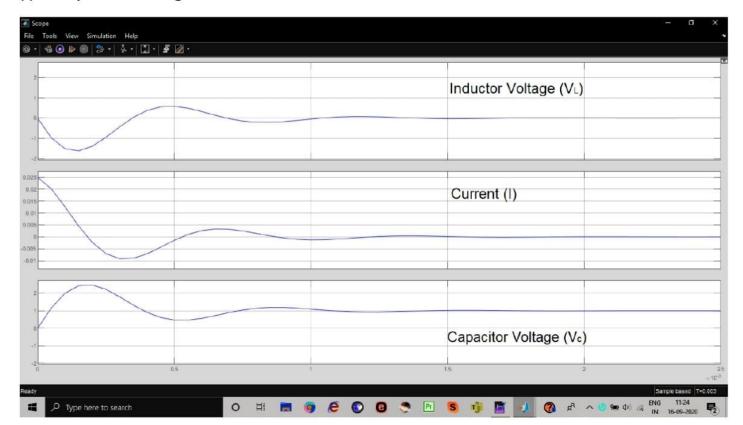(i) Response using "sL" as TF of Inductance



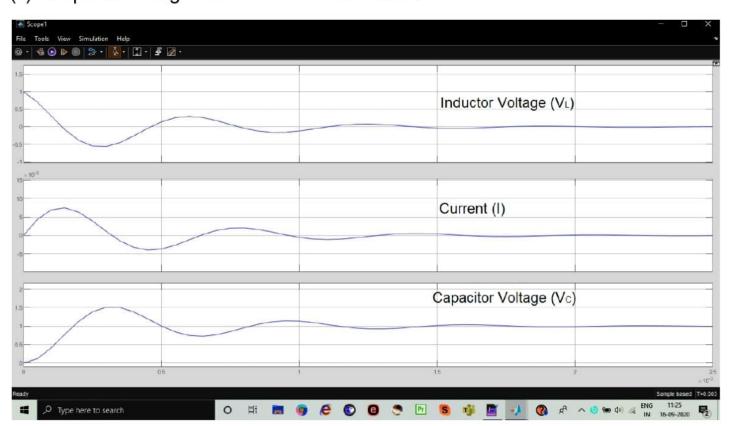
(ii) Response using "1/sL" as TF of Inductance



	limo) z	Response In (i)	Response in (li)
	Cwoert (I)	Jump of 0.025A at t=0,	Continuous at t=0, and later
	1 4 (4) 1	pass t=0 a damped(exponential)	damped oscillation
1		Oscillation.	52 148/1 GOV
	V _L	At t=0, It's value is zero	Tump of 1V at t=0, and
-	ant a	and decreasing furt after t=0.	later a damped oscillation
-	V _C	% overshoot is more than	% Opvershoot is around
1		100% i.e., Vc, peak > 2 Vc(00)	50% i.e., √c, peak ≈ 1.5√c(∞)

Reason behind it is that "il" is an improper Transfer Fuction. The problem with improper T.F is it is non-causal system and physically unrealizable. Because improper T.F involve derivatives in it, and to define a derivative we need to have info of signal value in future. Also derivative amplifies high frequency noise and distorts output for/at input discontinuities. But this effects are removed in case of "I" as it is a proper Transfer Function.

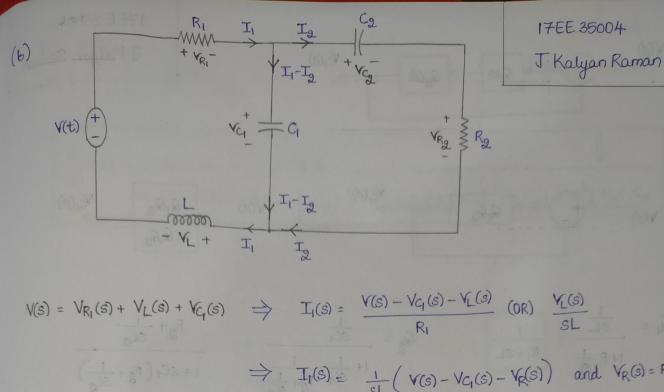Therefore using "I" T.F to represent Inductor is proper and correct.




$$V(s) = V_{R_1}(s) + V_{L}(s) + V_{G}(s) \Rightarrow I_{I}(s) = \frac{V(s) - V_{G}(s) - V_{L}(s)}{R_1} \quad (OR) \quad \frac{V_{L}(s)}{sL}$$


$$\Rightarrow I_{I}(s) = \frac{1}{sL} \left(V(s) - V_{G}(s) - V_{R}(s) \right) \quad \text{and} \quad V_{R}(s) = RI_{G}(s)$$


$$V_{C_{1}}(S) = \frac{1}{SC_{1}} \left(I_{1}(S) - I_{2}(S) \right)$$

$$V_{C_{1}}(S) = V_{C_{2}}(S) + V_{R_{2}}(S) = R_{2} I_{2}(S) + \frac{1}{SC_{2}} I_{2}(S) \Rightarrow I_{2}(S) = \frac{V_{C_{1}}(S)}{R_{2} + \frac{1}{SC_{2}}} = \frac{\frac{1}{R_{2}} V_{C_{1}}(S)}{1 + \frac{1}{R_{2}} \frac{1}{SC_{2}}}$$

$$1 + \frac{1}{R_{2}} \frac{1}{SC_{2}}$$

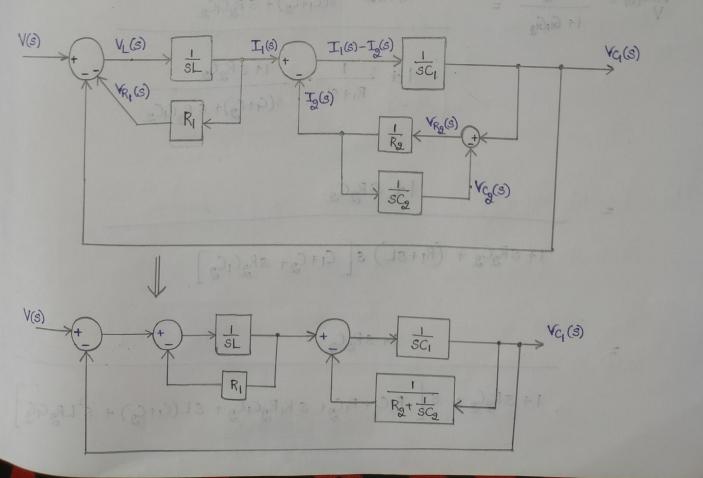

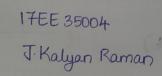

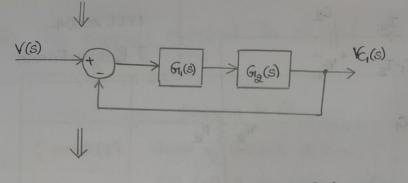

$$G_1 = \frac{1}{SL} = \frac{1}{R_1 + SL}$$

$$G_{lg} = \frac{\frac{1}{SC_1}}{1 + \frac{1}{SC_2}} = \frac{R_2 + \frac{1}{SC_2}}{1 + SC_1 \left(R_2 + \frac{1}{SC_2}\right)}$$

17EE35004 J Kalyan Raman

T.F btw & VCI (3)

$$\frac{V_{C_{1}}(s)}{V} = \frac{1 + sR_{2}C_{2}}{1 + s(R_{1}C_{1} + R_{1}C_{2} + R_{2}C_{2}) + s'(R_{1}R_{2}C_{1}C_{2} + LC_{1} + LC_{2}) + s^{3}LR_{2}C_{1}C_{2}}$$

U : TUHIT

gr a TU97UU

su at hon.


J = 2 1 - 1 = 2 1 - 1

一切」「かか」

our test and

0.8



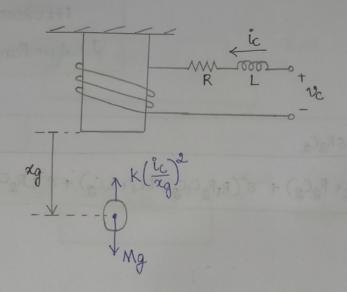

$$R = 20.L$$

 $M = 2kg$
 $L = 0.5H$
 $x_0 = 5x_10^{-3}m$
 $k = 3x_10^{-4}$ Nmt A⁻²

$$M \stackrel{\circ}{z}_{g} = Mg - k \left(\frac{ic}{z_{g}}\right)^{2}$$

$$v_{c} = Ri_{c} + L \frac{dic}{dt}$$

(a) ig, xg, ic and die are involved, and we need to use minimum states.

o'o
$$x_1 = x_g$$
, $x_2 = x_g$, $x_3 = x_c$ \Rightarrow $x_1 = x_g$, $x_2 = x_g$, $x_3 = \frac{dic}{dt}$ All variables are corrected

(b) Equilibrium point: given that
$$x_{10} = x_0 = 5 \times 10^{3} \text{m} \rightarrow x_0$$

$$\dot{x}_1 = 0 \Rightarrow x_{20} = 0 \Rightarrow \dot{x}_0$$

$$\dot{x}_2 = 0 \Rightarrow g - \frac{k}{M} \frac{x_{30}}{x_{40}} \Rightarrow x_{30} = x_{10} \sqrt{\frac{Mg}{k}}$$

$$\dot{x}_3 = 0 \Rightarrow -\frac{R}{L} x_{30} + \frac{1}{L} x_0 = 0$$

$$\Rightarrow x_{30} = x_{10} + \frac{1}{2} x_{30} + \frac{1}{2} x_{30} = x_{10} = x_{10} + \frac{1}{2} x_{30}$$

$$\dot{x}_3 = 0 \Rightarrow -\frac{R}{L} x_{30} + \frac{1}{L} x_0 = 0$$

$$\Rightarrow x_{30} = x_{10} + \frac{1}{2} x_{30} + \frac{1}{2} x_{30}$$

$$\dot{x}_3 = 0 \Rightarrow -\frac{R}{L} x_{30} + \frac{1}{L} x_0 = 0$$

$$\dot{x}_3 = 0 \Rightarrow x_{30} = x_{30} + \frac{1}{2} x_{30}$$

$$\dot{x}_3 = 0 \Rightarrow x_{30} = x_{30}$$

60 χο = 5x10 m , χο = 0 ; ιο = 1.278 A; νο = 25.56V

17EE 35004 J. Kalyan Raman

(C) Incremental State Space Representation

$$\frac{\partial f_1}{\partial x_1} = 0$$

$$\frac{\partial f_1}{\partial x_2} = 1$$

$$\frac{\partial f_1}{\partial x_3} = 0$$

$$\frac{\partial f_1}{\partial x_3} = 0$$

$$\frac{\partial f_{g}}{\partial x_{1}} = \frac{2k}{M} \cdot \frac{x_{3}^{2}}{x_{1}^{2}} \Big|_{x_{10}, x_{30}} = \frac{2k}{M} \cdot \frac{x_{30}^{2}}{x_{10}^{2}}$$

$$\frac{\partial f_{g}}{\partial x_{1}} = \frac{2g}{x_{10}}$$

$$\frac{\partial f_{g}}{\partial x_{2}} = 0$$

$$\frac{\partial f_{g}}{\partial x_{2}} = -\frac{2k}{M} \cdot \frac{x_{30}^{2}}{x_{10}^{2}}$$

$$\frac{\partial f_{g}}{\partial x_{3}} = -\frac{2k}{M} \cdot \frac{x_{30}^{2}}{x_{10}^{2}}$$

$$\frac{\partial f_{g}}{\partial x_{3}} = -\frac{2k}{M} \cdot \frac{x_{30}^{2}}{x_{10}^{2}}$$

$$\frac{\partial f_{g}}{\partial x_{30}} = -\frac{2k}{M} \cdot \frac{x_{30}^{2}}{x_{10}^{2}}$$

$$\frac{\partial f_{g}}{\partial x_{30}} = -\frac{2k}{M} \cdot \frac{x_{30}^{2}}{x_{10}^{2}}$$

$$\frac{\partial f_3}{\partial z_1} = 0$$

$$\frac{\partial f_3}{\partial z_2} = 0$$

$$\frac{\partial f_3}{\partial z_3} = -\frac{R}{L}$$

$$\frac{\partial f_4}{\partial z_2} = \frac{1}{L}$$

$$\frac{2q}{210} = \frac{2 \times 9.8}{5 \times 10^{-3}} = 3920 \quad \hat{j} - \frac{2}{240} \sqrt{\frac{kq}{M}} = -\frac{2}{5 \times 10^{-3}} \times \sqrt{\frac{3 \times 10^{-4} \times 9.8}{2}} \approx -15.34$$

$$-\frac{R}{L} = -\frac{20}{0.5} = -40 \quad \hat{j} - \frac{1}{L} = \frac{1}{0.5} = 2$$

°. Incremental TF

(d) T.F from 9 to x is given by $G(S) = C(SI-A)^TB$ $(SI-A) = \begin{bmatrix} S & -1 & 0 \\ -3920 & S & 15-34 \\ 0 & 0 & S+40 \end{bmatrix}$

17EE 35004 J. Kalyan Raman

$$(SI-A)^{-1} = \frac{1}{(S+40)(S^{2}-3920)} \begin{bmatrix} +S(S+40) & -(-3920)(S+40) & +0 \\ -(-1)(S+40) & +S(S+40) & -0 \\ +(-1)(15\cdot34) & -S(15\cdot34) & S^{2}-3920 \end{bmatrix}$$

$$= \frac{1}{(s+40)(s-3920)} \begin{bmatrix} s(s+40) & s+40 & -15.34 \\ 3920(s+40) & s(s+40) & -15.34s \\ 0 & 0 & s-3920 \end{bmatrix}$$

$$C(sI-A)^{-1}B = \frac{2x1x(-15.34)}{(s+40)(s^{2}-3920)} \Rightarrow G(s) = \frac{-30.68}{(s+40)(s^{2}-3920)}$$

- → order of G(G) = 3. (degree of denominator)
- → Type O system (no integrators)
- \rightarrow There is Right Hand Plane pole at $S=+\sqrt{3920}$, therefore the system in unitable