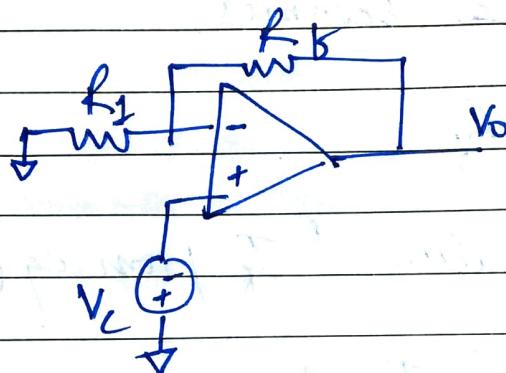



#

Input Bias Current

How to compensate the output offset due to input bias current?



Conceptual Development

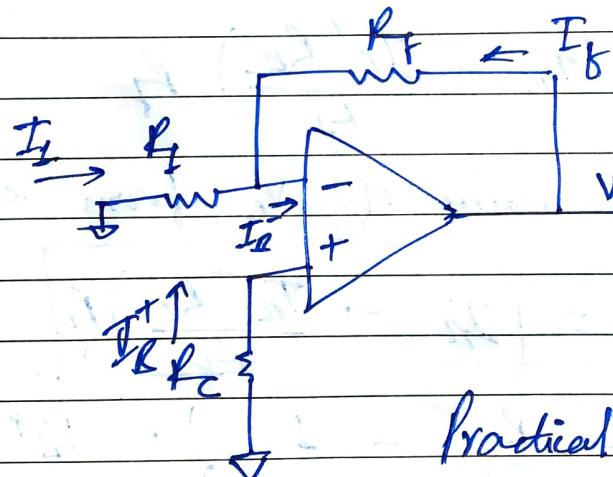

Practical Implementation.

$$\text{Here, } V_C = I_B R_C \quad \text{---(1)}$$

$$V_C = I_B R_I \quad \text{---(2)}$$

$$V_O - (-V_C) = I_F R_F$$

$$V_O + V_C = I_F R_F \quad \text{---(3)}$$

$$\text{Also, } I_B + I_F = I_E \quad \text{---(4)}$$

Because of compensation,

$$V_o = 0$$

Then, Eqⁿ (2) becomes.

$$V_C = I_F R_F$$

Substituting value of I_F from eq (4),

$$V_C = (I_R - I_S) R_F$$

Substituting value of I_S from eq(1) + (2),

$$V_C = \left(I_R - \frac{I_A^+ R_C}{R_L} \right) R_F$$

Substituting value of V_C from eq(1),

$$\boxed{I_A^+ R_C = \left(I_R - \frac{I_A^+ R_C}{R_L} \right) R_F}$$

$$\Rightarrow \frac{R_C}{R_F} + \frac{R_C}{R_L} = 1 \quad \left\{ \therefore I_A^+ = I_R \right\}$$

$$\Rightarrow \boxed{\frac{1}{R_C} = \frac{1}{R_F} + \frac{1}{R_L}}$$

$$\boxed{R_C = R_F \parallel R_L}$$

This configuration compensates the drop and minimize the additional offset voltage error.

#

Input Offset Current

How much output offset is getting created?

From the previous proof,

After substituting values on RHS of eqⁿ(3), we got that,

$$V_o + V_c = \left(I_B^- - \frac{I_B^+ R_C}{R_I} \right) R_f$$

$$\Rightarrow V_o + I_B^+ R_C = I_B^- R_f - \frac{I_B^+ R_C R_f}{R_I}$$

$$\Rightarrow V_o = I_B^- R_f - R_C I_B^+ \left(\frac{R_f R_I}{R_I} + 1 \right)$$

$$\Rightarrow V_o = I_B^- R_f - I_B^+ \times \frac{R_f R_I}{R_I + R_f} \times \frac{R_I + R_f}{R_I}$$

$$\Rightarrow \boxed{V_o = (I_B^- - I_B^+) R_f}$$


Taking $I_{OS} = I_B^- - I_B^+$

$$\boxed{V_o = I_{OS} R_f}$$

IM

Input offset Voltage

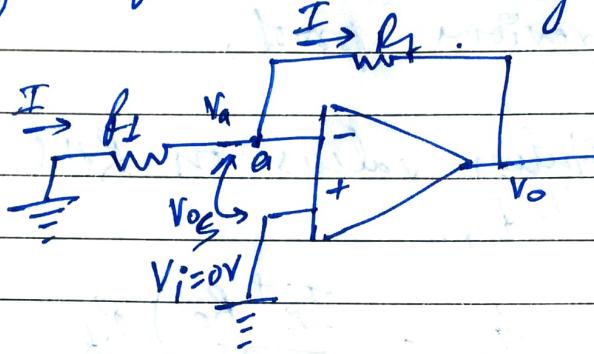Calculate the output voltage due to input offset of an inverting amplifier.



$$\text{Taking } V_a = V_{os}$$

$$I = \frac{-V_a}{R_f};$$

$$V_a - V_o = IR_f$$

$$V_{os} - V_o = -\frac{V_{os}}{R_f} R_f$$

$$\Rightarrow V_o = V_{os} \left(1 + \frac{R_f}{R_1} \right)$$

Tutorial problems :-

(a) Maximum output voltage due to
 V_{ios} & I_B =

$$\begin{aligned}
 & V_{ios} \left(1 + \frac{R_f}{R_s} \right) + R_f I_B \\
 &= \left(10 \times 10^{-3} \left(1 + \frac{10}{1} \right) + 10 \times 10^3 \times 800 \times 10^{-9} \right) V \\
 &= (110 \times 10^{-3} + 3 \times 10^{-3}) V \\
 &= 113 \text{ mV.}
 \end{aligned}$$

(b) As derived earlier,
to compensate the effect of bias current,

$$\begin{aligned}
 R_{comp} &= (R_s \parallel R_f) \\
 &= \frac{R_s R_f}{R_s + R_f} = \frac{1 \times 10^3 \times 10^3}{1 + 10^3} \text{ k}\Omega \\
 &= \frac{10^6}{11} \text{ k}\Omega = 909.09 \text{ k}\Omega
 \end{aligned}$$

(c) Now after connecting the R_{comp} ,
the maximum output offset voltage
becomes

$$\begin{aligned}
 & V_o = V_{ios} \left(1 + \frac{R_f}{R_s} \right) + R_f I_{os} \\
 &= (110 \times 10^{-3} + 10 \times 10^3 \times 50 \times 10^{-9}) V \\
 &= (110 \times 10^{-3} + 0.5 \times 10^{-3}) V \\
 &= 110.5 \text{ mV}
 \end{aligned}$$

2. (a) Maximum ^{output} offset voltage caused by input offset voltage =

$$V_{ios} \left(1 + \frac{R_f}{R_g} \right)$$

$$= 6 \times 10^{-3} \left(1 + \frac{10 \times 10^3}{100} \right) V$$

$$= 606 \text{ mV}$$

(b) Maximum output offset voltage caused by input bias current I_B =

$$= I_B R_f$$

$$= 500 \times 10^{-9} \times 10 \times 10^6 V$$

$$= 5V$$

Analog Signal Processing

Date:	_____
Page:	_____

Power Supply Rejection Ratio

Q10: $PSR = 90 \text{ dB}$

$$PSRR = \frac{\Delta V_o}{\Delta V_s}$$

$$90 = 20 \log \frac{0.5}{\Delta V_s}$$

$$\text{so } \Delta V_s = \frac{0.5}{10^{4.5}} \text{ V} = 15.81 \mu\text{V}$$
$$= 15.81 \mu\text{V}$$

Lecture-4.

Q11: $f_{3dB,cl} = \frac{0.35}{\text{Rise Time}}$


$$= \frac{0.35}{0.2 \times 10^{-6} \text{ s}} = 500 \text{ kHz}$$

Q12: $f_{3dB} \times A(0) = f_{3dB,cl} \times A_{cl}(0)$

$$5 \times 200000 = 50 \times f_{3dB,cl}$$

$$\Rightarrow f_{3dB,cl} = 100 \text{ kHz}$$

Lecture-5

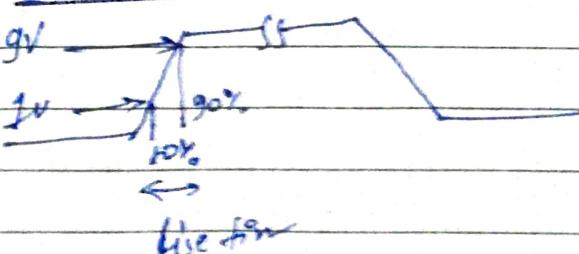


$$\# \text{ Slope} = \frac{\Delta V}{\text{Rise time}}$$

$$\Rightarrow 2V/\mu s = \frac{(9-1)V}{\text{Rise Time}}$$

$$\Rightarrow \text{Rise Time} = \frac{8}{2} \mu s = 4 \mu s.$$

Lecture - 7

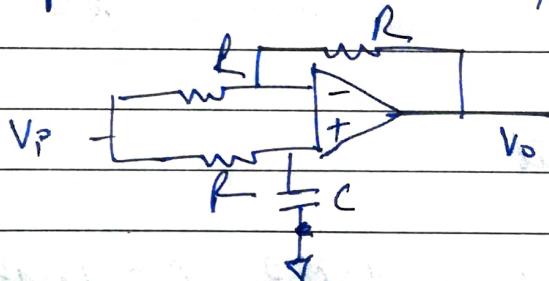- Q-1. Determine the phase angle & the time delay
 " for the circuit shown in figure for a frequency
 of 2kHz , $R = 39\text{k}\Omega$, $C = 1\mu\text{F}$.



Phase-lag Circuit.

$$\Rightarrow \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{1-j\omega RC}{1+j\omega RC}$$

$$\theta = -\tan^{-1}\omega RC - \tan^{-1}\omega RC$$

$$= -2\tan^{-1}(\omega RC)$$

$$= -2\tan^{-1}\left(\frac{f_1}{f_0}\right) \quad f_0 = \frac{1}{2\pi RC}$$

Phase angle: $\theta = -2\tan^{-1}\left(\frac{25 \times 2\pi \times 10^3}{39 \times 10^3}\right)^3$

Phase angle

$$\theta = -2\pi \tan^{-1} \left(\frac{22\pi \times 1 \times 10^3 \times 39 \times 20^3 \times 10^{-9}}{2\pi f_0} \right)$$

$$= -52.22^\circ$$

$$f_0 = \frac{1}{2\pi L C}$$

$$\text{Time delay} = \frac{|\theta|}{2\pi f_0} = \frac{52.22^\circ}{180 \times 2\pi \times 2000}$$

$$= 72.527 \mu\text{s}$$

Q2
= Phase-lead circuit

$$f = 20 \text{ Hz}, R = 39 \text{ k}\Omega, C = 1 \mu\text{F}$$

$$\theta = 180^\circ - 2\tan^{-1} \left(\frac{R}{X_C} \right)$$

$$= 180^\circ - 2\tan^{-1} \left(2\pi f R C \right)$$

$$= 180^\circ + 52.22^\circ = 232.22^\circ$$


$$\approx 127.78^\circ$$

$$\text{Time delay} = \frac{|\theta|}{2\pi f_0} = \frac{127.78^\circ \times \pi}{180^\circ \times 2\pi \times 2000}$$

$$= 177.47 \mu\text{s}$$

Lecture - 9

Date:	
Page:	

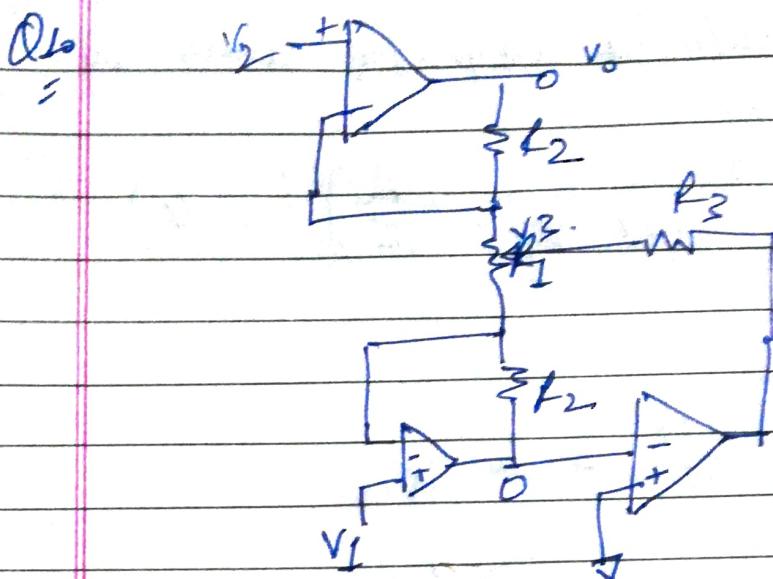

Prove that $V_0 = \left(1 + \frac{R_2}{R_1}\right) (V_2 - V_1)$

when wiper is at middle.

~~$$\Rightarrow V_0 = \left(\frac{R_1 + R_2}{2} + R_2\right) \frac{V_1}{R_2}$$~~

$$\frac{V_0 - V_1}{R_2} = \frac{V_2 - V_1}{\frac{R_1}{2}}$$

$$\Rightarrow V_0 - V_1 = \left(\frac{2R_2}{R_1}\right) \left(V_2 - \left(\frac{R_1 + R_2}{2} + R_2\right) \frac{V_1}{R_2}\right)$$


$$\Rightarrow V_0 = \left(\frac{2R_2 + 1}{R_1}\right) V_2 - \frac{2R_2}{R_1} V_1 \left(\frac{2R_2 + R_1}{2R_2 R_1}\right)$$

$$\Rightarrow V_0 = \left(\frac{2R_2 + 1}{R_1}\right) (V_2 - V_1) - V_1 \left(1 + \frac{2R_2}{R_1}\right)$$

$$\Rightarrow V_0 = (V_2 - V_1) \left(\frac{2R_2 + 1}{R_1} + 1\right)$$

$\text{Q20} =$ For the instrumentation amplifier shown in figure, verify
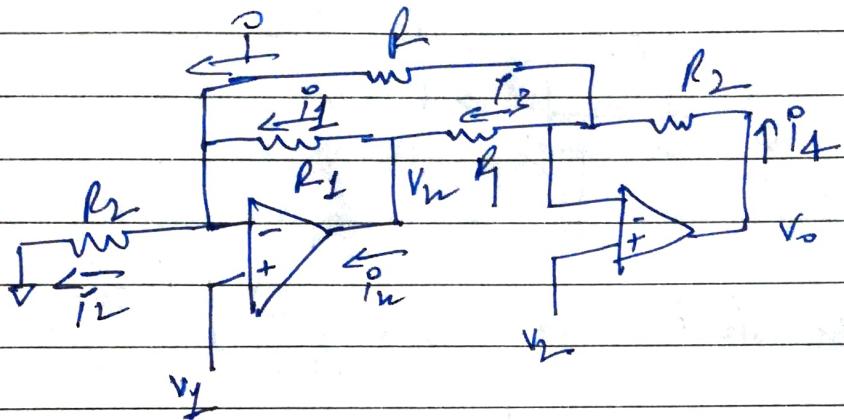
$$V_o = \left(1 + \frac{R_2}{R_1} + \frac{2R_2}{R}\right) (V_2 - V_1)$$



$$V_o - V_2 = R_2 i_4$$

$$i_2 = \frac{V_1}{R_2}$$

$$V_n - V_1 = i_1 R_1$$

$$V_2 - V_L = i R$$

$$i + i_1 = i_2$$

$$\frac{V_2 - V_L}{R} + \frac{V_n - V_1}{R_1} = \frac{V_1}{R_2}$$

$$\Rightarrow \frac{V_n - V_1}{R_1} = \frac{V_1}{R_2} + \frac{V_L}{R} - \frac{V_2}{R}$$

$$\Rightarrow V_n = \left(1 + \frac{R_2}{R_1} + \frac{R}{R}\right) V_1 - \frac{R}{R} V_2$$

$$I_4 = I_3 + I$$

$$\frac{V_0 - V_2}{R_2} = \frac{V_2 - V_1}{R} + \frac{V_2 - V_1}{R}$$

$$\Rightarrow \frac{V_0 - V_2}{R_2} = \frac{V_2 \left(1 + \frac{R_1}{R} \right) - \left(1 + \frac{R_2}{R} + \frac{R_1}{R} \right) V_1}{R_1} + \frac{V_2 - V_1}{R}$$

$$\Rightarrow V_0 = V_2 \left(1 + \frac{R_2}{R} + \frac{R_1}{R} \right) - \frac{V_1}{R_1} \left(1 + \frac{R_1}{R_2} + \frac{R_1}{R} \right) V_1 + \left(\frac{V_2 - V_1}{R} \right) R_2$$


$$\Rightarrow V_0 = V_2 \left(1 + \frac{R_2}{R_1} + \frac{R_2}{R} \right) - V_1 \left(\frac{R_2}{R_1} + \frac{1}{R_1} + \frac{R_2}{R} \right) + \left(\frac{V_2 - V_1}{R} \right) R_2$$

$$\Rightarrow V_0 = (V_2 - V_1) \left[1 + \frac{R_2}{R_1} + \frac{R_2}{R} + \frac{R_1}{R_2} \right]$$

$$\Rightarrow \boxed{V_0 = \left(1 + \frac{2R_2}{R} + \frac{R_1}{R_2} \right) (V_2 - V_1)}$$

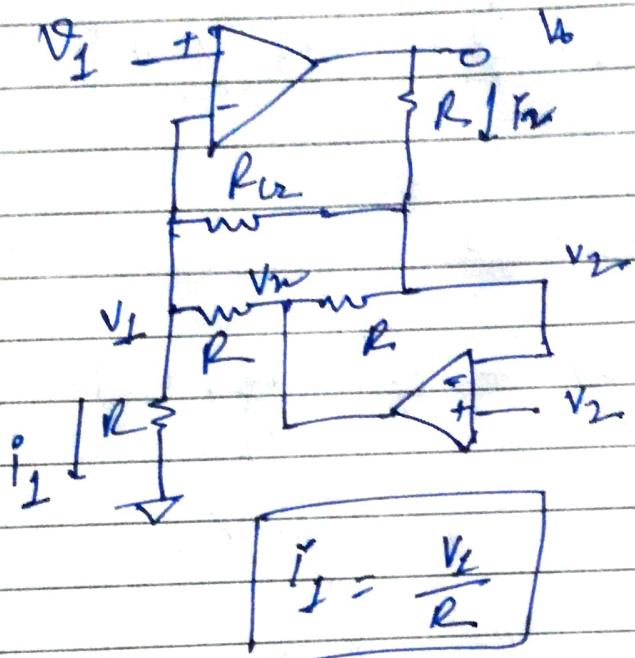Q3:- For the given amplifier below, show that

$$V_o = 2 \left(1 + \frac{R_2}{R_{in}} \right) (V_2 - V_1)$$



$$\frac{V_2 - V_1}{R_{in}} + \frac{V_m - V_1}{R} = \frac{V_1}{R}$$

$$\Rightarrow \frac{V_m - V_1}{R} = V_1 \left(\frac{1}{R} + \frac{1}{R_{in}} \right)$$

$$\Rightarrow V_m = V_1 \left(2 + \frac{1}{R_{in}} \right) - \frac{R}{R_{in}} V_2$$

$$\frac{V_o - V_2}{R} = \frac{V_2 - V_1}{R_{in}} + \frac{V_2 - V_1}{R}$$

$$\Rightarrow \frac{V_o - V_2}{R} = \frac{V_2 - V_1}{R_{in}} + \frac{V_2 \left(1 + \frac{R}{R_{in}} \right) - V_1 \left(2 + \frac{1}{R_{in}} \right)}{R}$$

$$\Rightarrow V_0 = \frac{V_2(R_2 + r)}{R_2} - V_1 \frac{R_2}{R_2}$$

$$+ V_2 \left(1 + \frac{r}{R_{12}} \right) - V_1 \left(2 + \frac{r}{R_{12}} \right)$$

$$\Rightarrow V_0 = 2V_2 \left(1 + \frac{r}{R_{12}} \right) - 2V_1 \left(1 + \frac{r}{R_{12}} \right)$$

$$\Rightarrow \boxed{V_0 = 2 \left(1 + \frac{r}{R_{12}} \right) (V_2 - V_1)}$$

Z